

A new 130 nm FE readout chip for microstrip tracking detectors



Aurore Savoy-Navarro ¹⁾, Albert Comerma ²⁾, E. Deumens ³⁾,
Thanh Hung Pham ¹⁾, Rachid Sefri ¹⁾

¹⁾*LPNHE-Université Pierre et Marie Curie/IN2P3-CNRS, Fr*

²⁾*Universitat de Barcelona. Dept d'Estructura i Constituents de la Materia, Sp*

³⁾*IMEC, Leuven, Be*


LCWS'o8, Chicago, Nov 16-20

Synopsis




- Results from SiTR_130-4
- Design and foundry of the new SiTR_130-88
 - Perspectives

- 
- Results from SiTR_130-4
 - Design and foundry of the new SiTR_130-88
 - Perspectives


SiTR_130-4

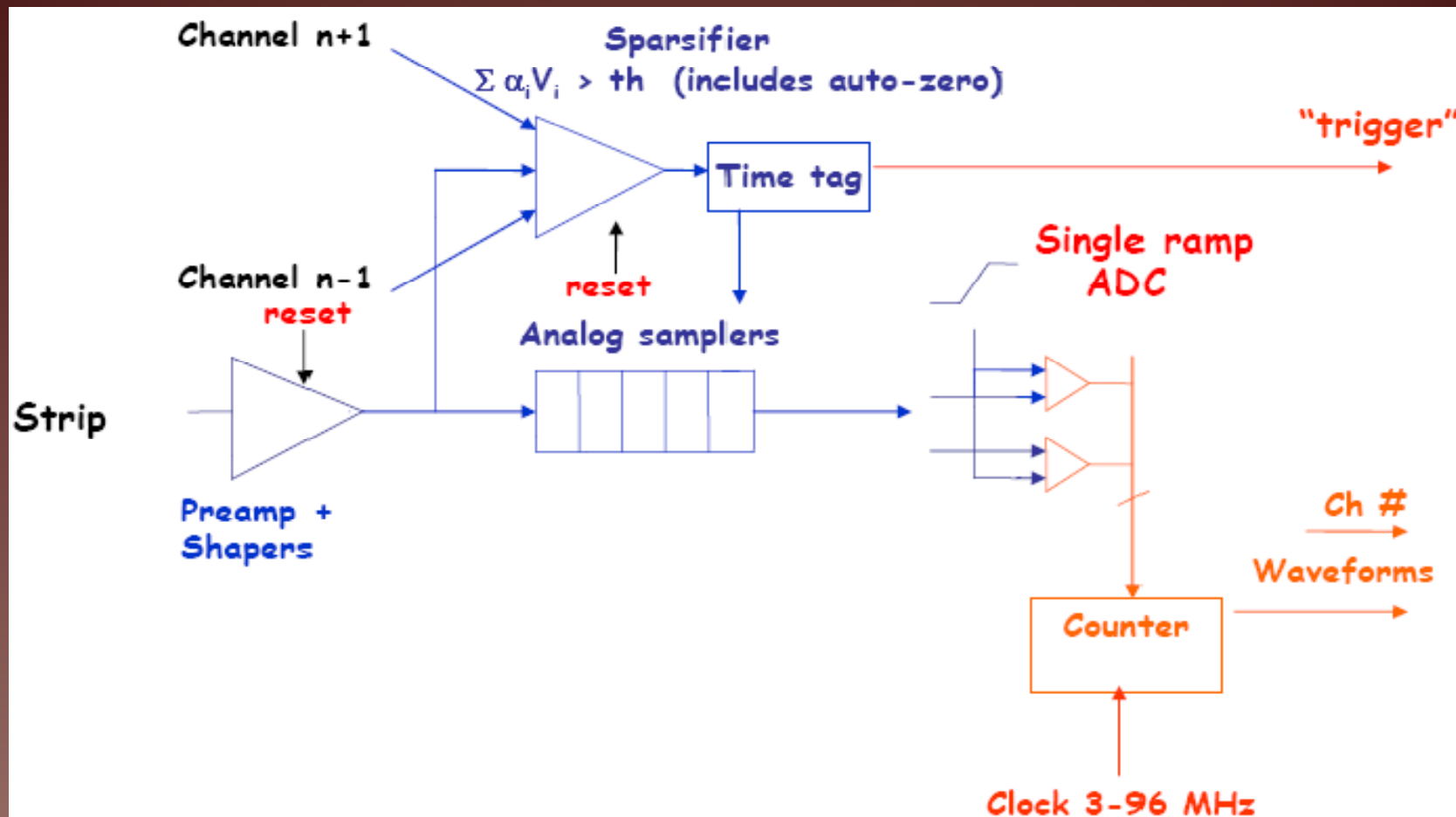

SiTR_130-4: performances

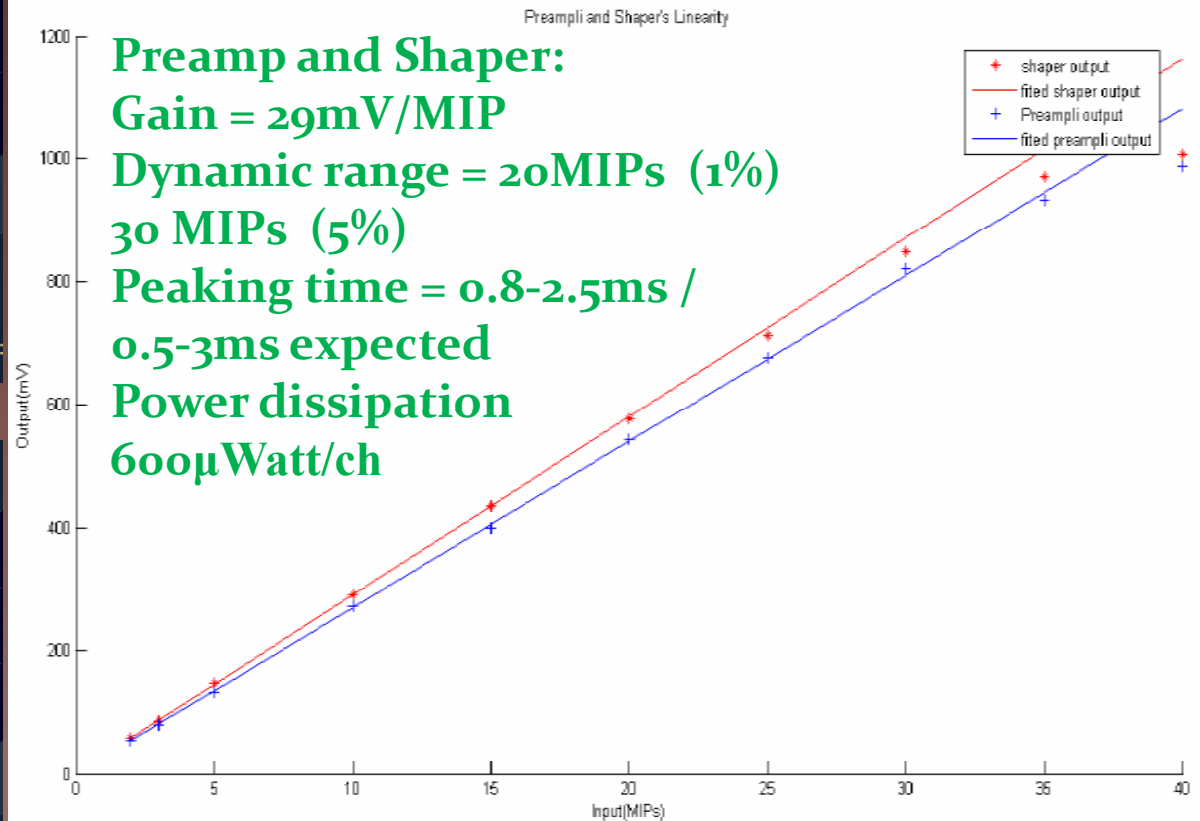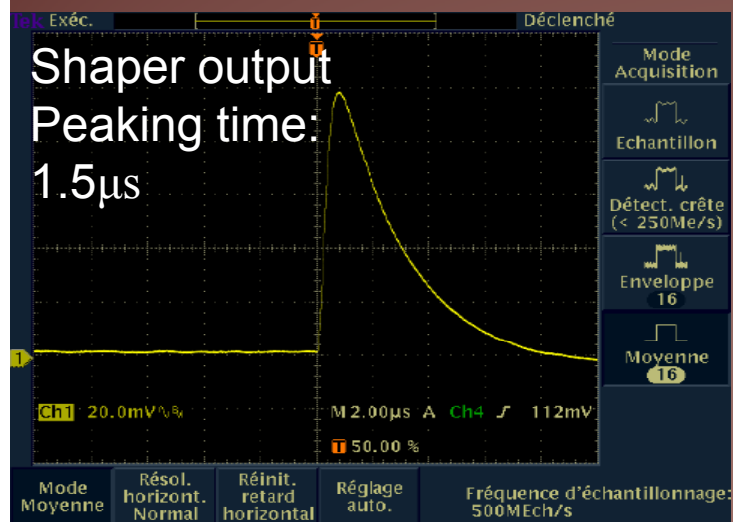
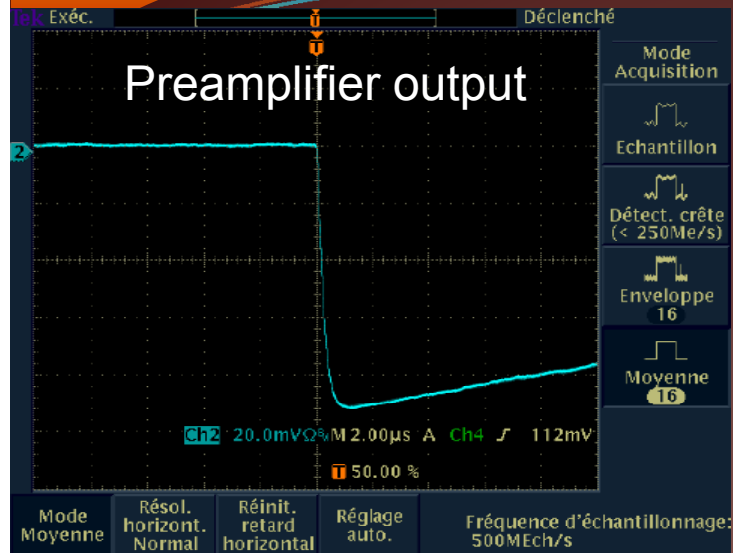


SiTR_130-4: performances (cont'd)

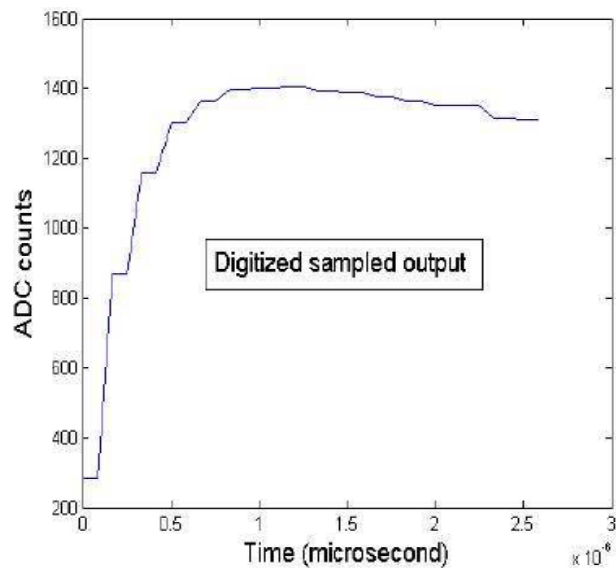

Digitized analogue
pipeline output test
pulse (left) and Laser
response of detector
+ 130nm chip (right)

Digital oscilloscope

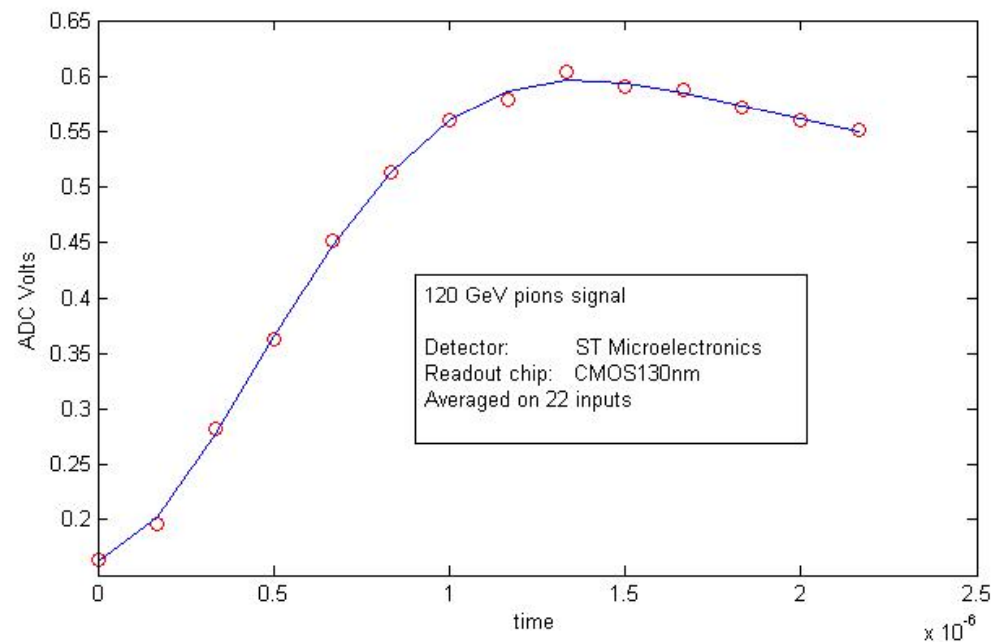 


SiTR_130-4: test beam performances




Results with the new HPK + SiTR-130

Black=beam off, red=beam on; 1 strip S/N 18

1 chip: S/N ~ 23

 

 
Test beam at SPS
CERN, Oct 2007
combined with EUDET
MAPS telescope



Also extensive studies with Sr90 source at Lab test bench
The beam test includes a collaborative effort with several SiLC institutions
(CU Prague, IFCA, IEKP, HEPHY, LPNHE, OSU, Torino U./INFN, CERN and
DESY collaboration as well)

- 
- Results from SiTR_130-4
 - Design and foundry of the new SiTR_130-88
 - Perspectives

SiTR_130-88 schema

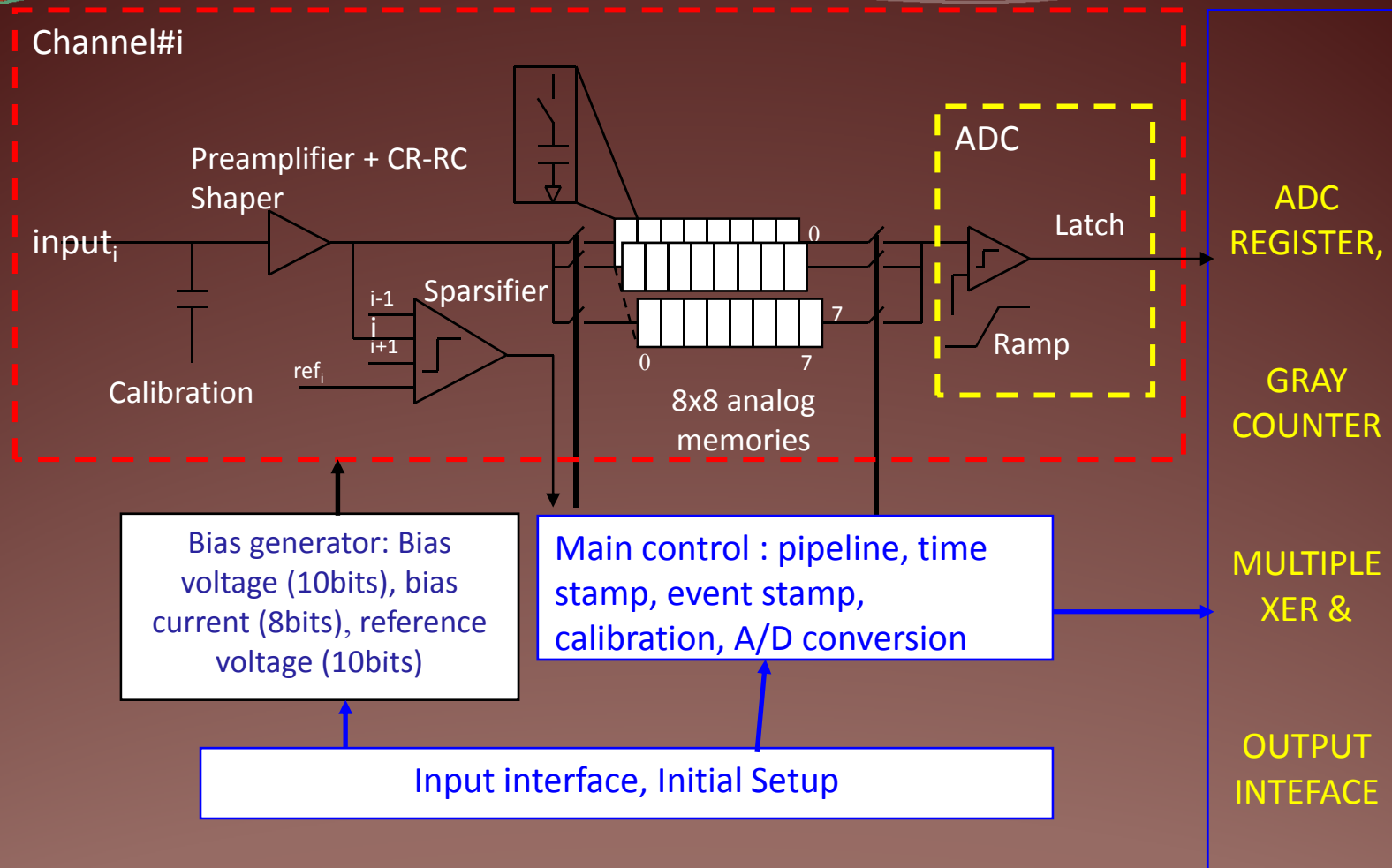

After very encouraging results obtained with the first pre-prototype
Go to the full version: SiTR_130-88

Main features of new circuit

88 channels (1 test channel): Preamplifier, shaper, sparsifier, analogue pipeline (8x8 cells), 12 bits ADC

2D memory structure: 8x8/channels

Fully digital control:

- Bias voltage(10 bits) and current (8 bits)
- Power cycling (can be switched on and off)
- Shaping time programmable
- Sampling frequency programmable
- Internal calibration (fully programmable 10 bits DAC)
- Sparsifier's threshold programmable per channel
- Event tag and time tag generation


=> High fault tolerance

=> High flexibility, robustness

.....

2 Trigger modes: Internal (Sparsification integrated)
External (LVTTL) for beam test


LAYOUT VIEW and PHOTOGRAPH

 

Size: 5mmx10mm
88 channels (105um pitch)
105umx3.5mm/channel

Analog: 9.5mmx3.5mm
Digital : 9.5mmx700um

 
Submitted June 24th '08, received September 12 the naked chips



Photograph of the new chip SiTR_130-88

New readout chip in 0.13 μm : packaged version

BONDING DIAGRAM FOR CQFP208 PACKAGE

 

Package 208 pins



- 50 analog input
- 21 analog test out
- 33 digital pin (22 test pins)
- 107 supply pins

20 packaged chips
delivered October 15th

For a detailed test of chip
functionality & performances

Test is “easy” because the chip is “fully programmable”

Summary of simulation studies

  

Main present results from the simulation studies

Preamplifier:

Charge gain: 27mV/MIP \pm 5%

Linearity: 17 MIP (1%) to 29 MIP (5%)

Shaper: 30mV/MIP \pm 5%

Shaping time: 0.5 to 1.5 μ s

Linearity: idem preamplifier

Noise: 625 + 9 e-/pF (1.5 μ s)

Pipeline (8x8)

Sampling rate (2)

Linearity: idem preamplifier

ADC conversion time: about 85 μ s (48 MHz clock)

Calibration:


Integrated capacitor: 100 fF

Calibration pulse amplitude: 10 bits DAC (same as bias generator)

Overall power dissipation per channel: about 1mWatt

Total, not including power cycling

Summary of simulation studies (con'td)

 

Pipeline Input

Pipeline Output

Write command

Read command

Pipeline simulation

Writing
phase

Reading
phase


Among the big challenges in
designing this chip: to find a way
to perform the
mixed mode simulation

Analogue


Mixed Mode simulation using
AMS Designer - Cadence

Digital

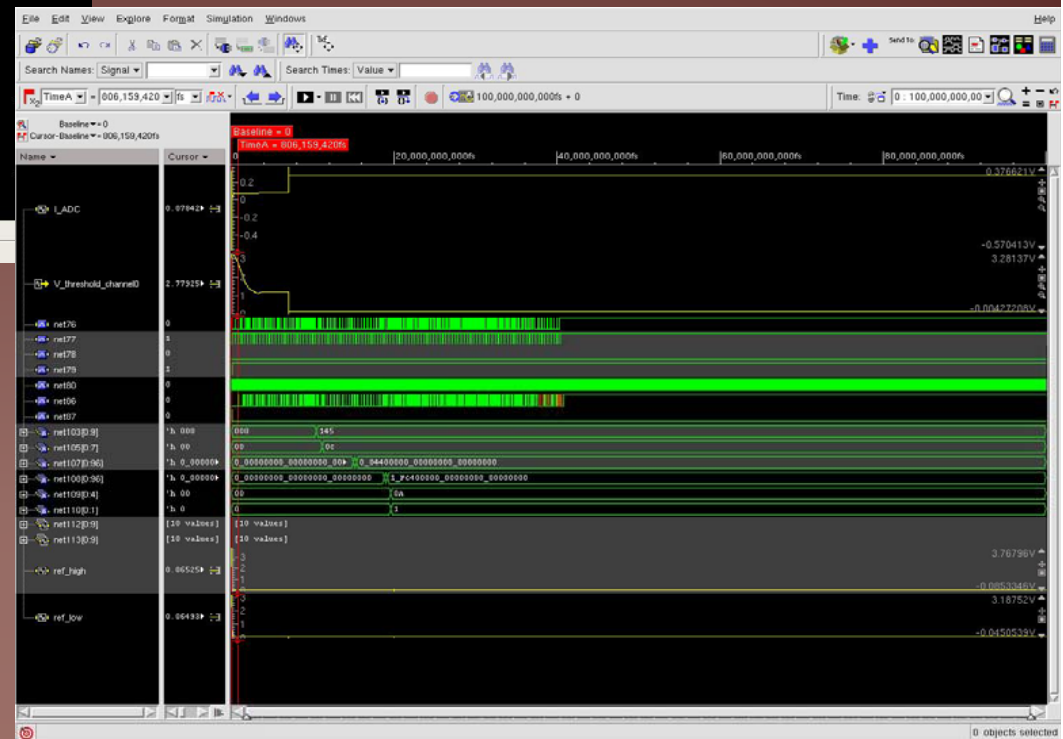Simulation result
Yellow : Analogue signal
Green : Digital signal




Digital part

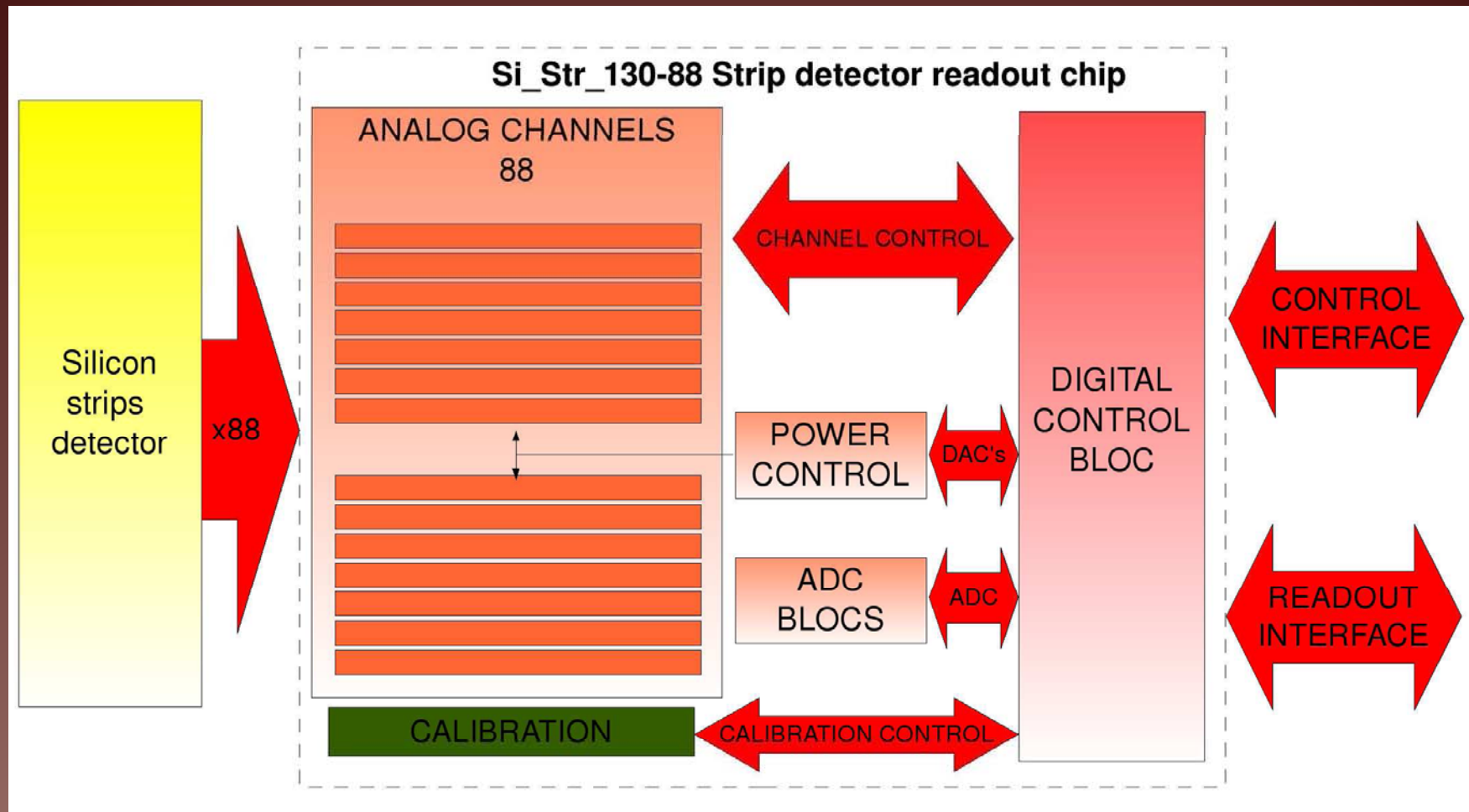

SiTR_130-88: System overview

DAQ during the bunch train


During acquisition;

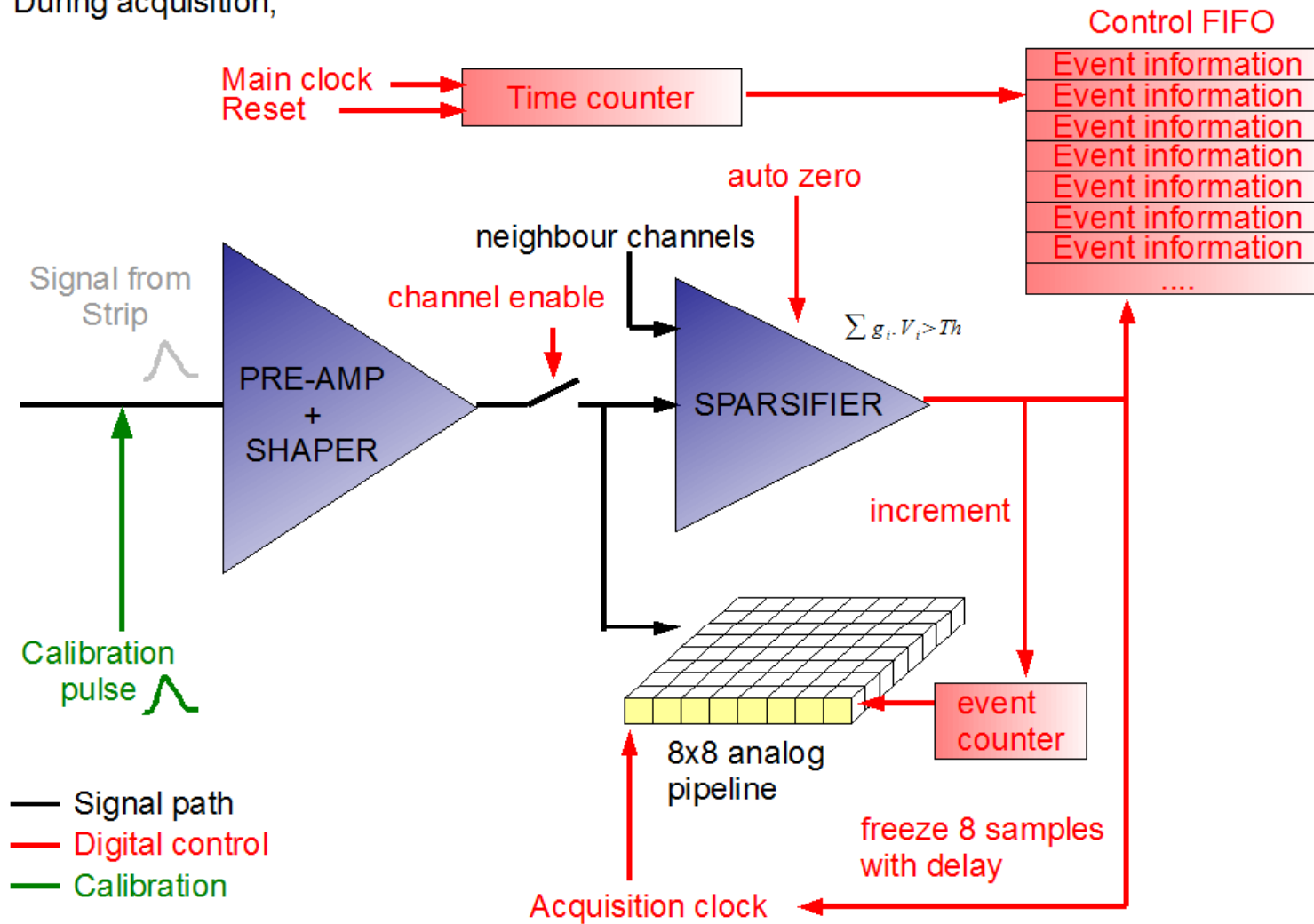


Sampling and conversion time:

All the 88 channels of the chip are converted in parallel.

 
There are 8x8 samples to be converted per channel; the conversion time per channel is approximately $85 \mu\text{s}$ thus a total of 5.44 ms is needed for the conversion



 Reconstruction of the pulse height: 8 samples including pedestal




During IDLE time;

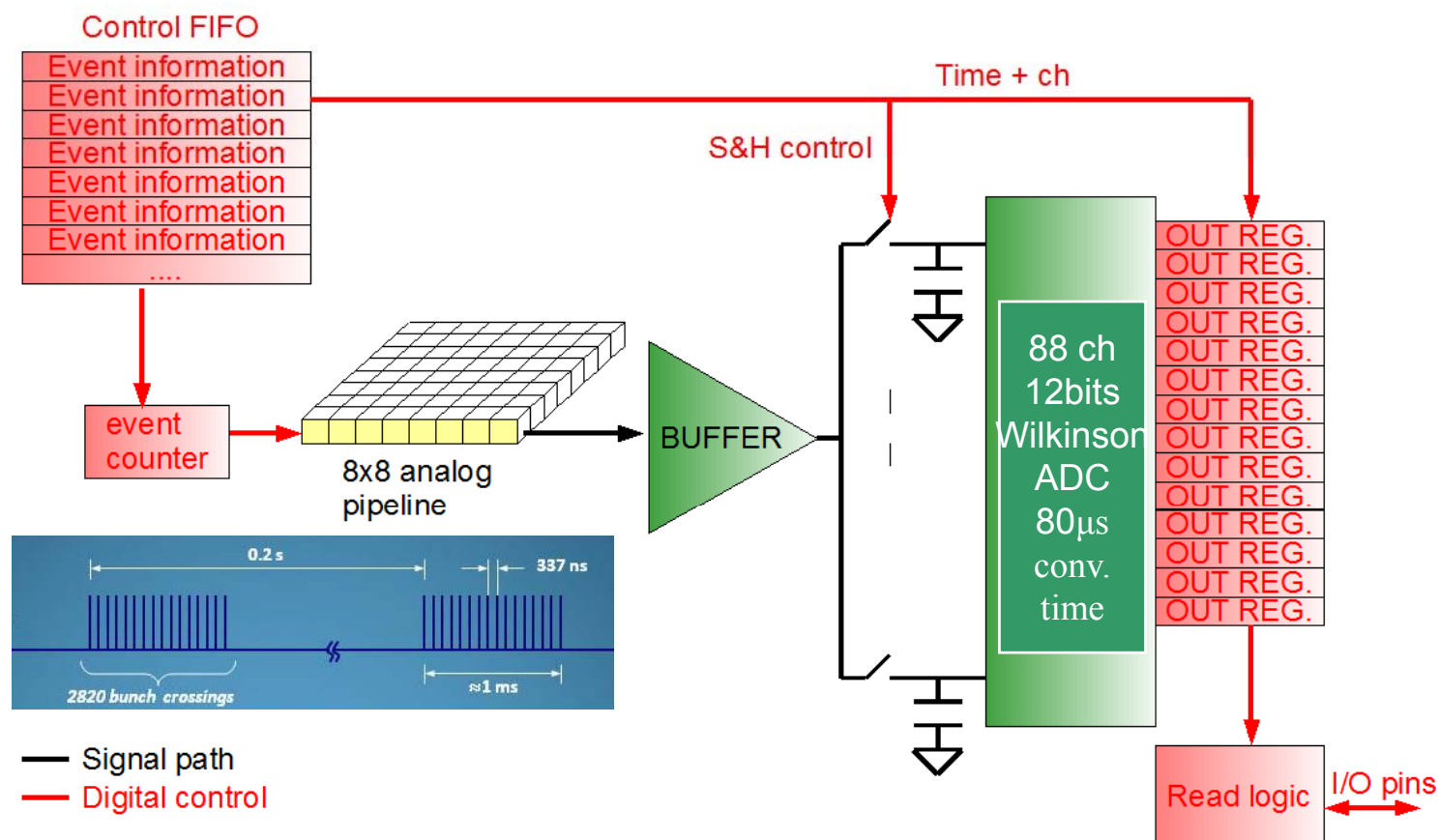

The acquisition control block is constructed around a finite state machine (fsm), with 4 states

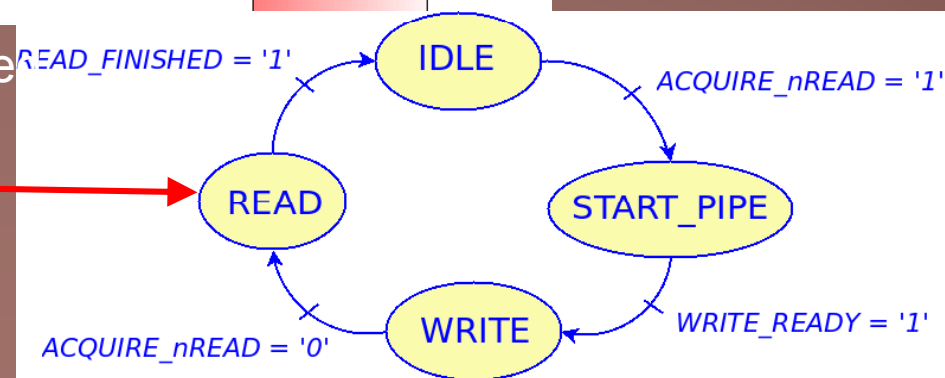(For more information see presentation at the DAQ session)



- 
- Results from SiTR_130-4
 - Design and foundry of the new SiTR_130-88
 - Perspectives

Next version improvements

- Go to basic blocks of 256 channels and build modules of 512 channels or 1024 out of them (multiplexing factor is still under investigation)
 - Thinning of the chip
 - Next version in full wafer process (gain in space)
 - Include latest results from the tests on the present chip
 - Try the 90 nm CMOS technology
-
- For the longer term it is intended to prepare a fast version CLIC-like
 - Pursue the direct connection chip onto the strip detector (bump bonding now, and starting to investigate 3D vertical interconnect as part of the global effort)

NOW WE ARE WORKING ON TESTING THIS CHIP!!