

Serial Powering

Concept, realization and characterization of serially powered pixel modules

Duc Bao Ta

University of Bonn




SiD Meeting SLAC
27. April 2007

Overview

- Motivation for and Concept of *Serial Powering*
(example: ATLAS Pixel Detector)
- Implementation on ATLAS Pixel FE-I3 Modules:
 - Regulator Measurements
 - Design and Test of a *Serial Powering* Module
 - Operation of a Chain of *Serial Powering* Modules (half-stave)
 - Noise Pickup Measurements
- Summary and Outlook


ATLAS Pixel Detector

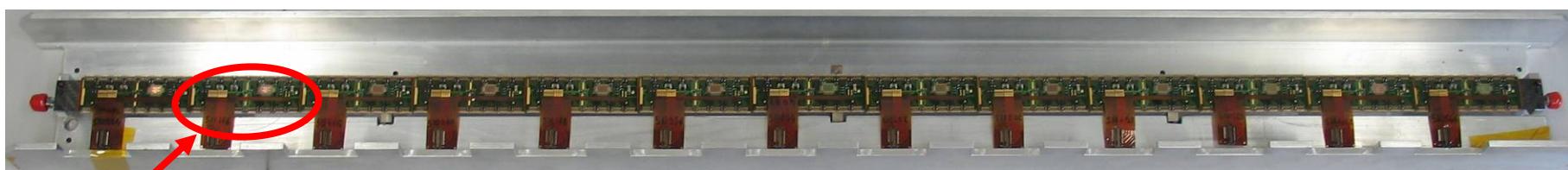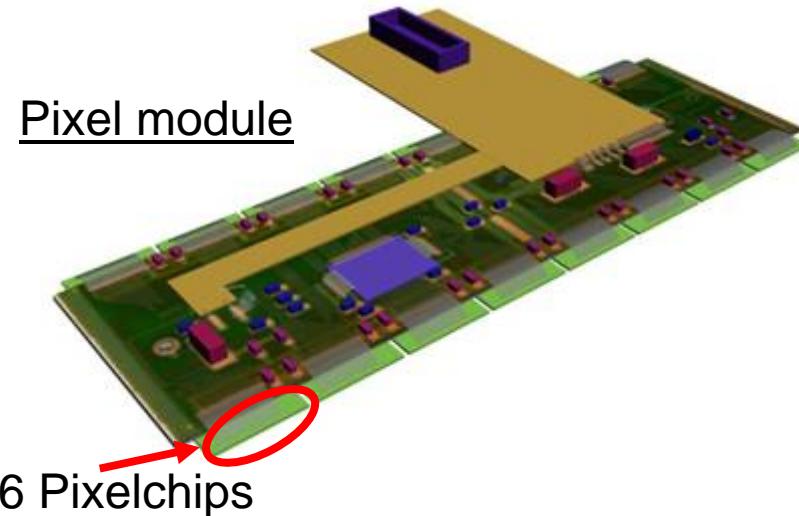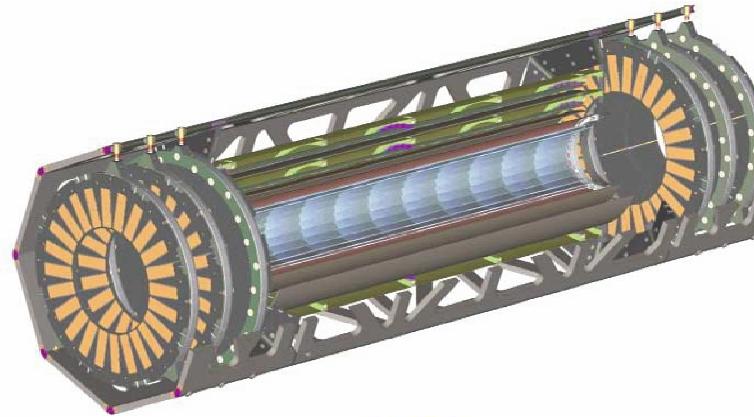- High granularity:
 - 80Mio. output channels
 - 1744 modules
- High power density at low voltages:
 - analog: 1.6V/1.3A
 - digital: 2.0V/1.0A




Motivation and Concept of Serial Powering

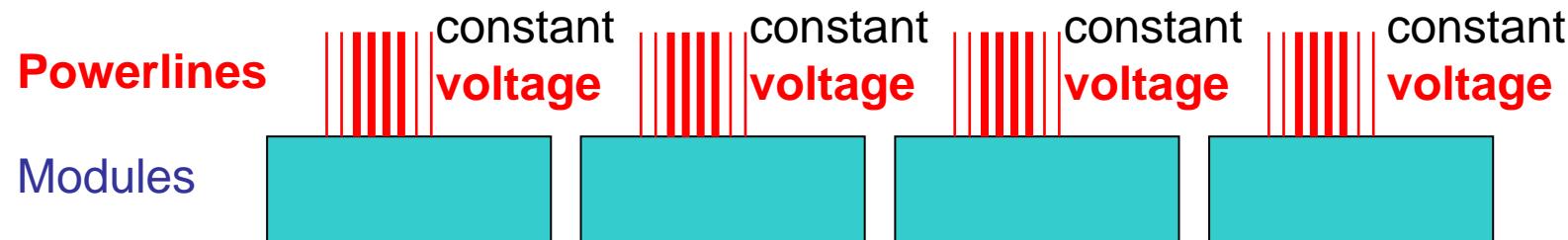- Currently used in the pixel detector, **Parallel Powering**:





- Idea of **Serial Powering**:

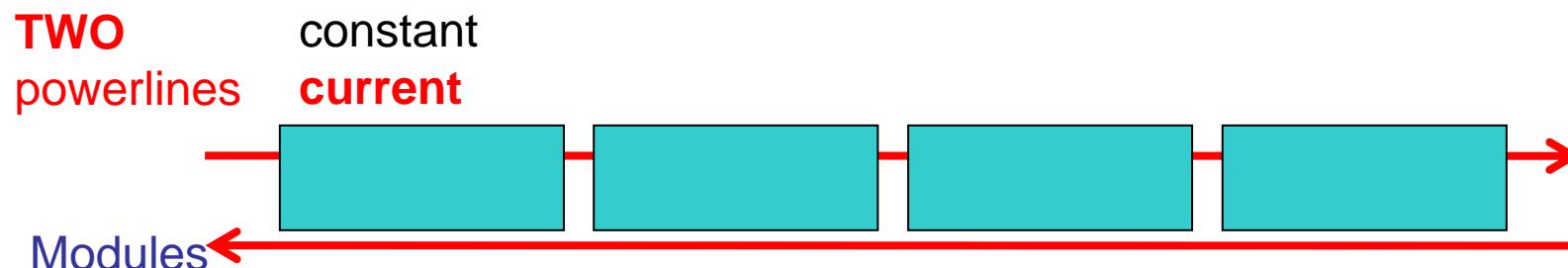


Basic Principle

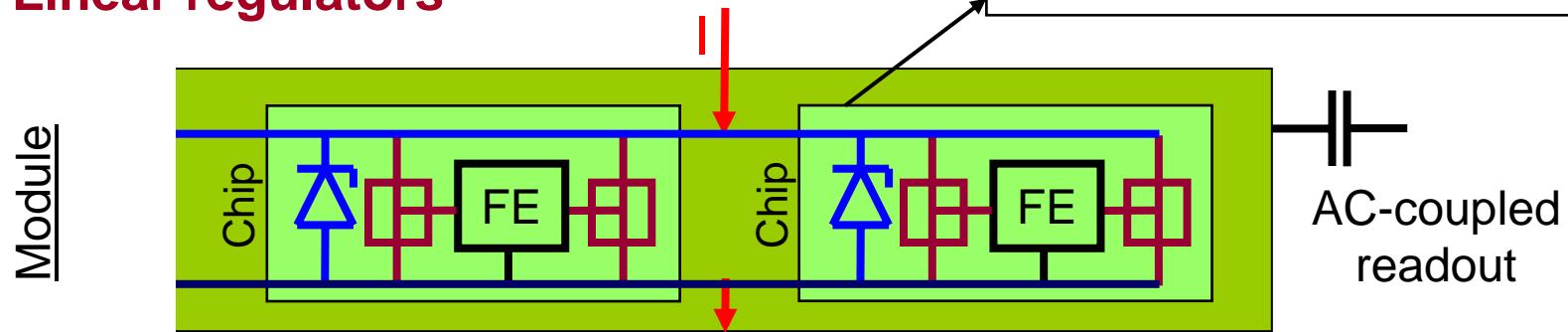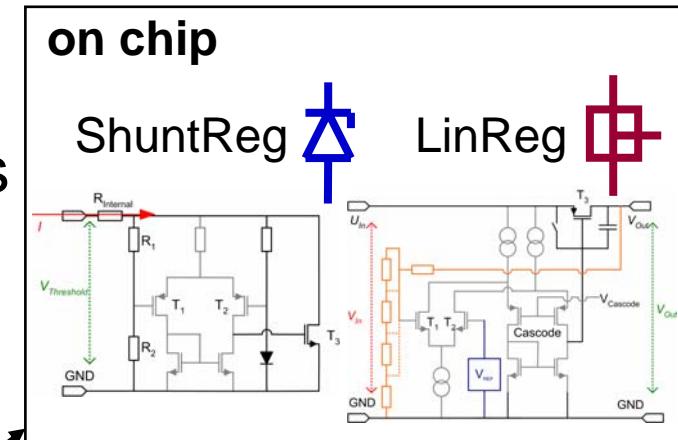- Constant current through all modules
- Voltages generated **on chip** by
 - Shunt regulators
 - Linear regulators



Alternative scheme

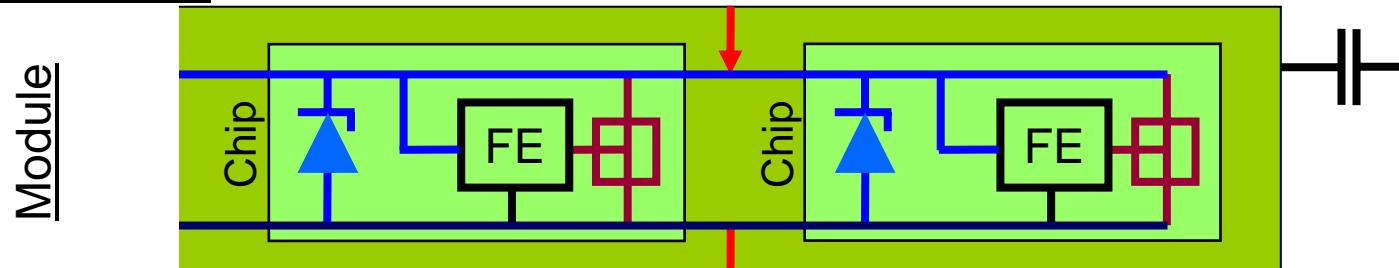

Motivation and Concept of Serial Powering

Advantages of Serial Powering

- Less cables therefore less material in detector
 - power cable length per stave: PP 121m, **SP 2.8m (2.3% of PP)**
 - Radiation length: PP 0.073%, **SP 0.011% (15% of PP)**
- Less power losses in cables
 - Voltage drop: 6.4V
 - power losses per stave: PP max.192W, **SP max.19.2W (10% of PP)**
- **No external, distant regulation** of voltages necessary

Concerns...

Possible disadvantages

- Higher power consumption of modules due to higher current (nom. increase of power consumption 35%)
- Fear of loss of a whole stave/chain due to one defect regulator
- **Noise pickup through power lines**





yes,...but

- Less heat from cables counterbalance the increase of module heat (max. increase of total heat 17%)
- Also: less heat pickup by other systems from cable power losses
- Parallel use of 16 shunt regulators on a module
- This will be addressed later in this talk

Shunt Regulators I3

Designed by Laurant Blanquart

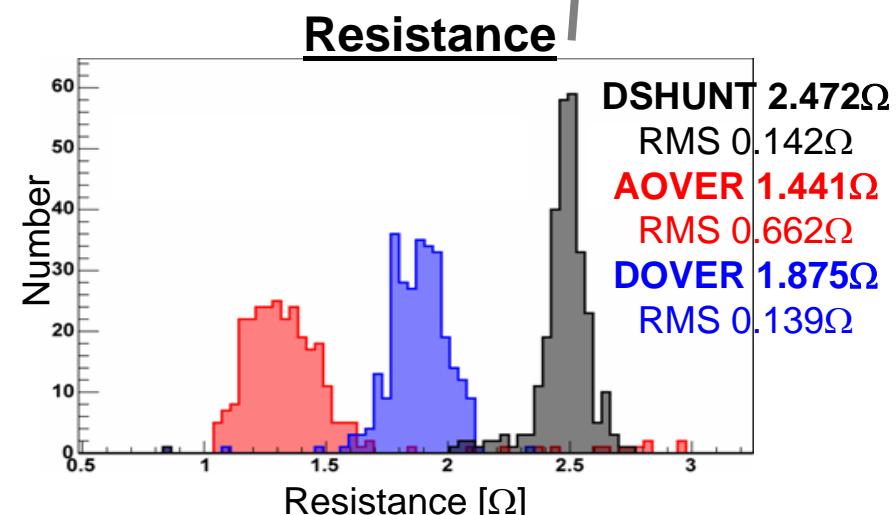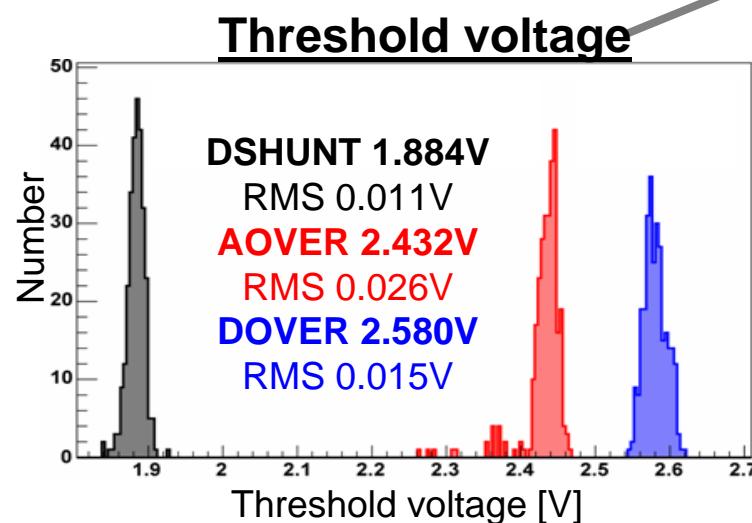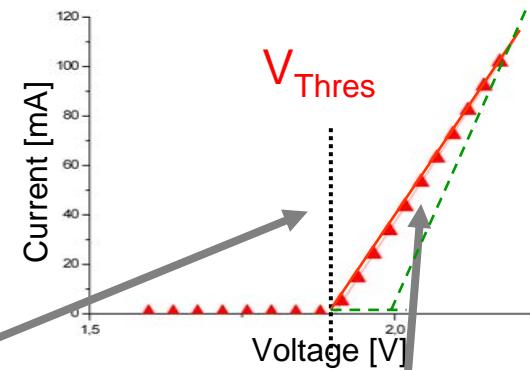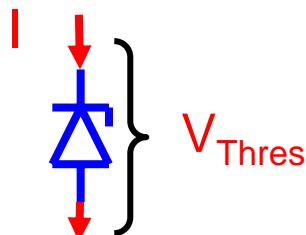- Important properties:
 - Threshold voltage
 - Resistance
- 3 shunt regulators on chip:
 - DShunt (2.0V), AOver (2.4V) and DOver (2.7V)







Regulator Measurements on I3 Chips

Linear Regulators I3

Designed by Laurant Blanquart

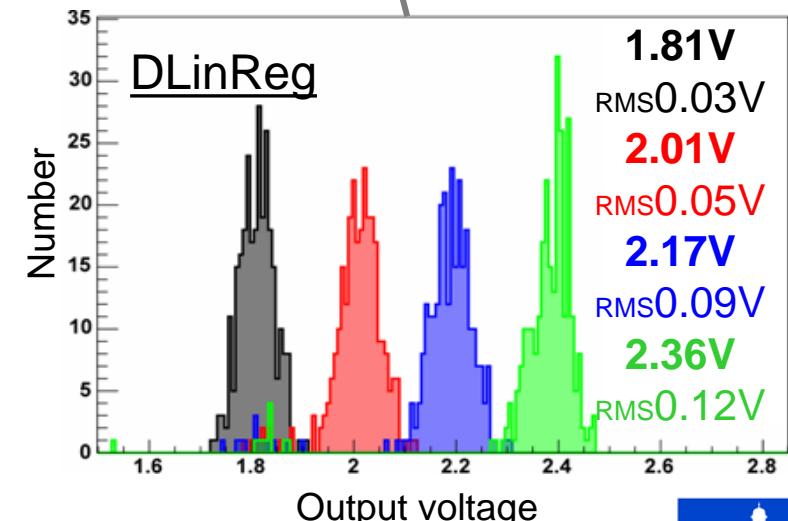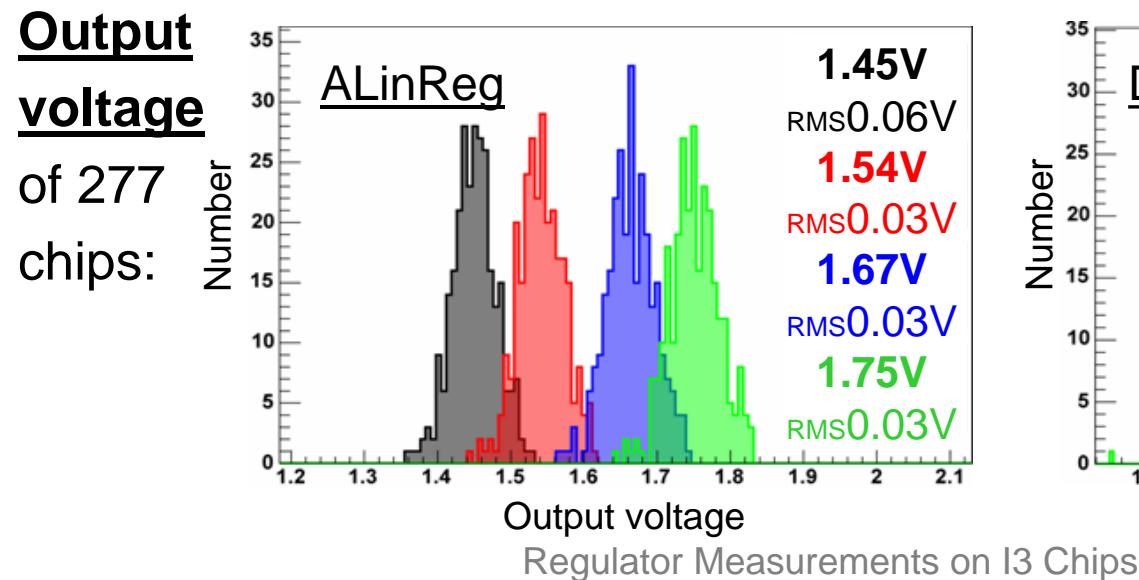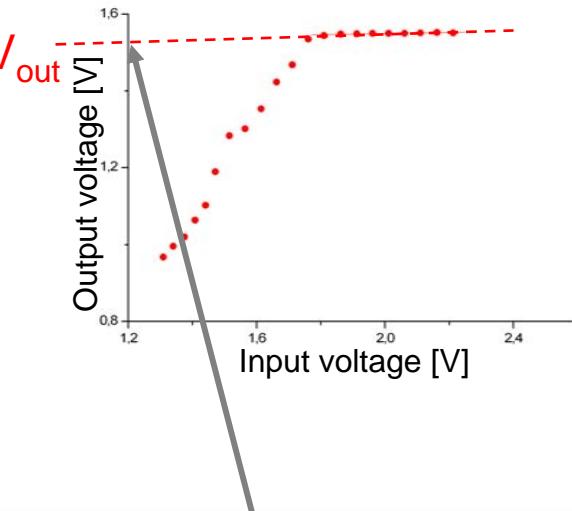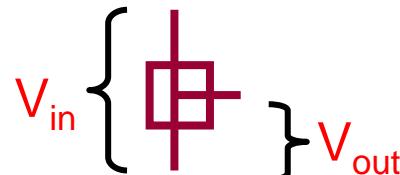
- Important properties:
 - Output voltage
 - Voltage drop ($V_{in} - V_{out}$)
 - Stability vs input voltage or vs load
- 2 linear regulators on chip:
 - ALinReg (1.5V-1.8V) and DLinReg (1.8V-2.4V), both in 4 steps






Voltage drop ($V_{in} - V_{out}$)

ALinReg:


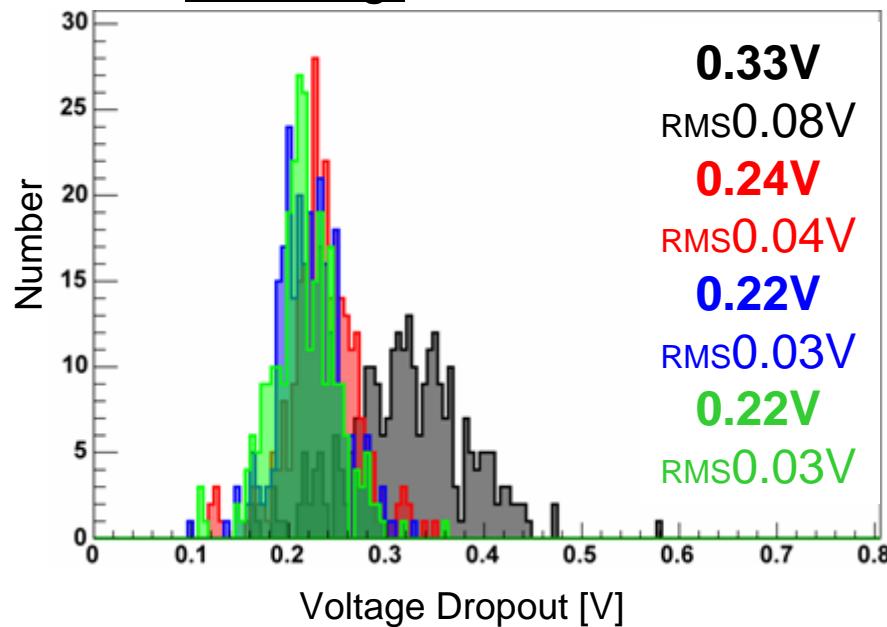


DLinReg:

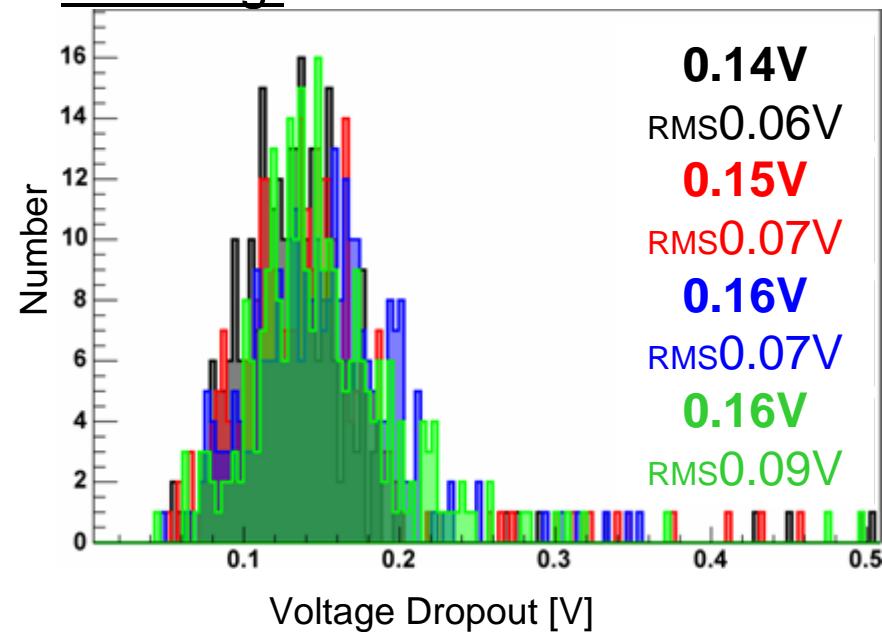

Single Serial Powering module

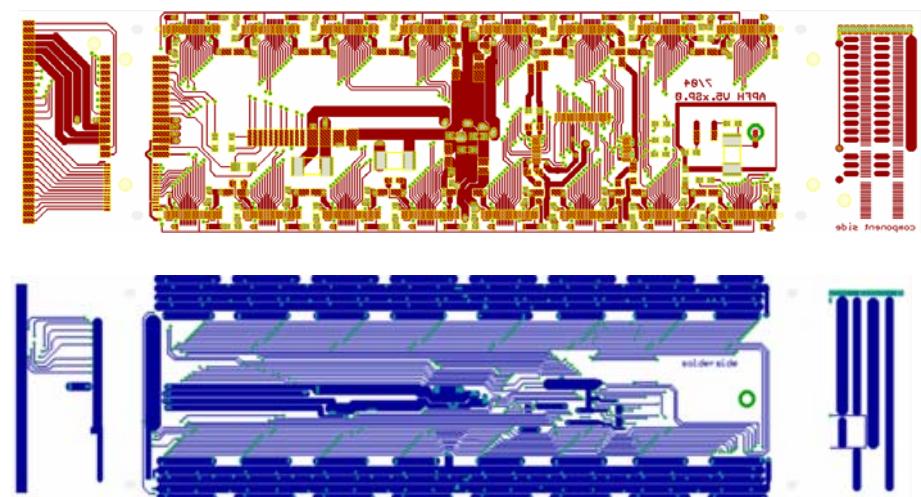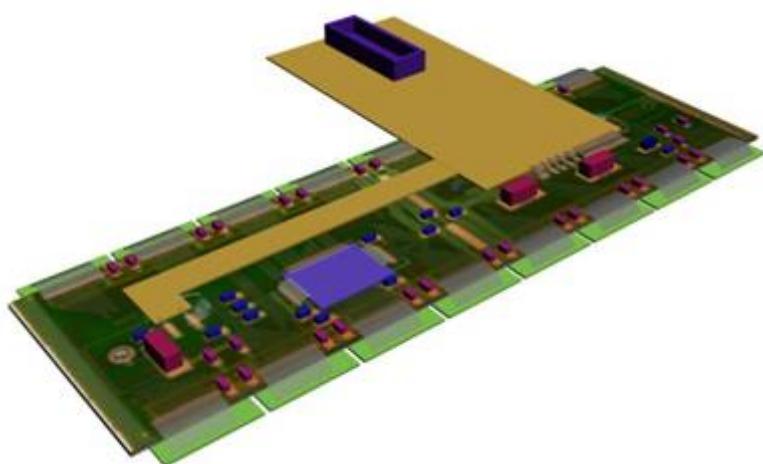- Using already available production chips and dummy/damaged module
- Change bonding scheme / Dedicated flex hybrid




Test of a single Serial Powering module

11


Performance of Single I3 modules

- Single Serial Powering Module performance as good as Parallel Powering Modules (esp. noise)?

- Reminder of SP scheme:

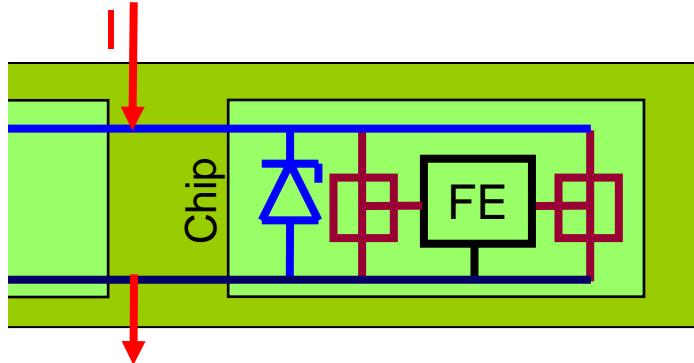

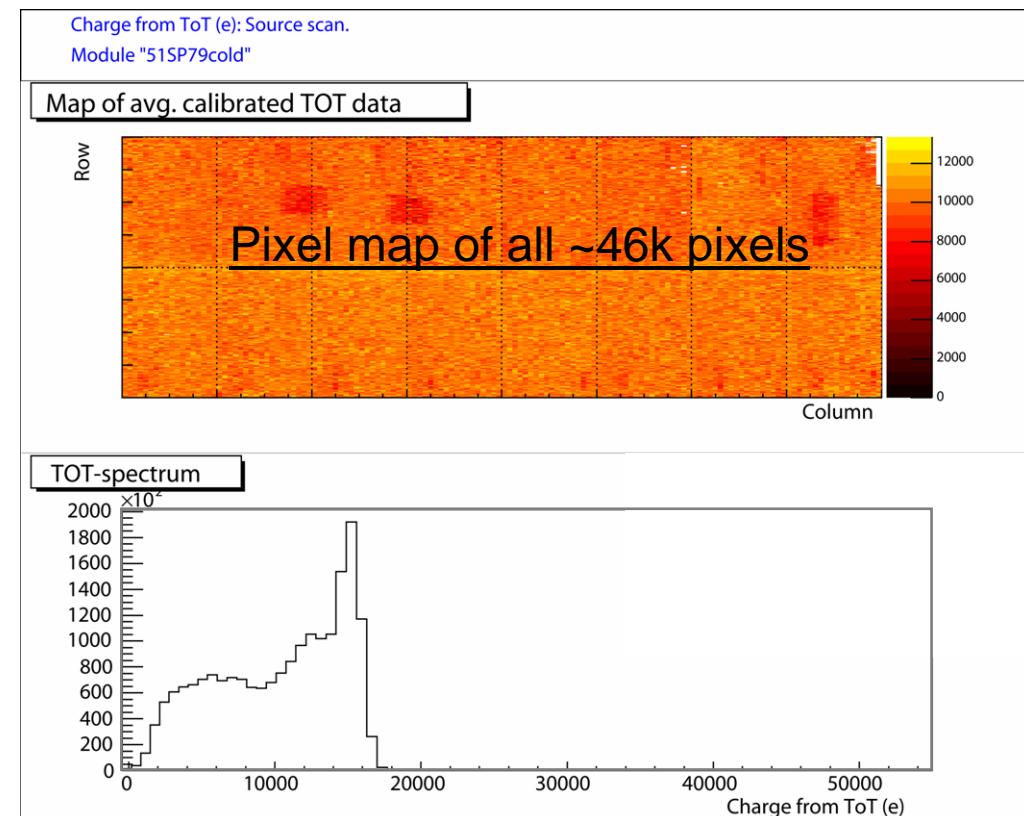- Source scan with ^{241}Am as a qualitative proof



Test of a single Serial Powering module

12




	<i>Serial Powering</i>	Parallel Powering (510471)
Threshold	4226e⁻	4169e ⁻
Dispersion	90e⁻	64e ⁻
Noise	186e⁻	183e⁻
Autotuning	4171e⁻	
Dispersion	70e⁻	
Noise	186e⁻	
In-Time-Threshold	5624e⁻	5532e ⁻
Overdrive (Timewalk)	1451e⁻	1344e ⁻
Crosstalk	0.93% (n)	<1%
ToT@20ke ⁻	30.2ns	28.6ns

Fully working, no difference to PP-Modules

Serial Powering Dummy I3 Half-Stave

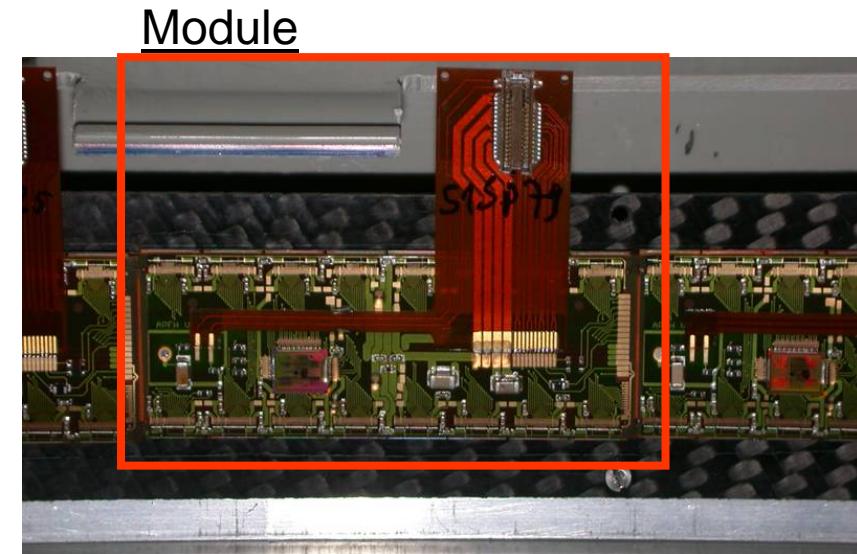- 6 Modules (4 with dedicated *Serial Powering Flex*)
 - Dummy stave structure with cooling pipe
 - Approx. 0.3Mpixels




Half stave




Serial Powering Dummy I3 Half-Stave

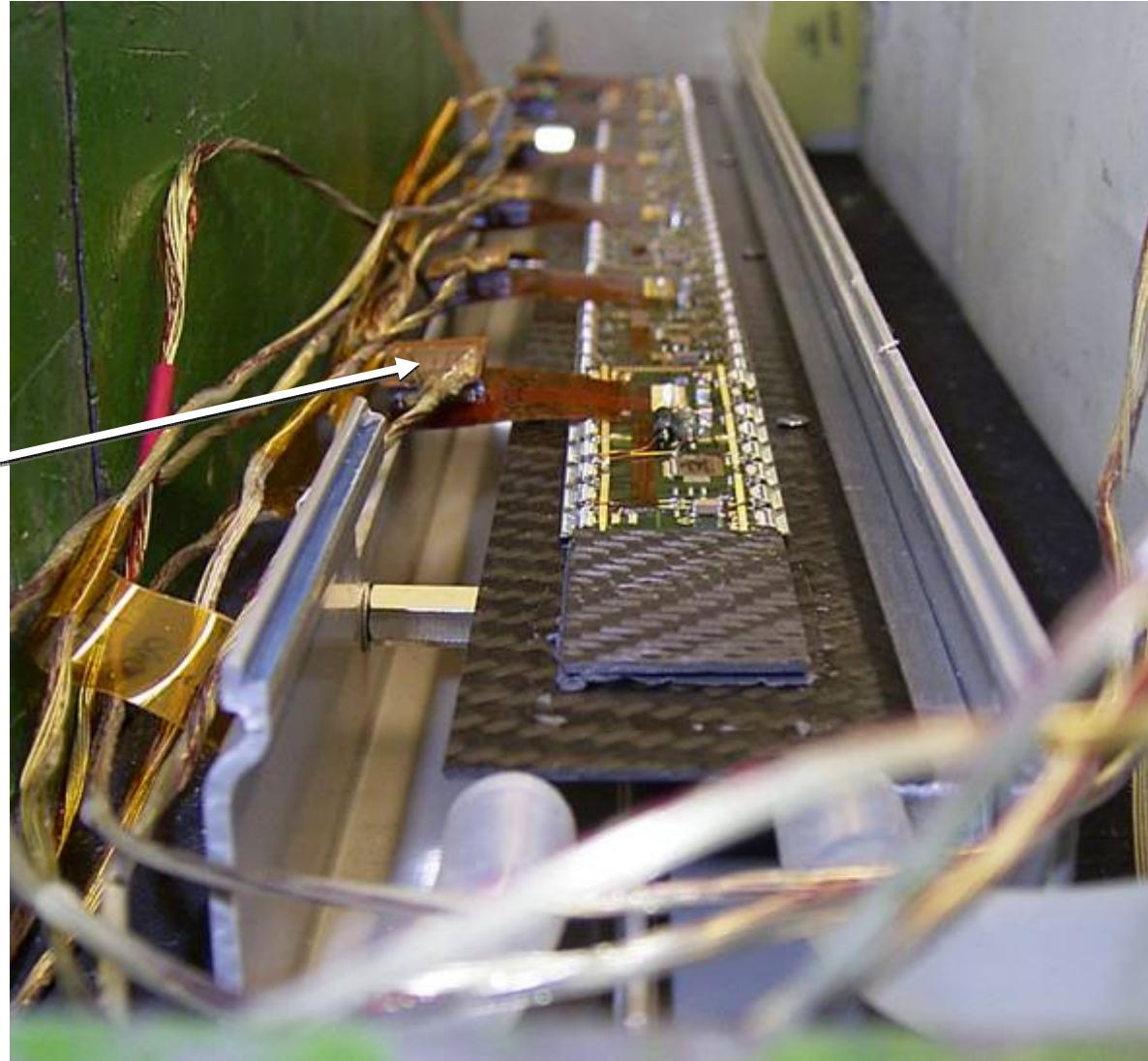PP cables,
serial routing done by
AC-Coupling Board



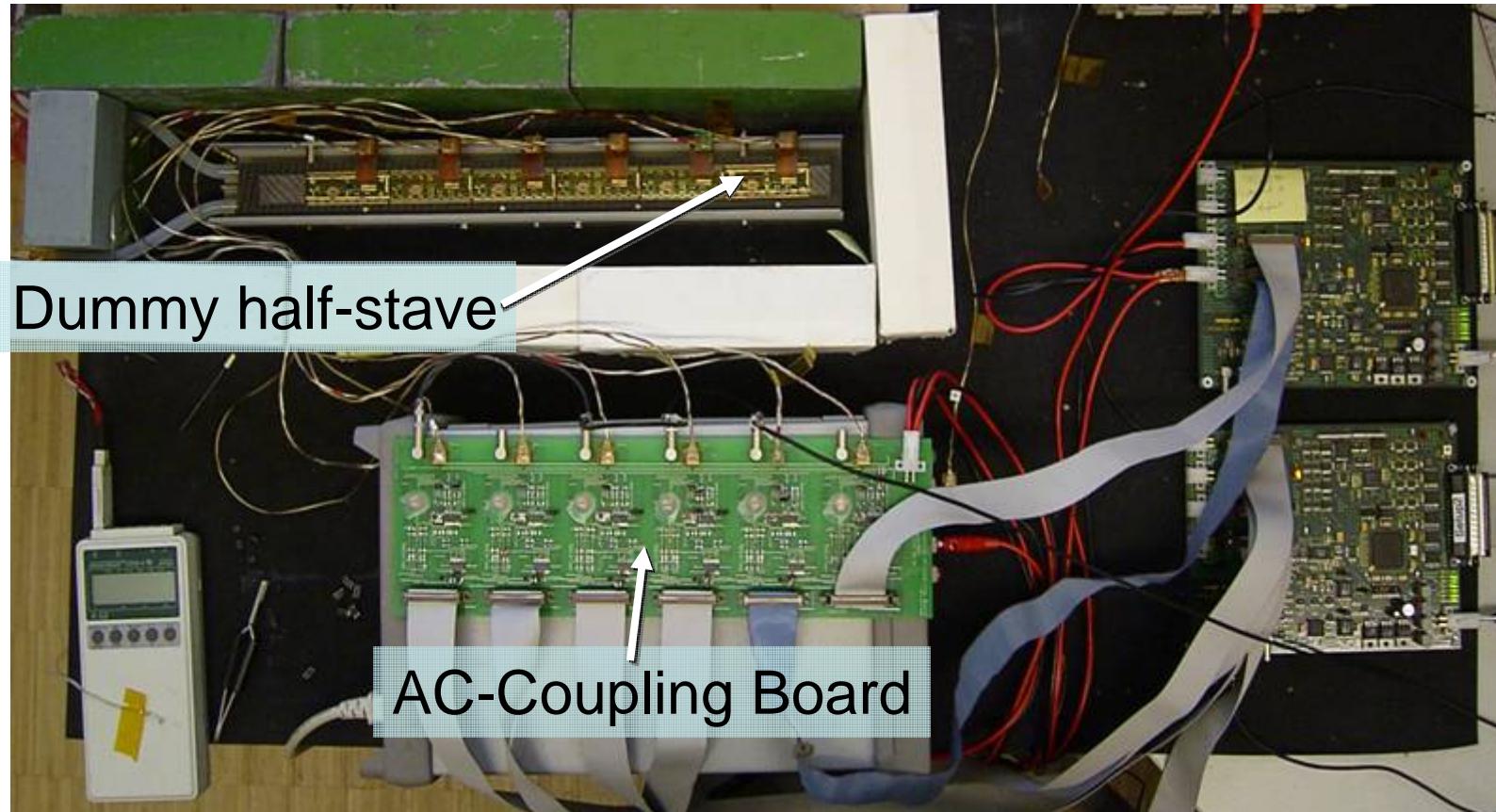- AC-Board & 2 read out systems fully working




Noise Measurements on Dummy Half-Stave



- Full half-stave operation, as good as single module operation?
- XCK and STROBE to all six modules at the same time
- Threshold scan performed on all modules, read-out of two modules at the same time



Threshold Map

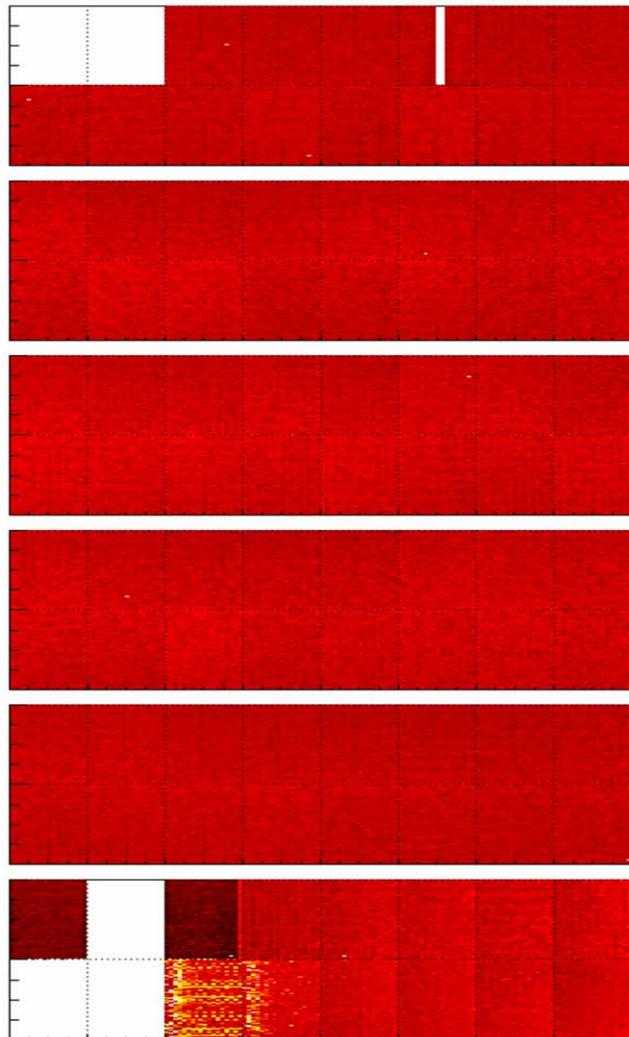

Noise Map

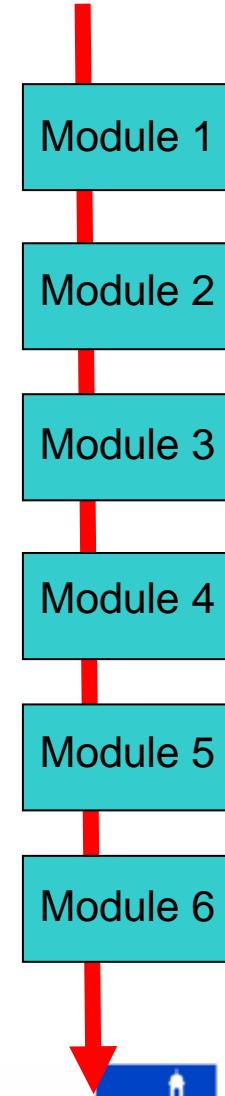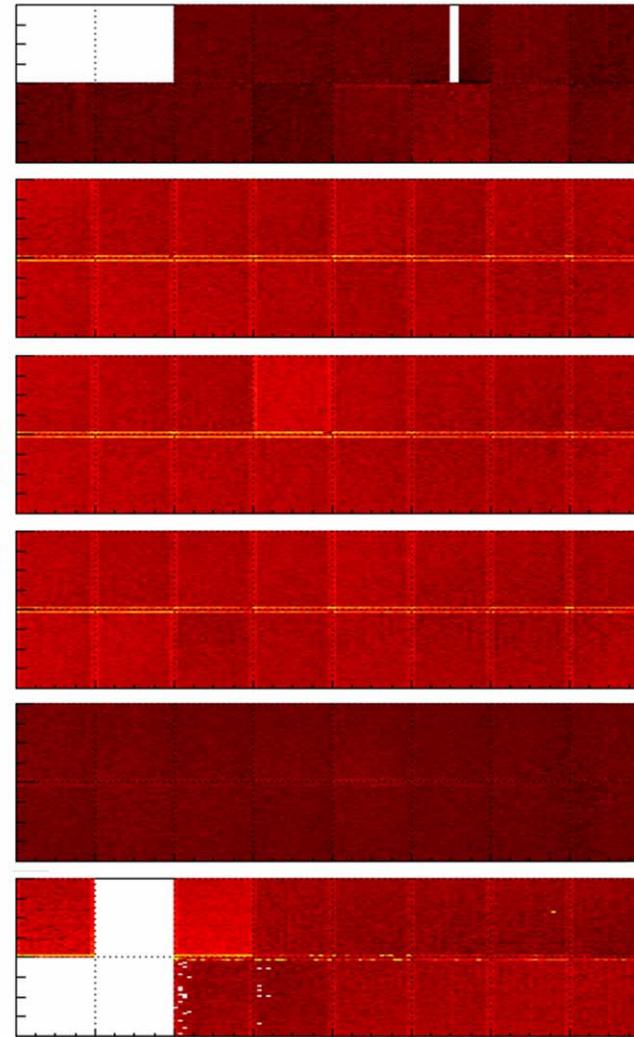

Noise Measurements on I3 Dummy Half-Stave



Threshold [e^-]

(Dispersion [e^-])

4134 (57)

4156 (69)

4173 (70)

4162 (70)

4132 (58)

4160 (91)

Noise [e^-]

(Δ to single SP powered [e^-])

127 (4.4)*

182 (-0.6)

186 (-0.3)


184 (-4.4)

133 (0.0)*

172 (-5.3)


*no sensor

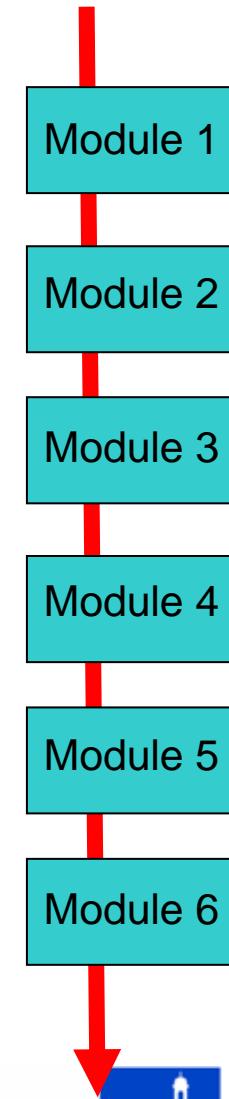- No difference to single-module operation and to Parallel Powered modules





Noise Pickup Global Threshold DAC=0,

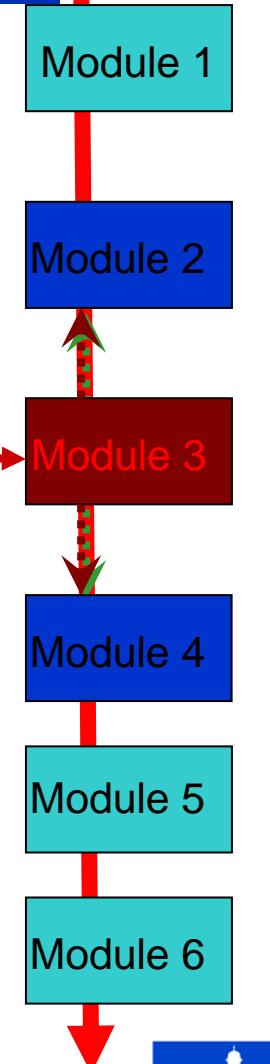- **Big concern:**
Do other modules pickup noise through the power lines?
- Noisy module achieved by setting **Global Threshold DAC=0**
- XCK and STROBE to all six modules **at the same time**
- Threshold scan performed on all modules, read-out of two modules at the same time





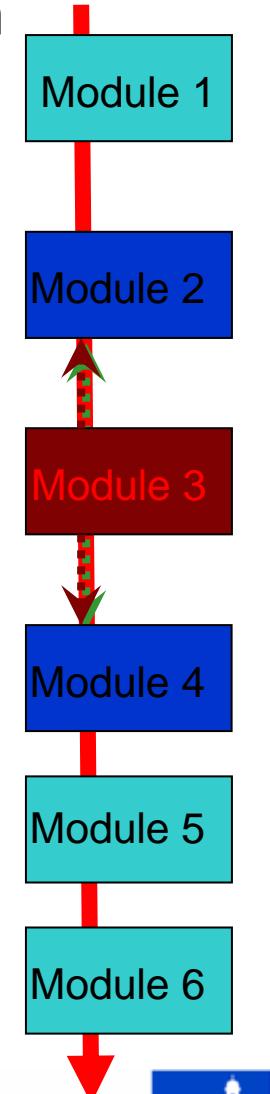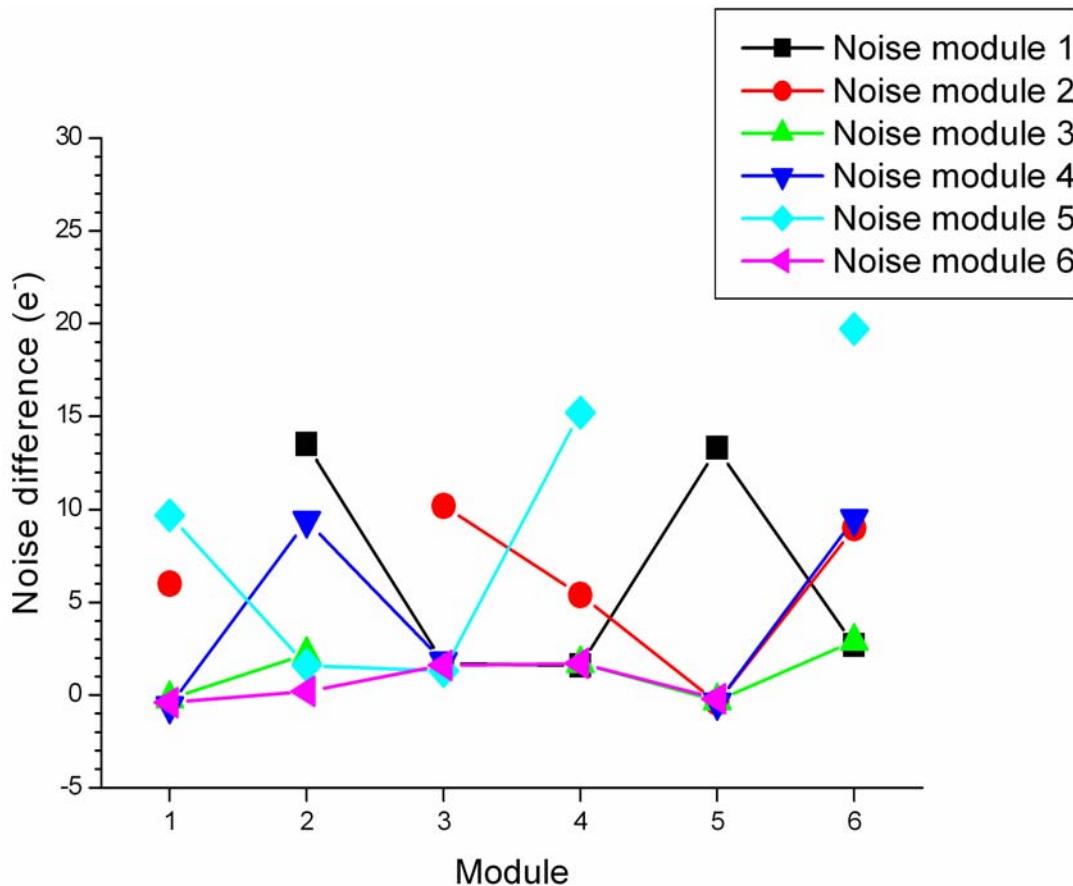- Noise difference [e^-] to normal half-stave operation




- **Little noise pickup**

Noise Pickup Measurements on Dummy Half-Stave

Noise Pickup Measurements

Frequency Dependence

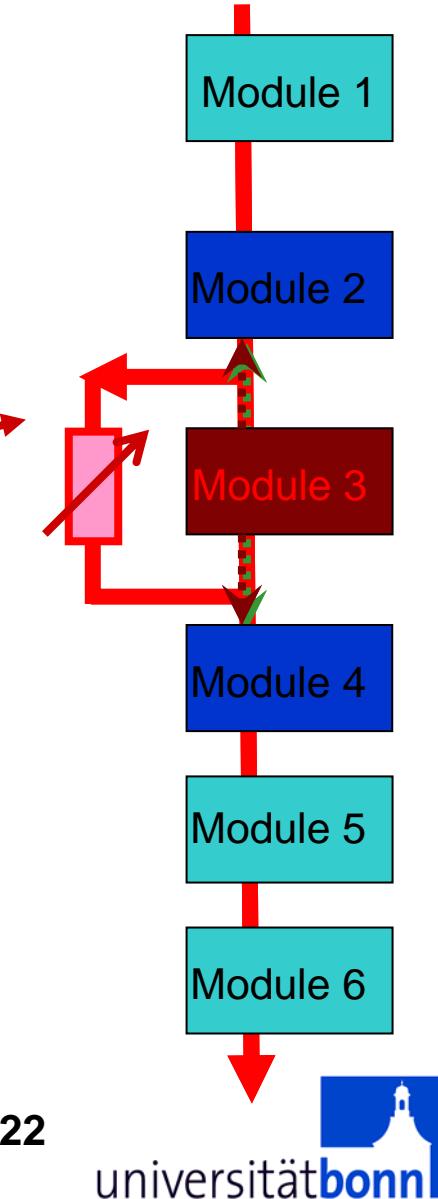
- **Again:**
Do other modules pickup noise through the power lines?
- Noisy module achieved by a **parallel, switchable load** between 300mA and 500mA, frequencies up to 40MHz
- XCK and STROBE to all six modules **at the same time**
- Threshold scan performed on four modules, read-out of two modules at the same time




Noise Pickup Measurements

Frequency Dependence (cont.)

Module parallel
to switchable load

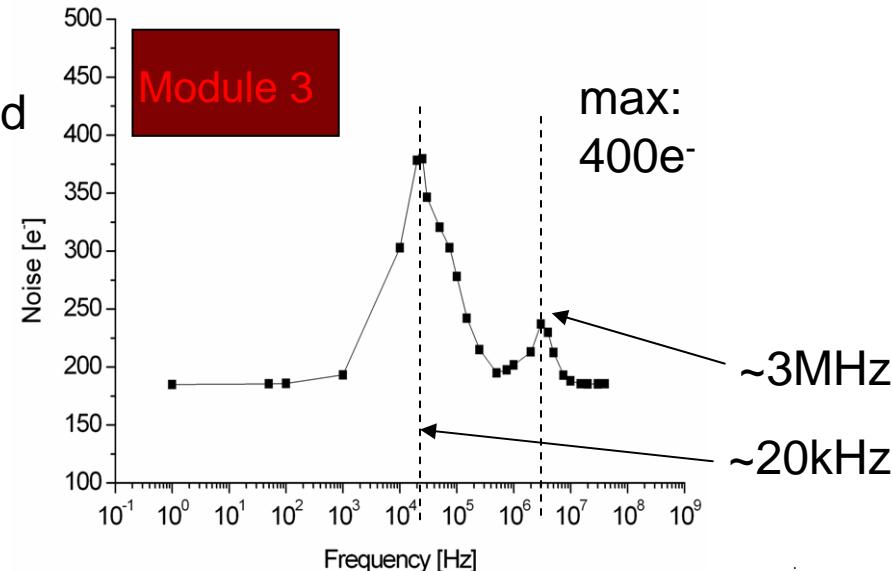

Neighbouring
modules

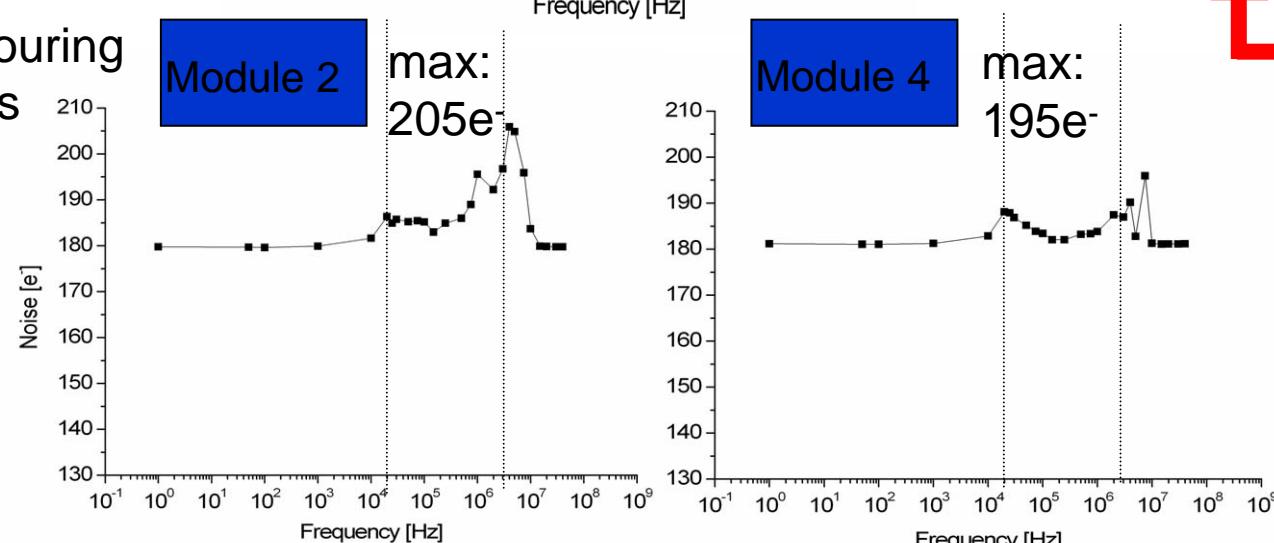

Noise Pickup Measurements on Dummy Half-Stave

Summary

- The implementation with present I3-modules has shown:
 - Serial Powering module/s performance **comparable to Parallel Powering modules**
 - Filtering of a chain of modules sufficient, **hardly noise pickup from noisy modules**
- Serial Powering is a viable and reliable alternative power scheme
 - for the ATLAS pixel detector (upgrade)
 - for pixel detectors, tracking detectors in general

Outlook


- AC-coupled readout → Decoupling via optical readout
- System test with full stave (13 modules)
- Full system design (cables, readout, power supplies)

- Temperature dependence, irradiated regulators on chips/modules
- Regulator for Module Control Chip

- New FE-design 130nm (90nm) technology, specially dedicated and optimized to SP

References

- **D.B. Ta et al.** *Serial Powering: Proof of Principle demonstration of a scheme for the operation of a large pixel detector at the LHC*, Nucl. Instr. & Meth. A557 (2006) 445–459.
- **T. Stockmanns et al.** *Serial powering of pixel modules*. Nucl. Instr. & Meth. A511 (2003) 174–179.
- **T. Stockmanns** *Multi chip module development for the ATLAS pixel detector*. PhD thesis BONN-IR-2004-12 (2004) (in German).
- **D.B. Ta** *Development and demonstration of Serial Powering on ATLAS pixel modules and module ladders (functionality and reliability tests)* diploma thesis BONN-IB-2005-04 (2005) (in German)

 

Backup slides

Concept, realization and characterization of serially
powered pixel modules


28

Alternative Serial Powering Schemes

- Extended Scheme
 - Uses: DOVER 2,7V,
ALINREG 1,6V and
DLINREG 2,0V for FE+MCC

- Basic Scheme
 - Uses: DSHUNT 2,0V and
ALINREG 1,6V, MCC ~2,0V

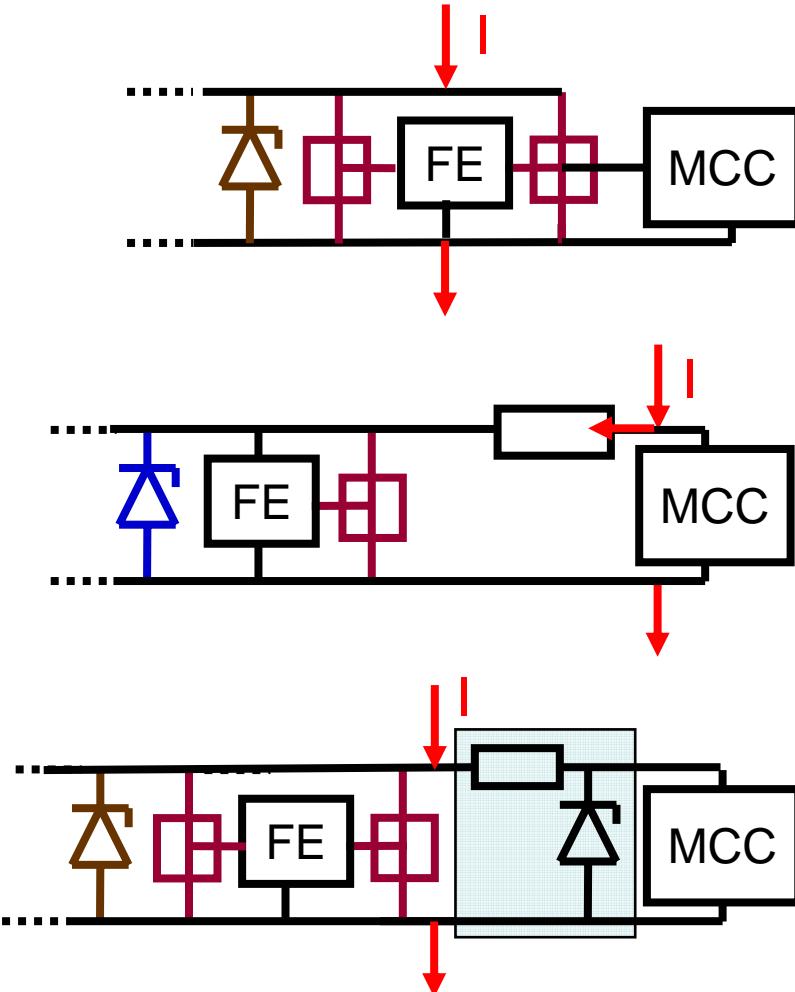
- MCC Extended Scheme
 - Separate Regulator for MCC






- Three I3 Modules with different schemes
 - Noise map:


Basic
(no sensor)

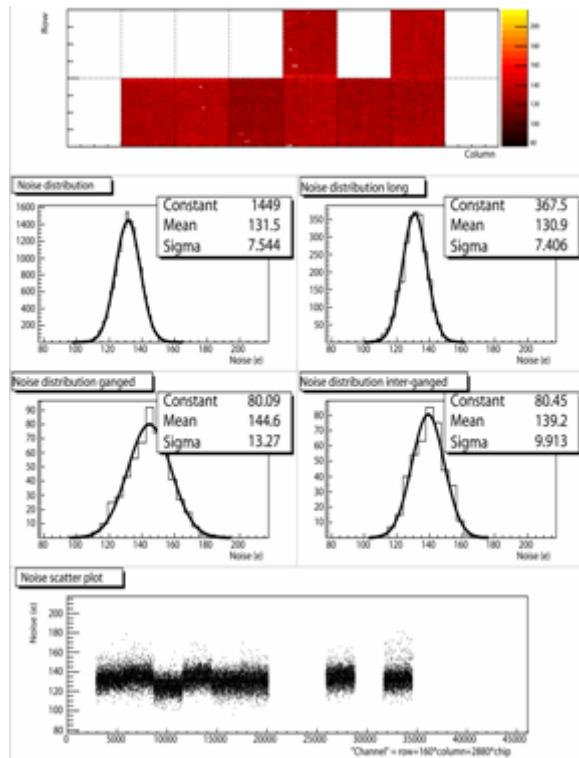

Improved
(no sensor)

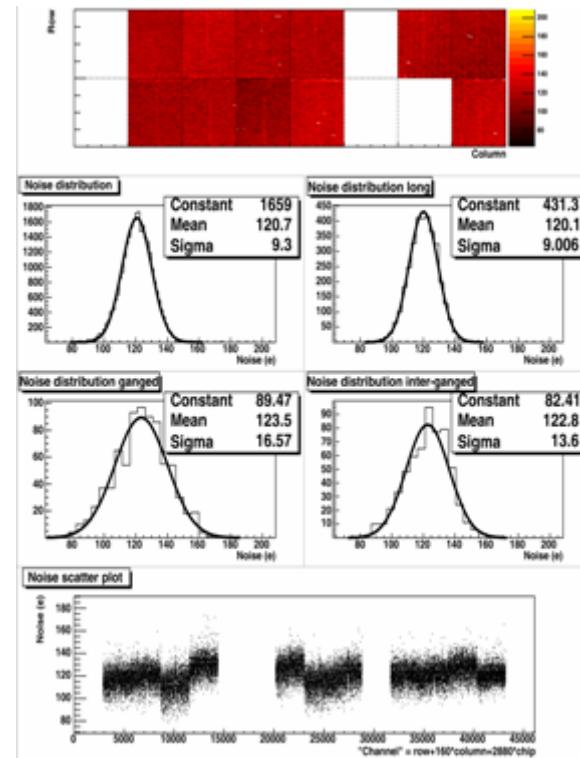

separate MCC-Regulator

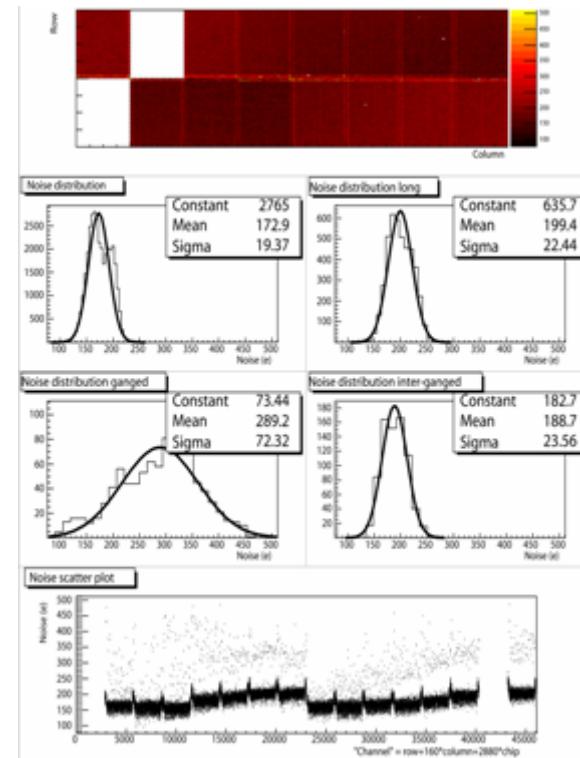

Backup slides





	Basic (no sensor)	Extended (no sensor)	MCC Extended	Parallel Powered Module (510970)
Threshold [e^-]	4143	4132	4194	4189
Dispersion [e^-]	52	51	73	75
Noise [e^-]	134	121	179	196

- No difference between schemes, no difference to PP modules
- Decided to use the improved scheme, simple, flexible and DLinReg can handle extra load



Design of a Serial Powering Flex

- Extra bond pads for regulator pads
- Separate VDDD and VDDA lines
- Filter capacities for every voltage and every chip
- Increased filter capacities
- Minor improvements on all bond pads
- Useable for several schemes



Design of a Serial Powering Flex (cont.)

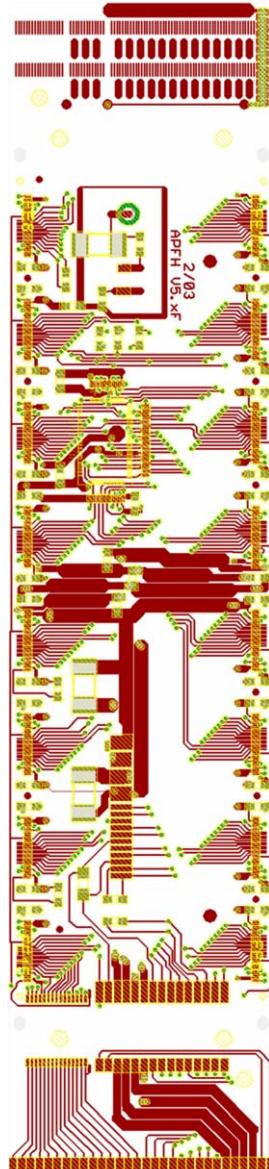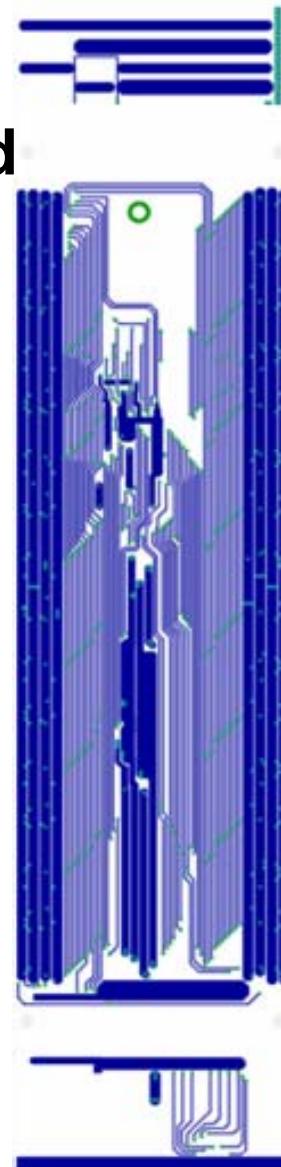**Old**

Backup slides

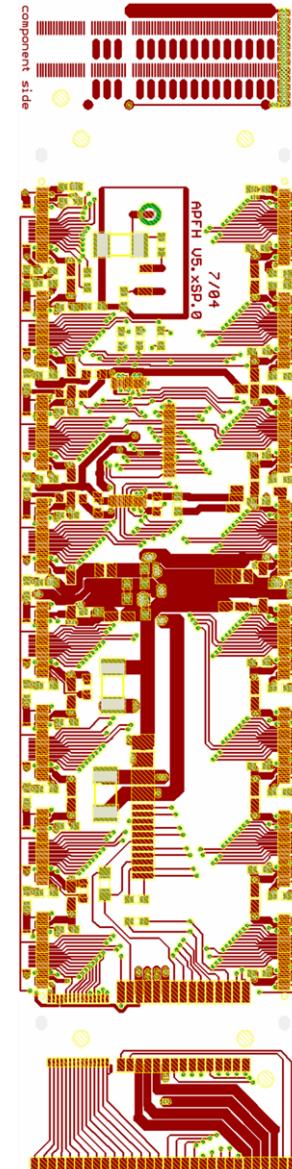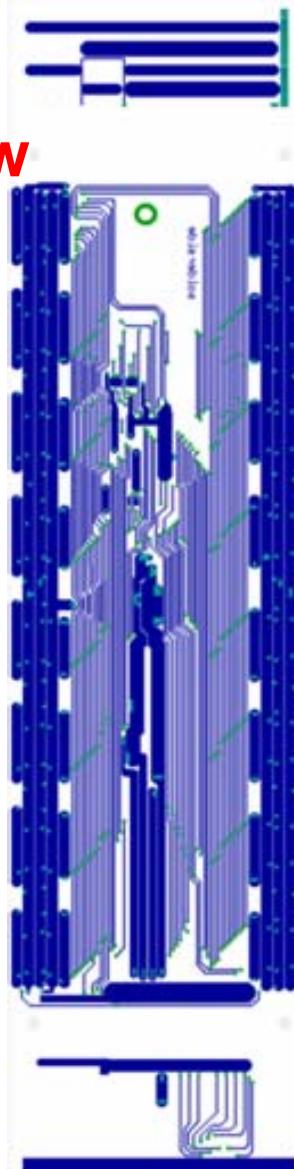**New**

33

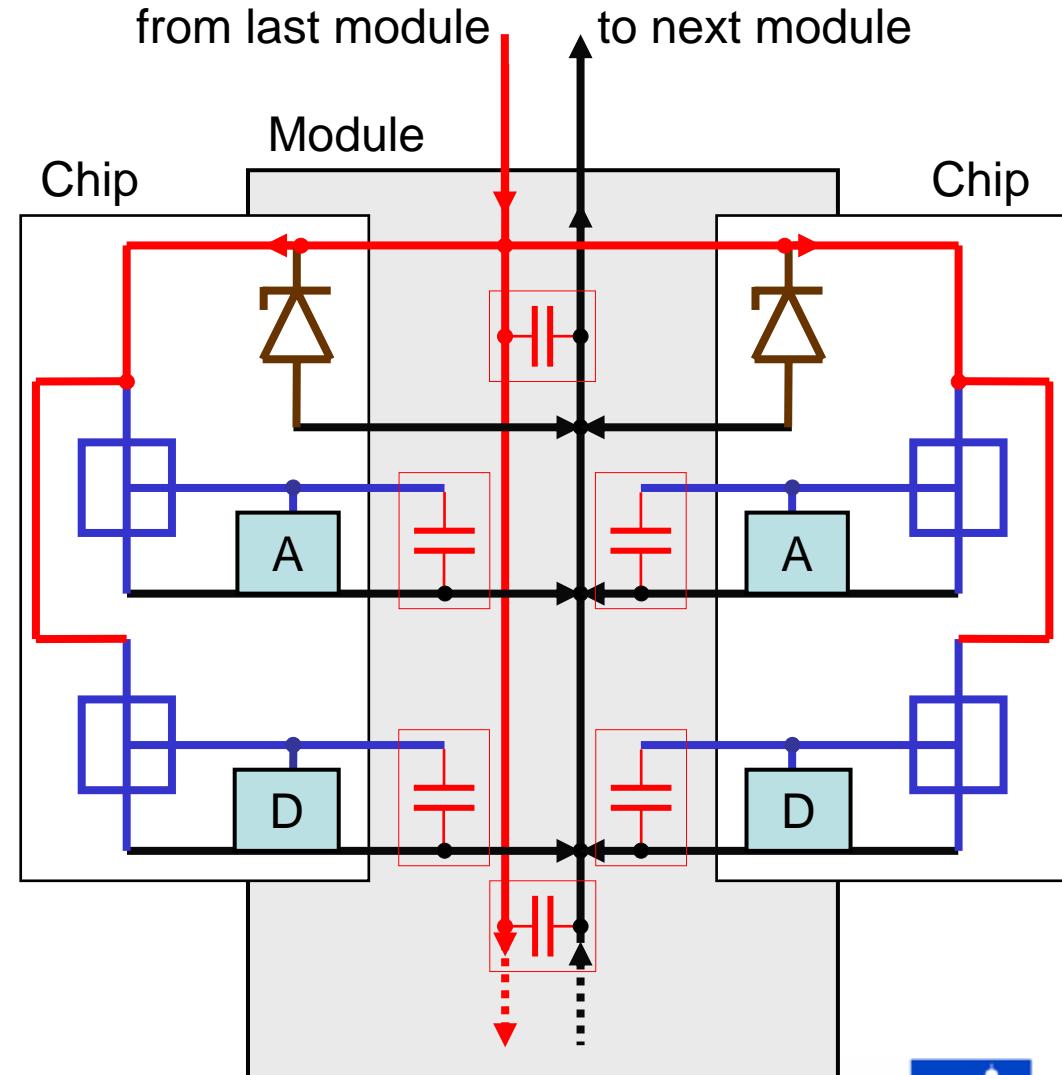
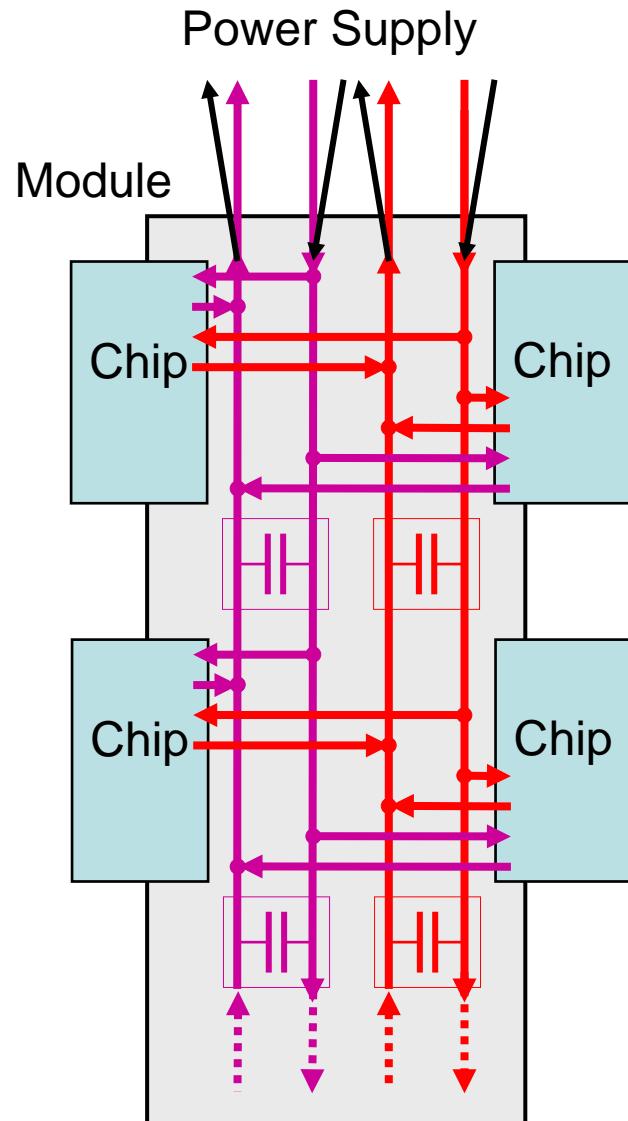


Backup slides

34

Irradiated Regulators

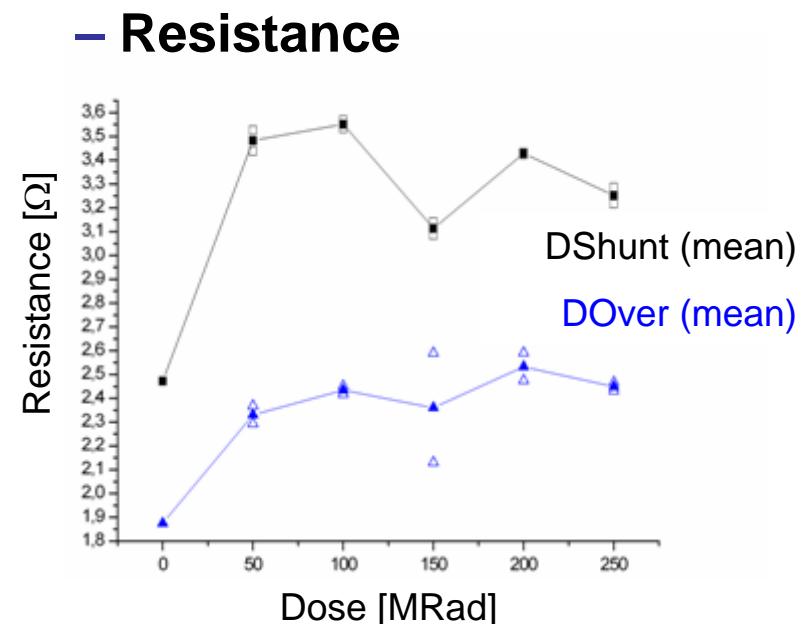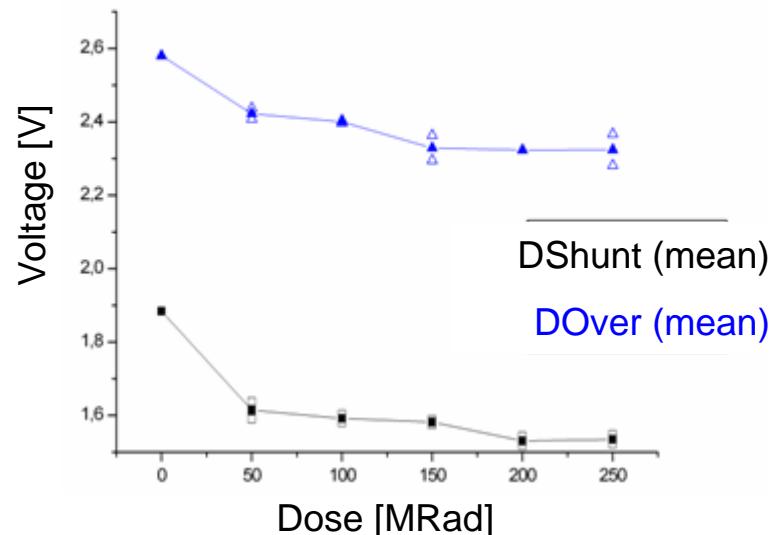
- 2x5 chips passively irradiated at PS with doses from **50MRad to 250MRad**
- Chips & **regulators are working**, even with dose ~ 5 x ATLAS lifetime
 - Threshold voltage
 - Resistance






- Output voltages

ALinReg:

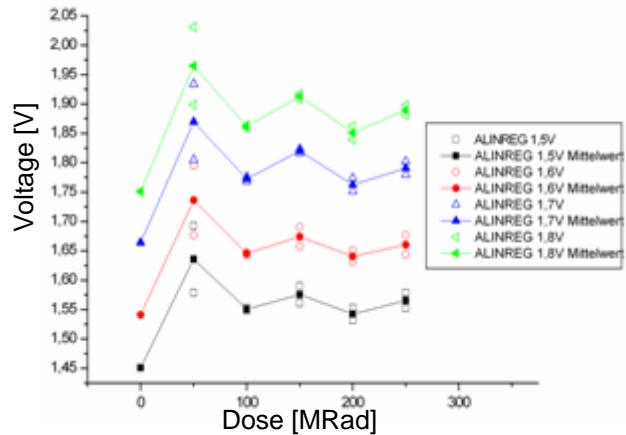


DLinReg:

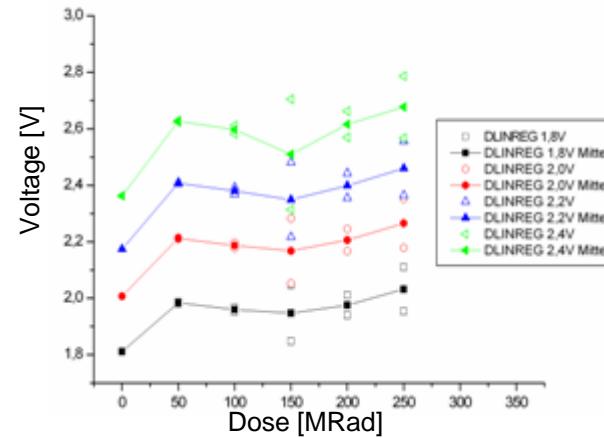


- Voltage dropout

ALinReg:

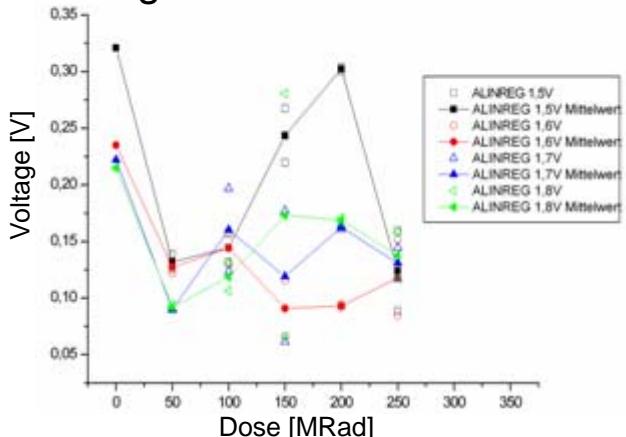

DLinReg:

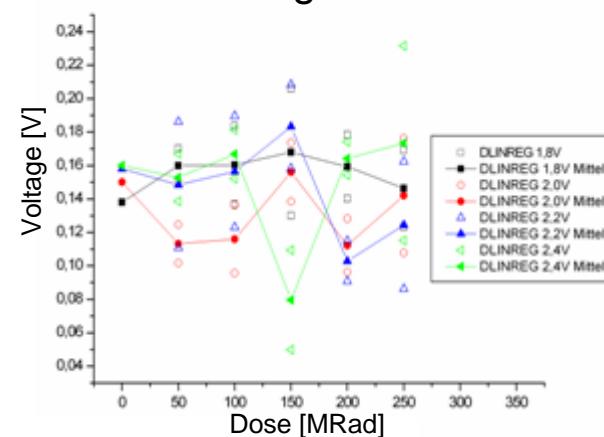


Backup slides





- Dependence on input voltage (slope)

ALinReg:

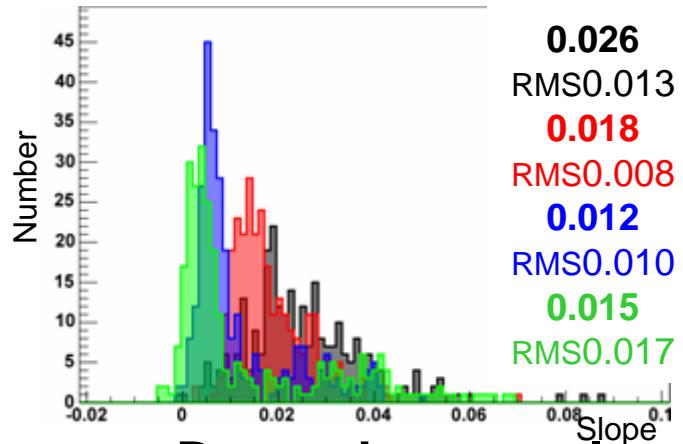


DLinReg

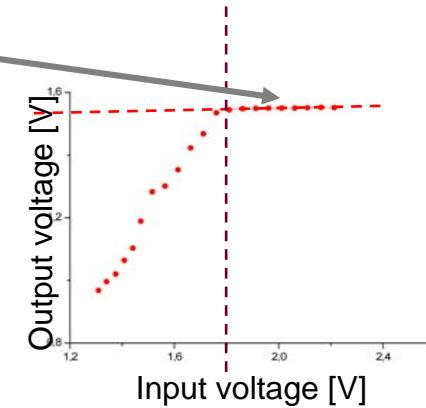
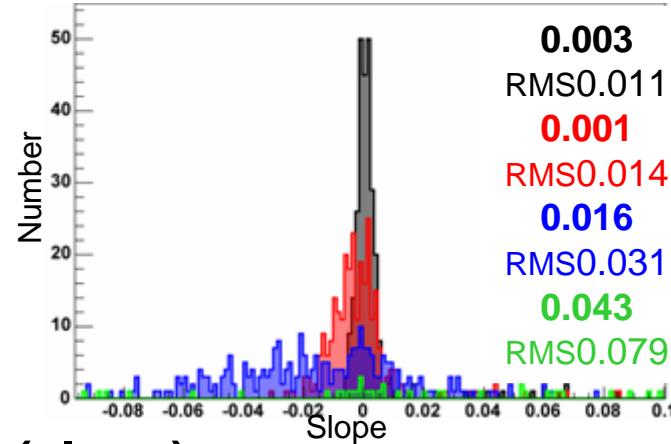


- Dependence on load (slope)

ALinReg:

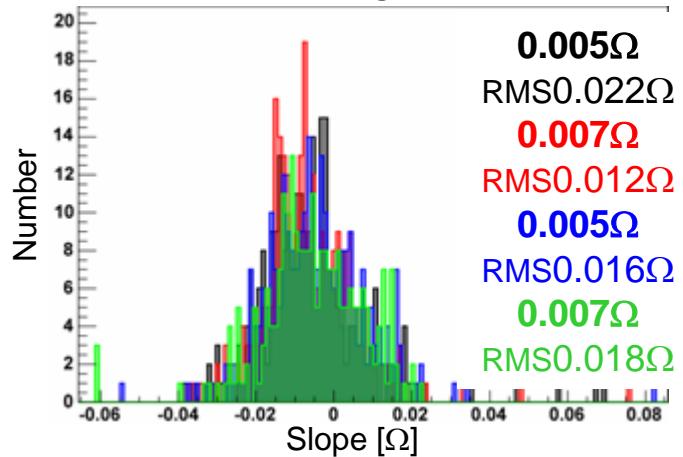

DLinReg

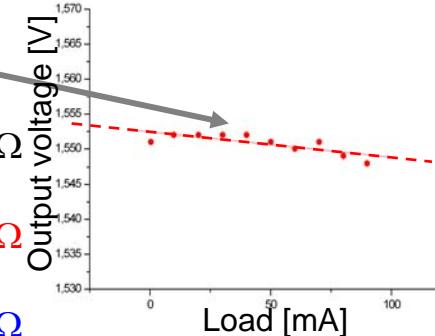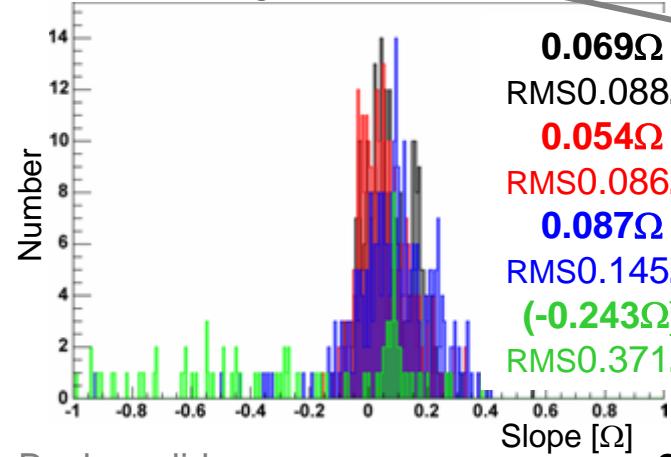


Backup slides


37

Noise Pickup Measurements

Frequency Dependence (cont.)

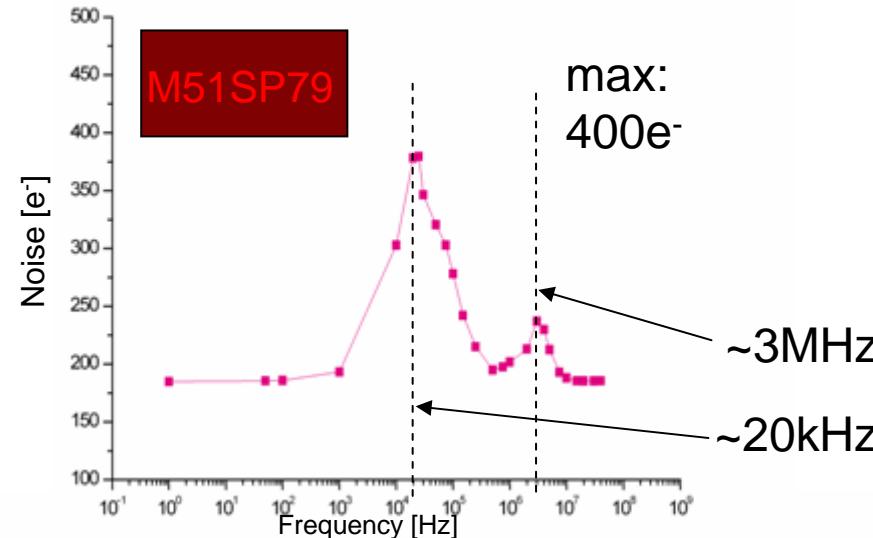
M51SP11

 max:
 205 e⁻

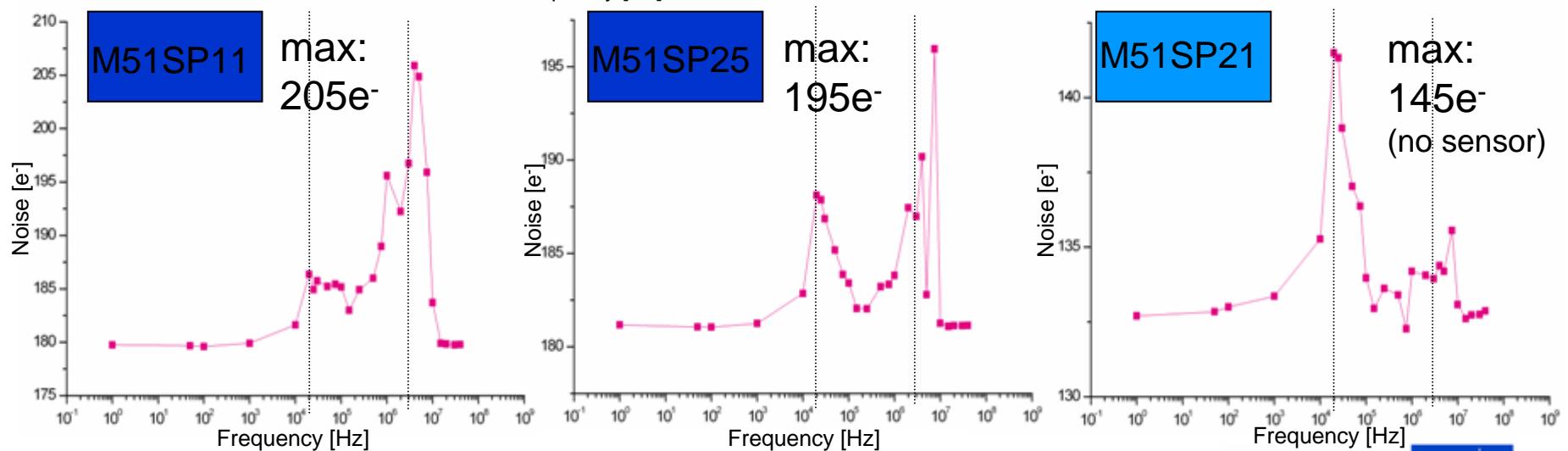 Noise [e⁻]

M51SP25


 max:
 195 e⁻
M51SP21

 max:
 145 e⁻
 (no sensor)

Backup slides

38

AC Coupling

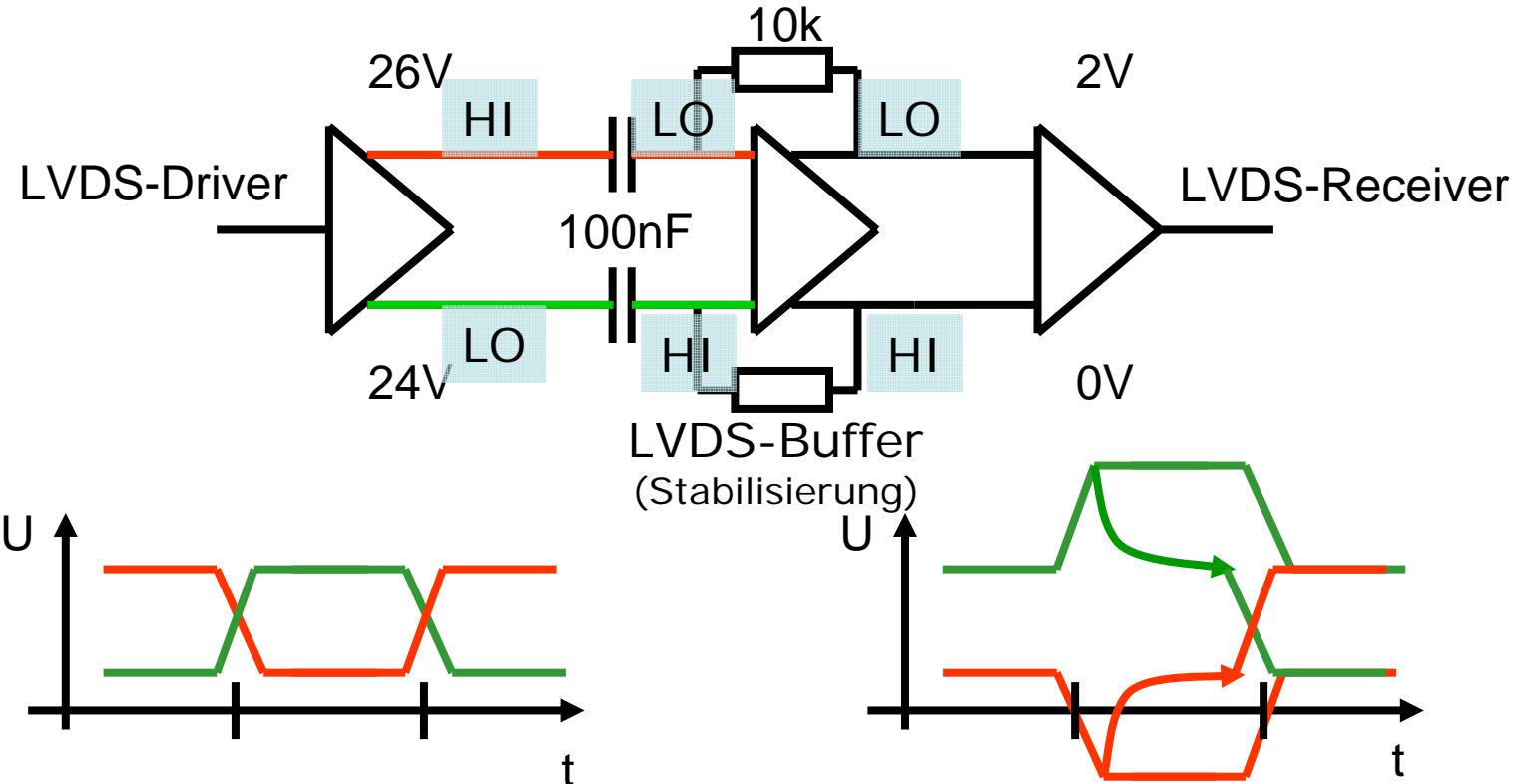

AC-Coupling Final Implementation

