

LP/HP Diplexer with Gaussian Response

20/09/07

The design for a LP/HP diplexer requires

1. LP transient response gives $\sim 2\text{ns}$ flat top when generator pulse is 5ns rectangular.
2. LP 3dB cutoff frequency at 170MHz .
3. LP Attenuation at $600\text{MHz} \sim 30\text{dB}$.
4. Constant impedance 50ohm towards the generator.

6^{th} order Gaussian LP is chosen, which satisfies the attenuation and flat top transient requirements. 6^{th} order LP ends with a capacitor, which could be used to incorporate capacitor in the following amplifier. HP channel uses Gaussian 5^{th} order. The LP and HP have the same cutoff frequency 170MHz . Constant impedance is achieved along the whole frequency range.

The design is realized with ladder circuits. Normalized element values are obtained from [1]. To achieve constant diplexer impedance, design of individual LP/HP circuits must use infinite source resistance. Figs. 1-3 show the design of exact values and its time/frequency domain responses. Figs. 4-6 show the practical element values and the corresponding time/frequency domain responses. The results show that the practical values satisfy the design requirements very well.

[1] Anatol I. Zverev, 'Handbook of Filter Synthesis', 2005 by John Wiley & Sons, Inc..

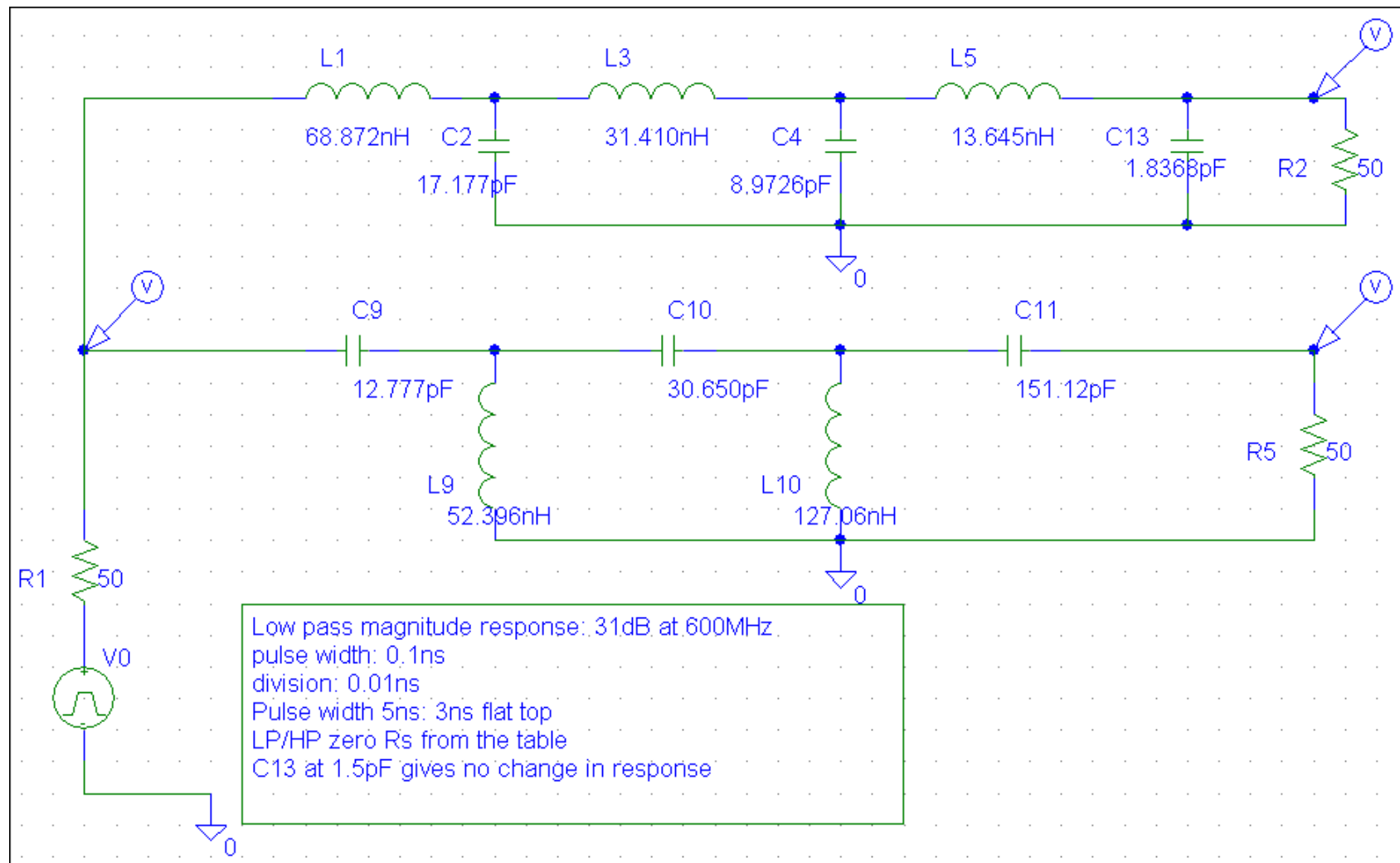


Fig. 1

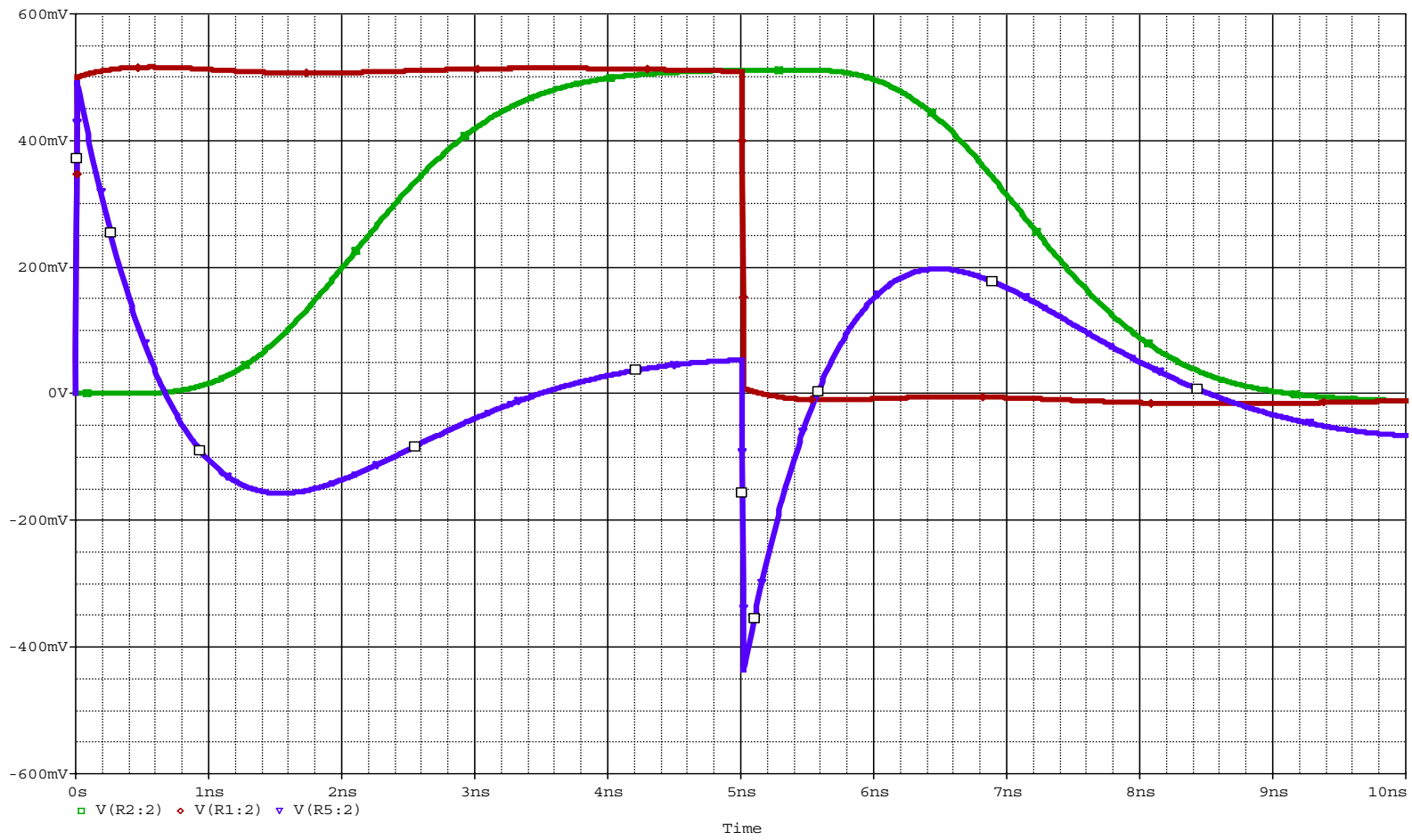


Fig. 2.
 Horizontal: one division = 1ns. Vertical: one division = 200mV

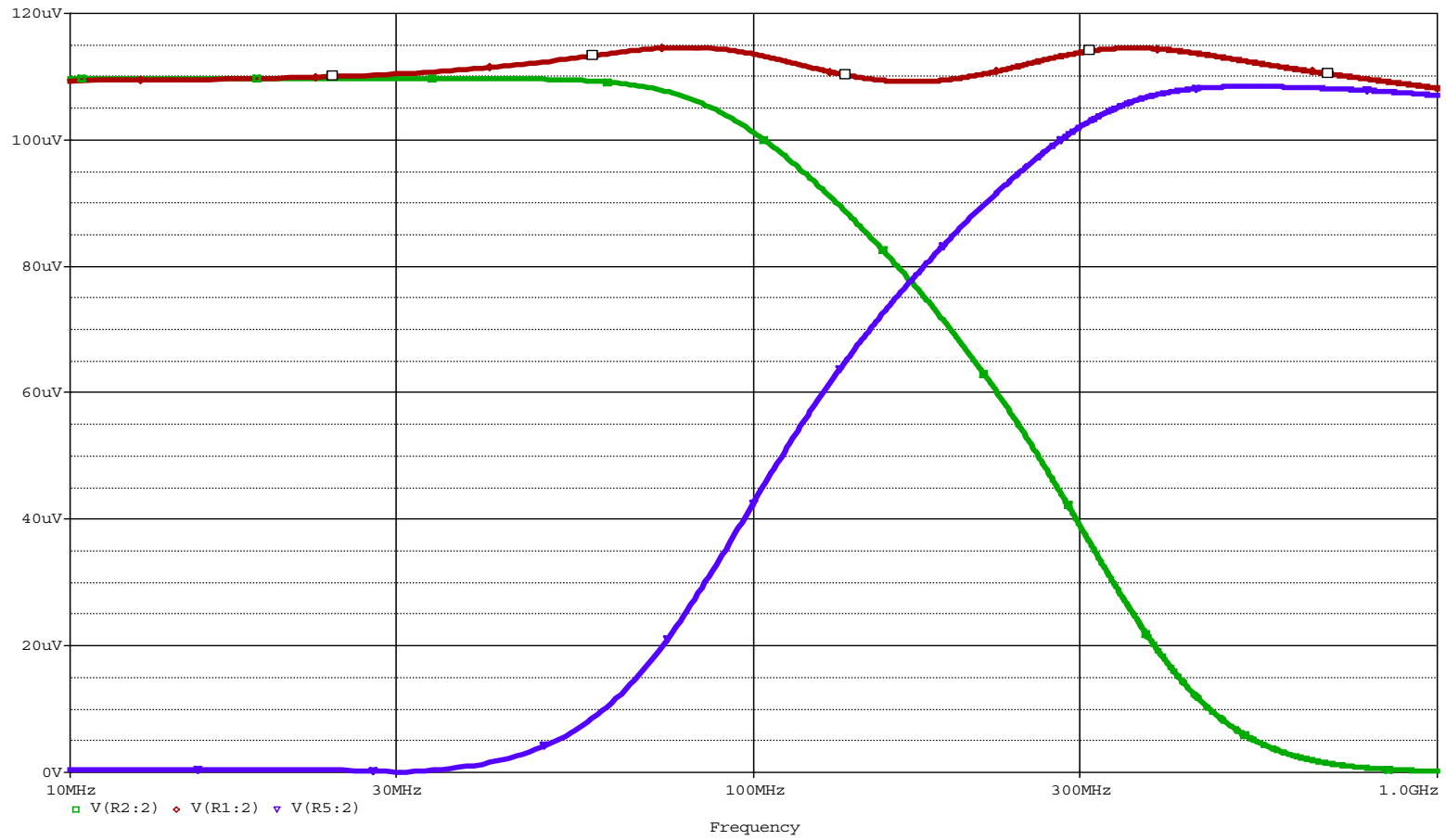


Fig. 3
Horizontal: log, (10-100-1000)MHz. Vertical: arbitrary units

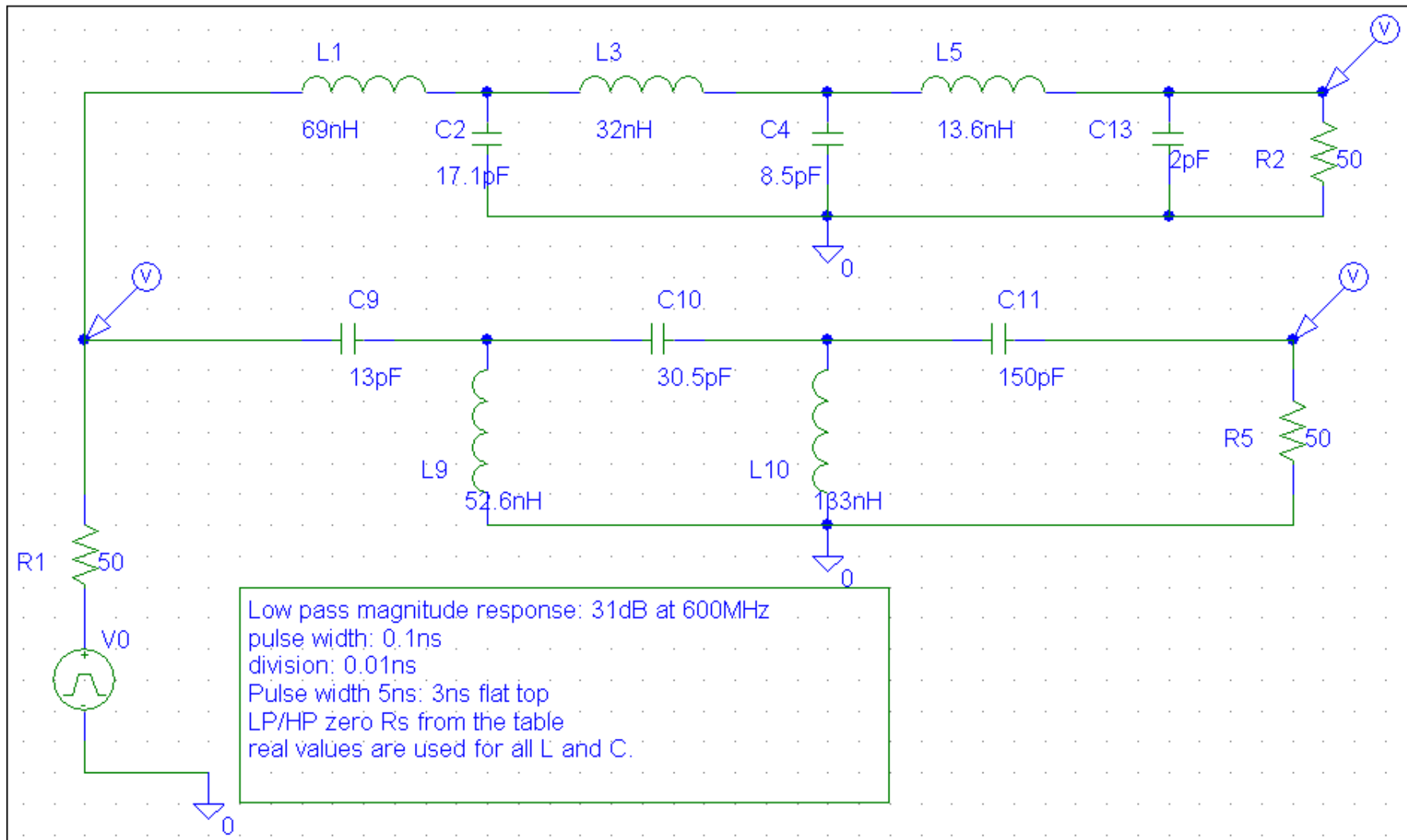


Fig. 4

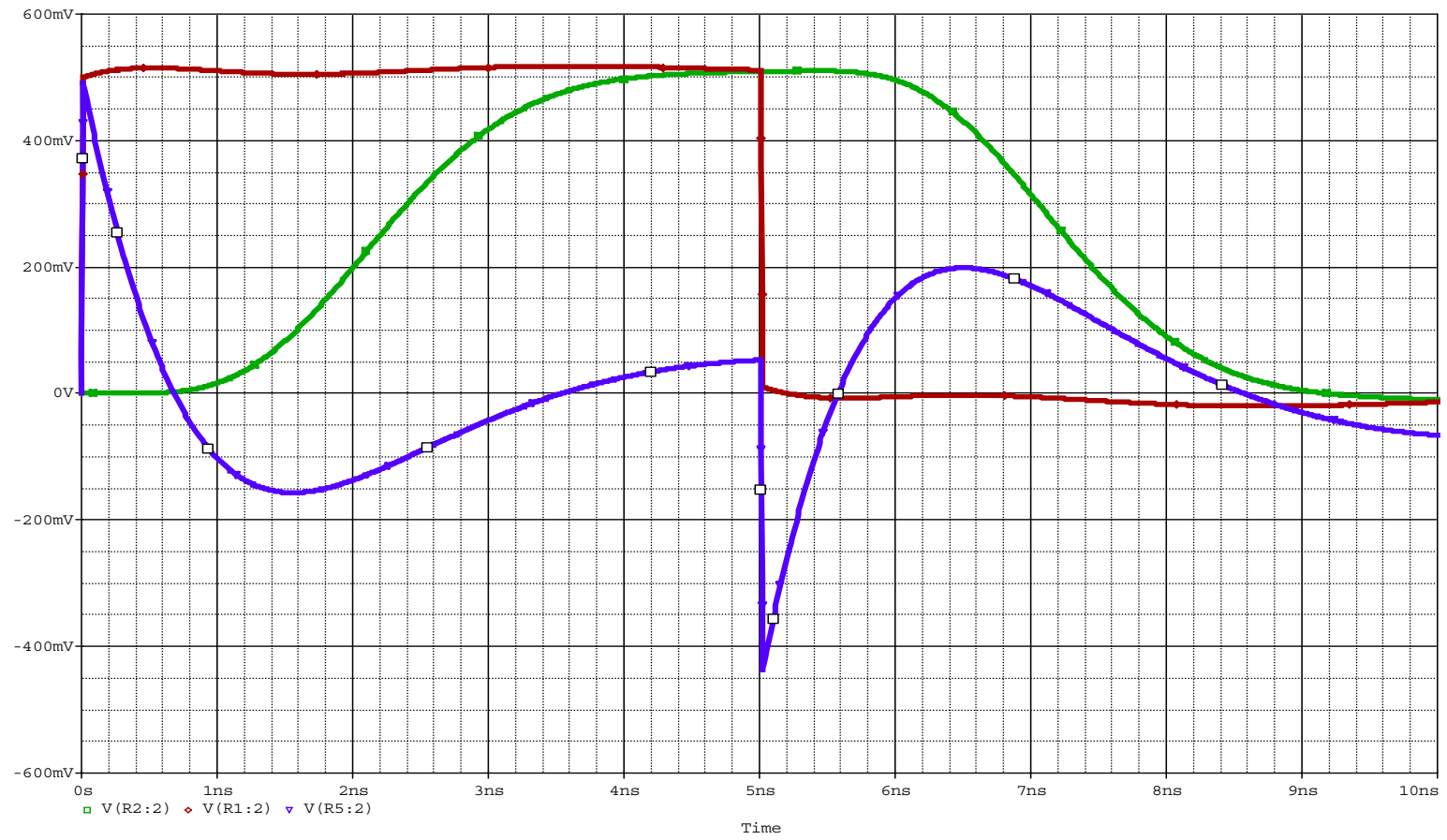


Fig. 5
 Horizontal: one division = 1ns. Vertical: one division = 200mV

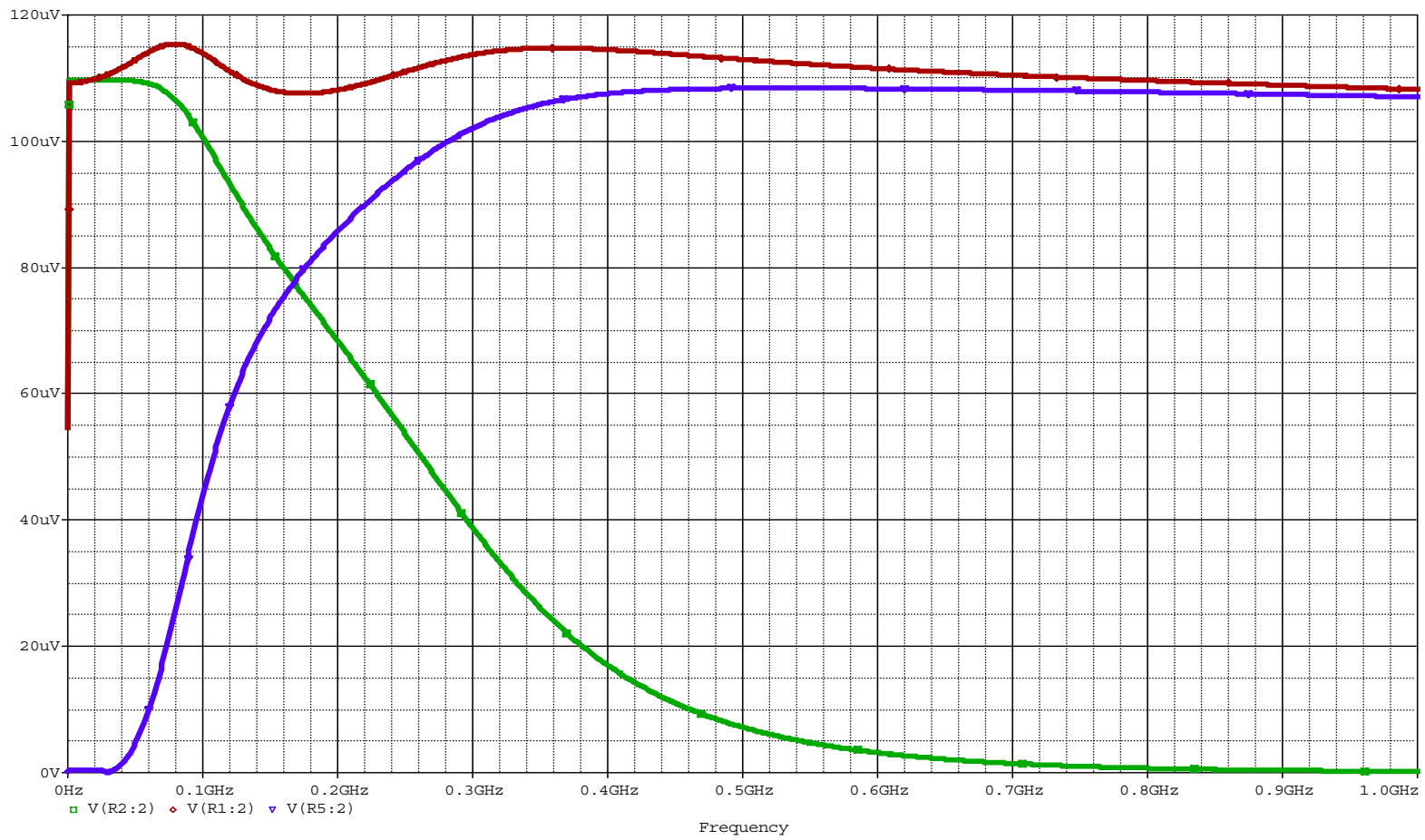


Fig. 6
Horizontal: linear, (0-1000)MHz. Vertical: arbitrary units