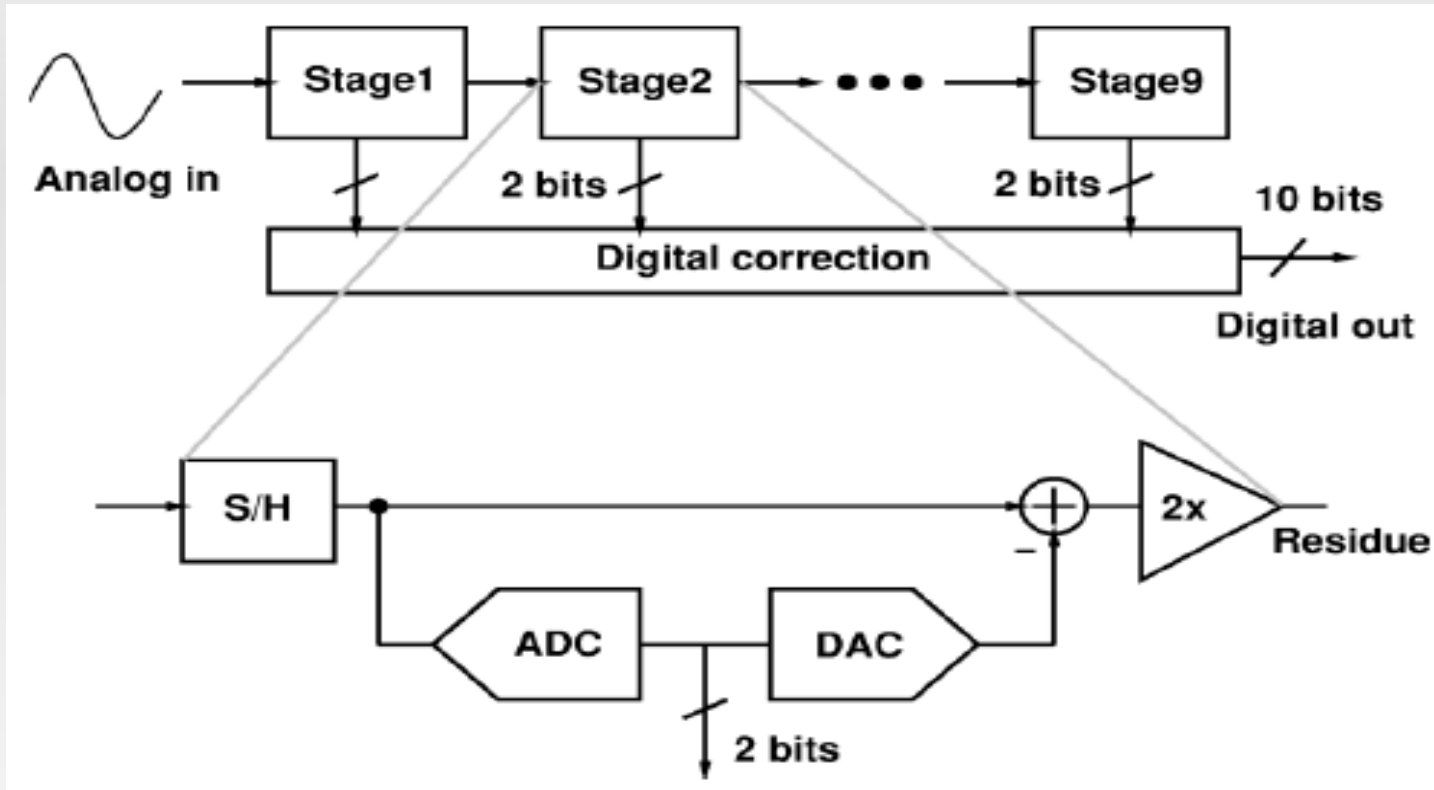


First test of prototype ADC for LumiCal detector

M. Idzik, K. Swientek, S. Kulis

AGH University of Science and Technology
Krakow, Poland


Pipeline ADC concept



Last stage is simplified

- 9 stages for 10 bit
- A stage produces 2 bits and multiplies signal by 2
- Digital correction relaxes comparator requirements


One 1.5bit stage

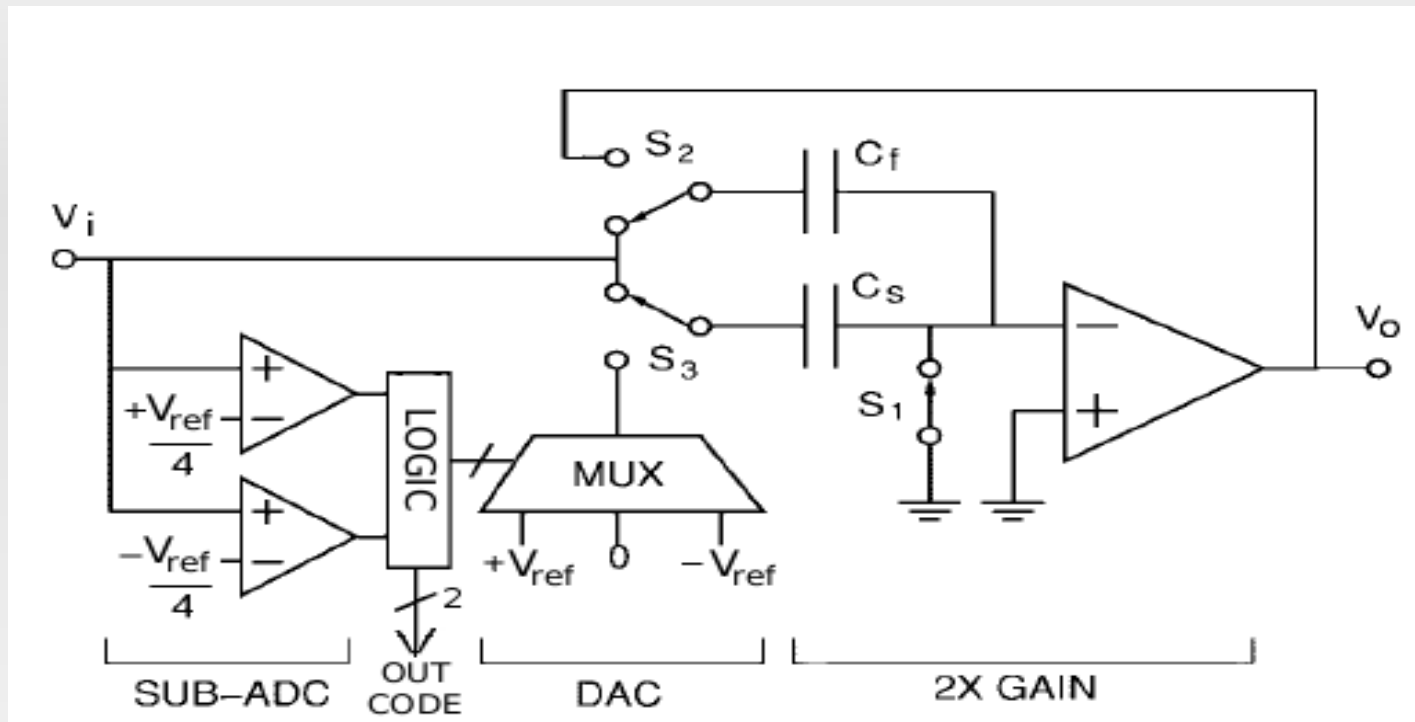

3 different output values coded on 2 bits:
00, 01, 10
so it is called 1.5 bit stage

- Switch capacitor circuit – needs clock
- Two phases:
 - 1) charging capacitors
 - 2) multiplication by 2 and subtraction

Fully differential implementation

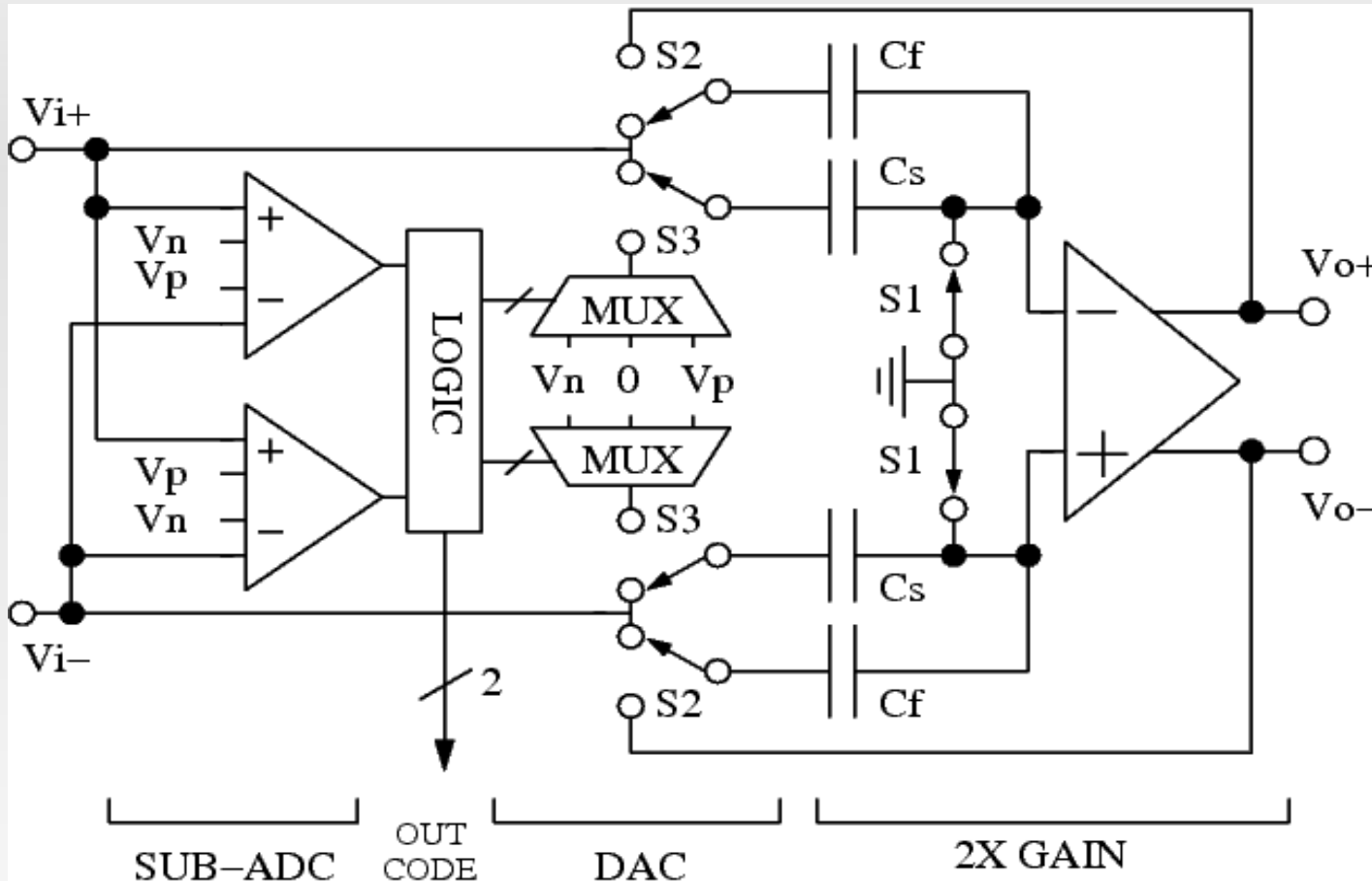

Doubled elements:


- capacitors
- switches
- MUXes

Differential elements:

- compar.
- amplifier


- Differential signal is not sensitive to disturbances from e.g. digital elements

First simple prototype

 

- submitted in June
- only 8 stages
- no digital correction in chip
- external biasing
- size 1.15x1.11 mm
- differential input

Printed Circuit Board

 


Test Setup




... during measurement

Very preliminary results

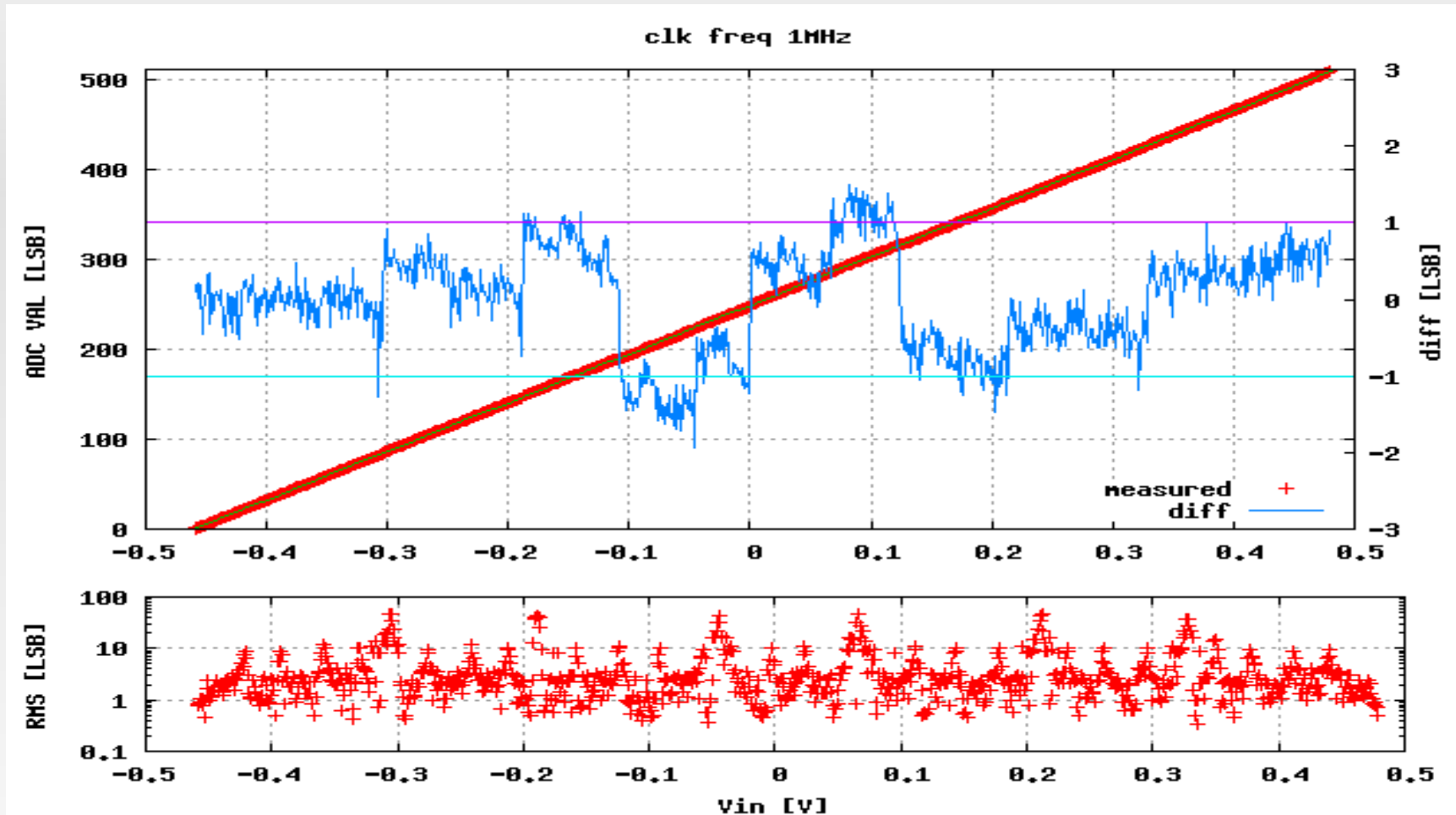

- Static (DC) meas.
- Not proper ADC readout
- Fluctuations
- Average as a ADC out

Very preliminary results 2

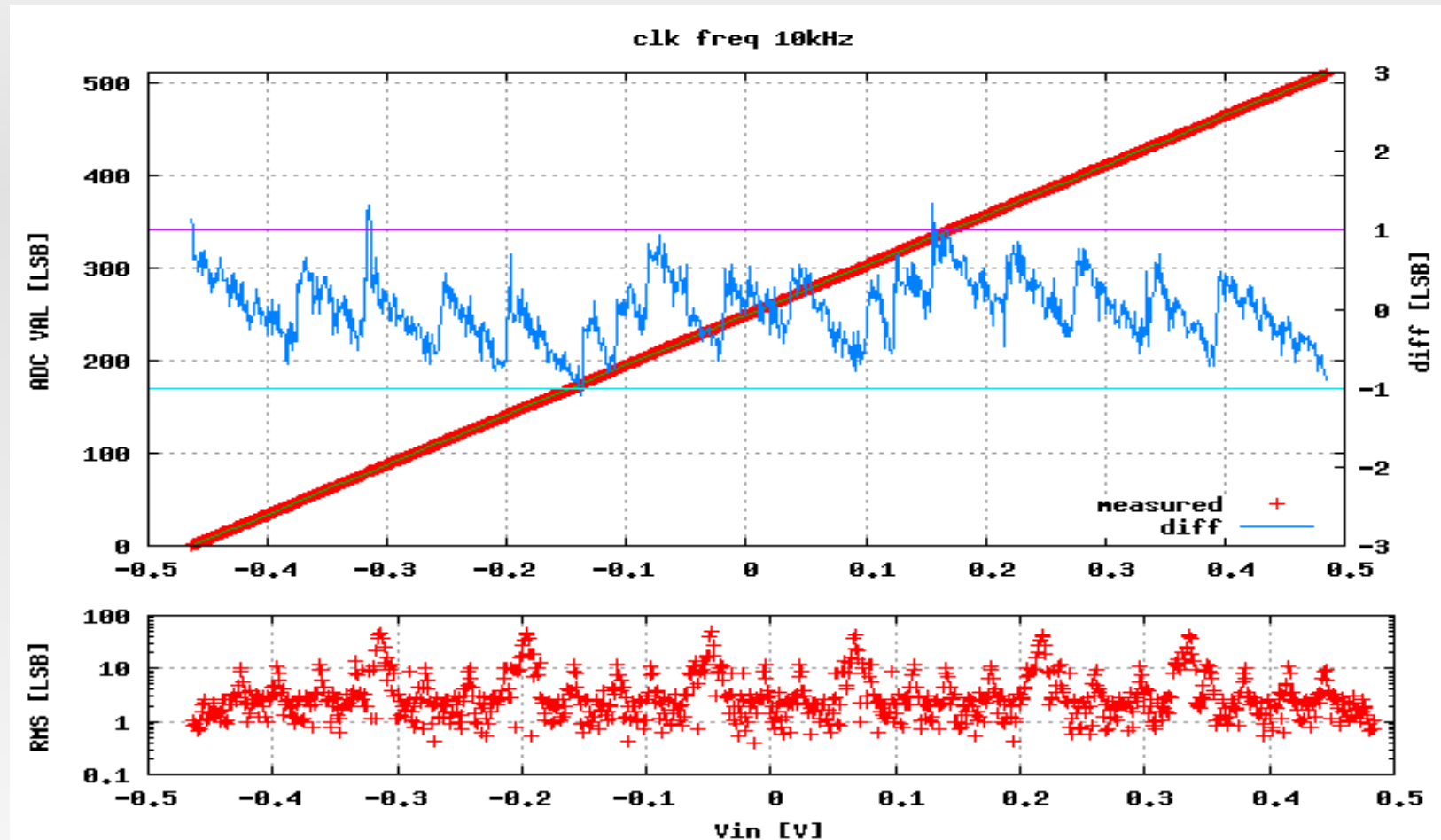

- Other clk freq — other result ?!
- Timing problems but looks promising

Conclusions

- Very preliminary ADC measurement
- We have only look on static behaviour
- Results look promising but ...
- We need
 - improve DC test setup
 - make dynamic tests
 - measure ADC parameters