



First measurements of LumiCal front-end prototypes

Marek Idzik, Szymon Kulis

AGH Kraków



Outline

- ❑ Introduction
- ❑ Front-end design & simulations
- ❑ First measurements
- ❑ Summary



Challenges of LumiCal front-end


Large C_{det} range 10-100 pF

Test mode S/N ~ 10 for MIP

Charge sensitive amplifier

$Q_{max} \sim 10$ pC

$C_f \sim 10$ pF

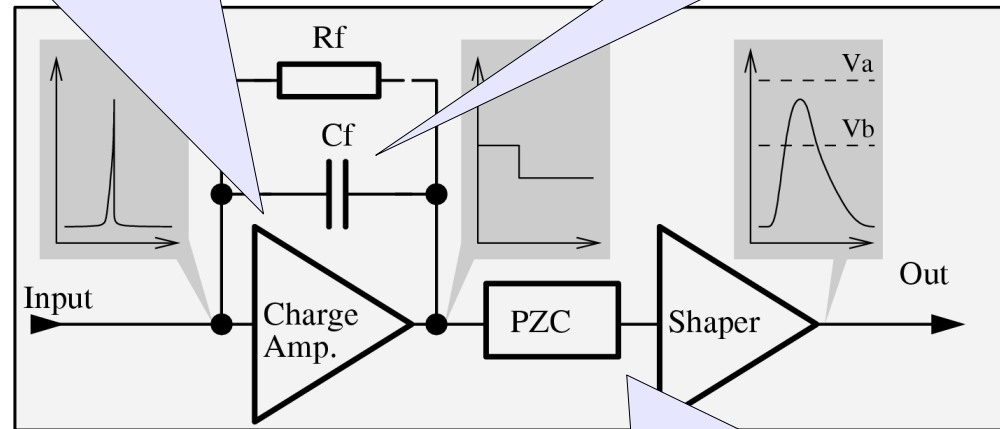

Test & Physics mode

Variable gain


$\Delta t \approx 300$ ns, high occupancy

PZC + Shaper $T_{peak} \sim 60$ ns




LumiCal readout architecture

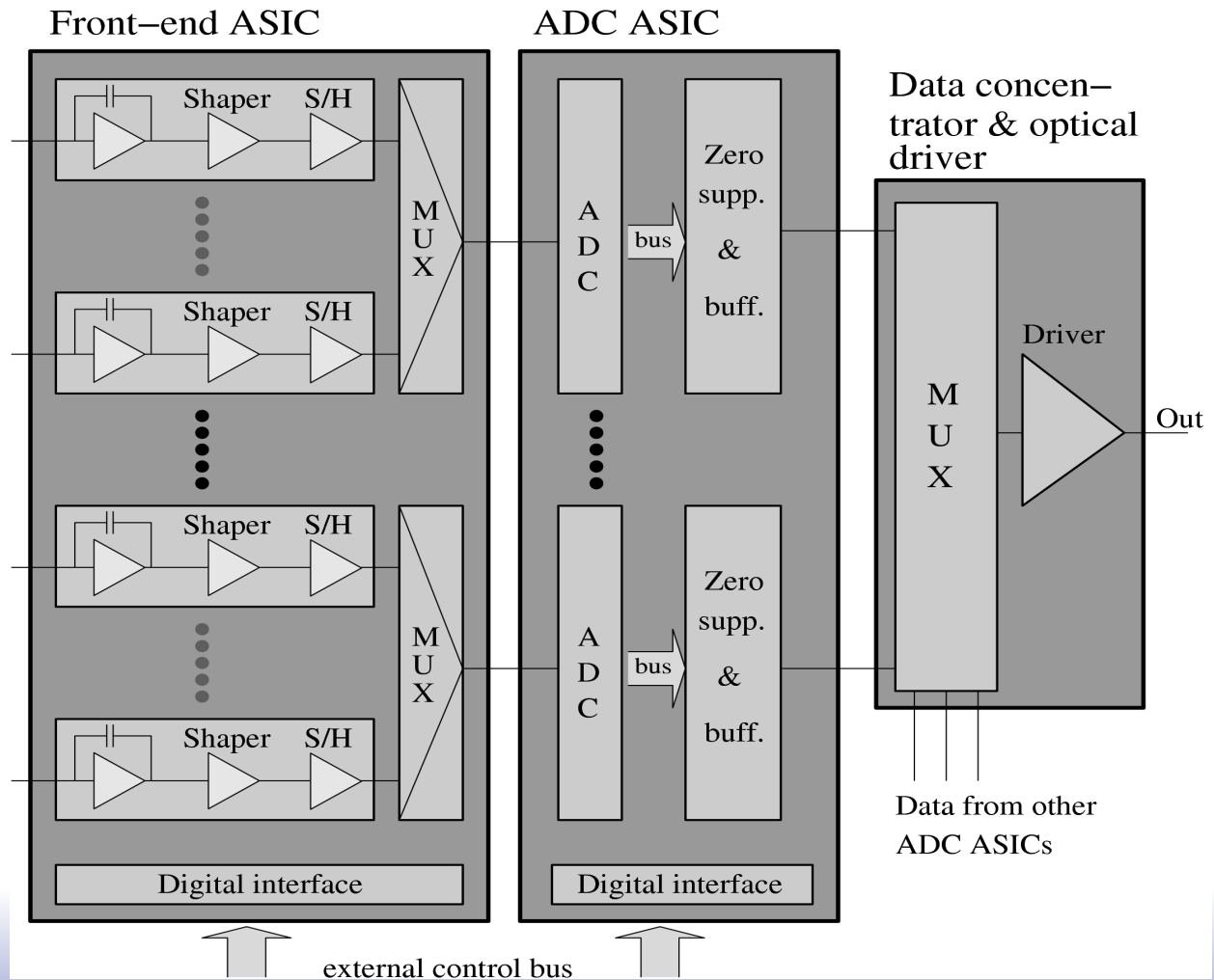- Front-end ASIC will contain 32-64 channels
- An ADC will serve ~8(?) front-end channels
- First prototypes in AMS 0.35 μm






Front-end electronics architecture

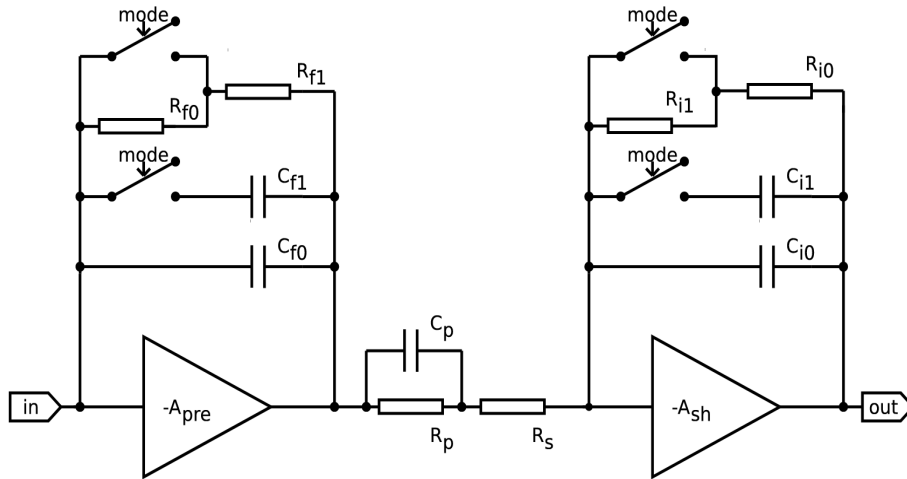

- Preamplifier: $I_{pre} \sim 2.5\text{mA}$, PMOS input, $C_f \sim 10\text{pF}$ (physics), $C_f \sim 0.5\text{pF}$ (test)
- Shaper: 1st order, $T_{peak} \sim 60\text{ns}$, variable gain, $I_{sh} \sim 0.5\text{mA}$


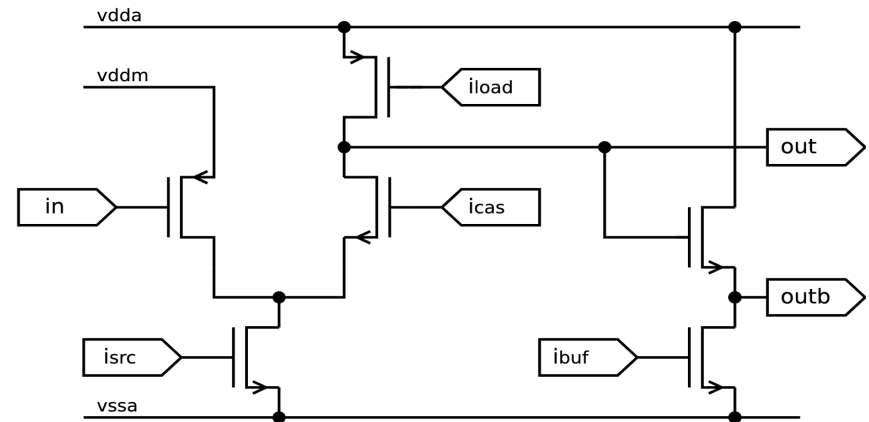
► Both Preamplifier and Shaper designed as folded cascode plus source follower






Front-end simulations

  ► Front-end response in test (mode0) and physics (mode1) mode for different C_{det}




 ► Output amplitude versus injected charge in physics mode










 
Alternative front-end Switched-Reset configuration



Switched-Reset configuration

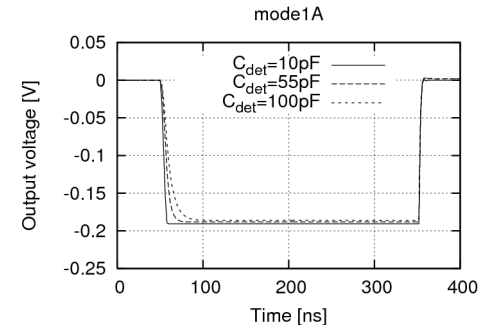 

 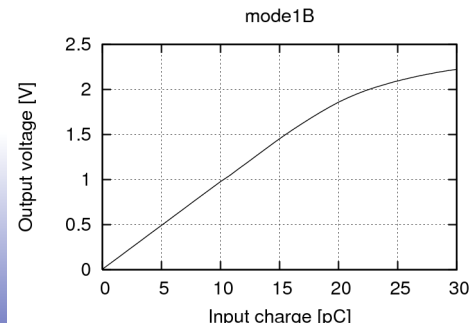  Response in test (mode0) and physics (mode1) mode




► Output amplitude versus Q_{in} for different gain setting



Layout of LumiCal front-end ASIC


 
Prototype ASIC containing 12 channels submitted in
june 2007



Pad Pitch 100 μm


First measurements

  - ❑ 40 ASICs received
- ❑ PCB designed & produced
- ❑ Setup in progress
- ❑ Tests with generator and external capacitance started



Pulse shape


RF (low gain)

 

Preamp+PZC & CR-RC


Preamp with CfRf

RF HIGH GAIN

 

Pulse shape


RF (low gain)

 

Preamp+PZC & CR-RC


Preamp with Cf-MOSf

MOS HIGH GAIN

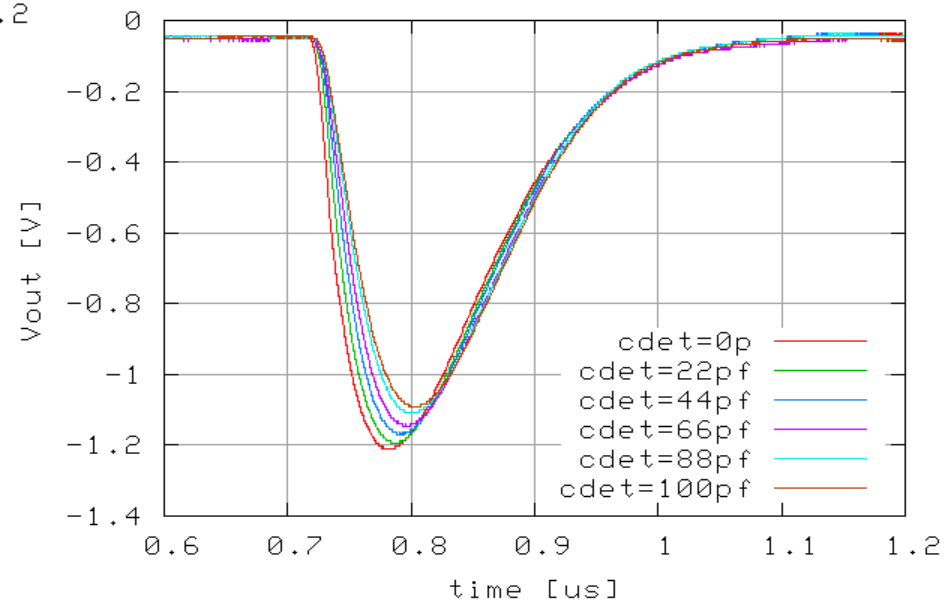

Amplitude vs frequency


Rf (low gain)

 

Preamp+PZC & CR-RC


Preamp with CfRf

Rf (high gain)

 


Amplitude vs frequency

MOS (low gain)

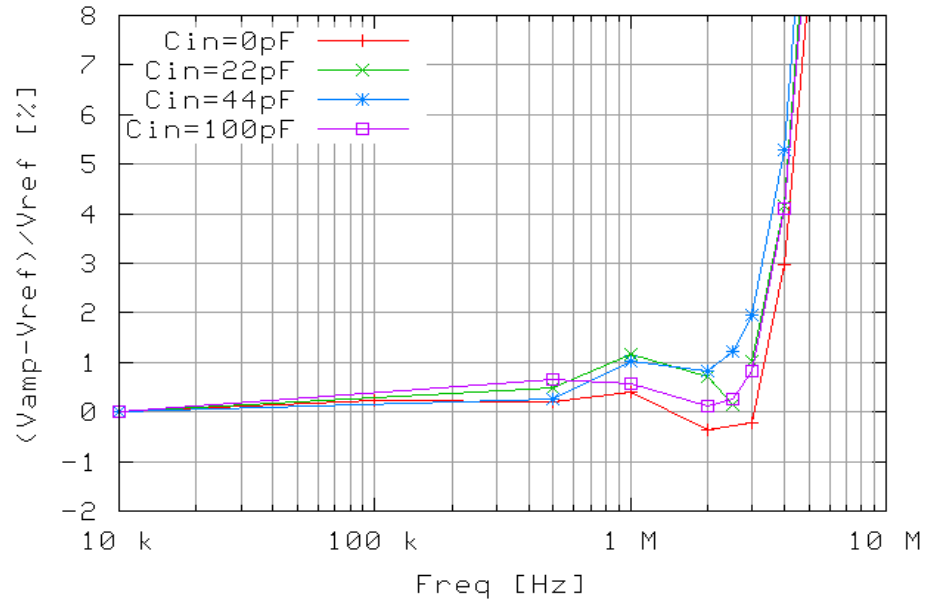


Preamp+PZC & CR-RC
Preamp with Cf-MOSf

MOS (high gain)

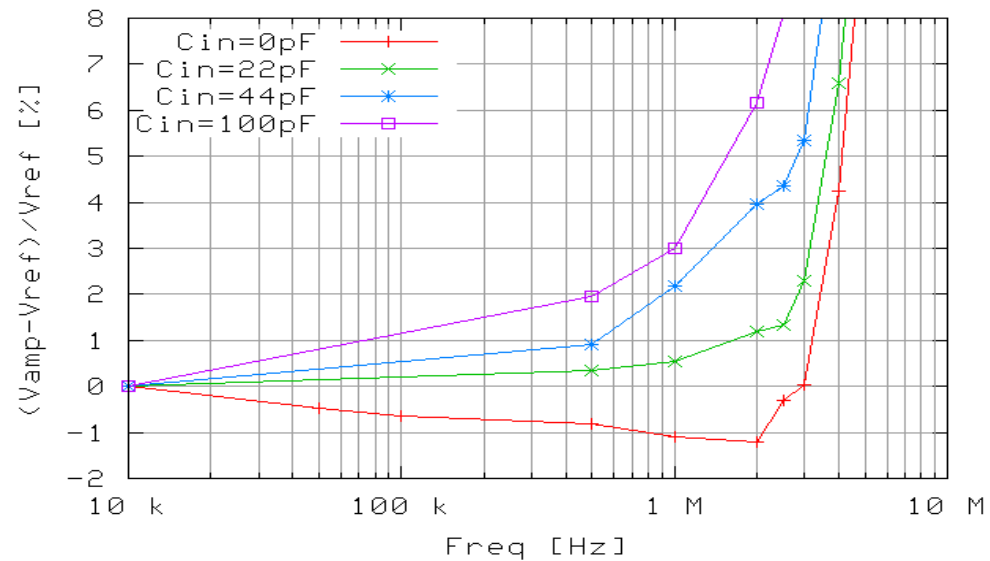


Amplitude vs Qin

Rf (low gain)

 

MOS (low gain)

 


Summary

- ❑ Measurements just started, quantitative results not yet available. 1-2 months needed to complete tests.
- ❑ Some important issues (noise!) not yet studied
- ❑ Discussion and decisions about future directions (i.e. dynamic threshold ?) needed



ADC architecture

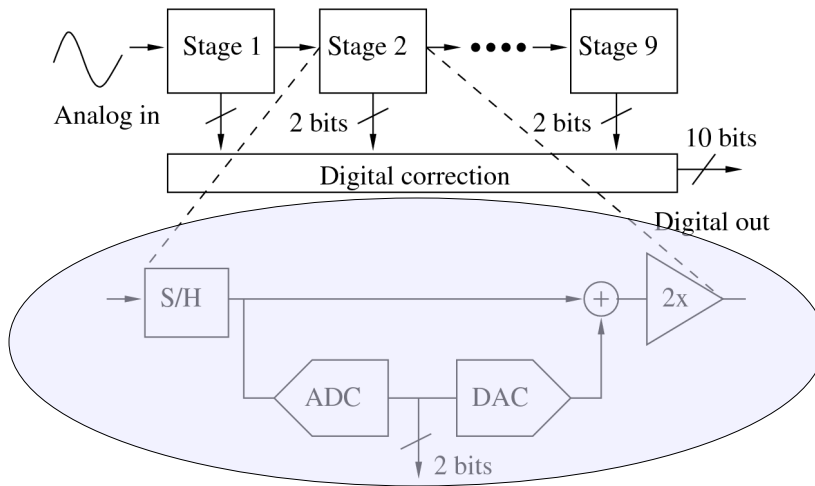


Pipeline advantages

- ❑ 10 bit pipeline ADC
- ❑ 1.5 bit per stage
- ❑ Fully differential architecture


- ▶ High throughput
- ▶ Robustness
- ▶ Power efficient
- ▶ Reasonable area



1.5 bit stage architecture

 


Dynamic latch comparators

 



Layout of ADC blocks

 Prototype ASIC contains 8 pipeline stages



Pad Pitch 100 μm



Summary & milestones

- ❑ Now - first prototypes of the front-end and ADC functional blocks are being submitted
- ❑ ~December 2007 - tests of prototypes completed, design of ADC, S/H
- ❑ ~March 2008 - submission of ADC prototypes and front-end prototypes including S/H
- ❑ ~October 2008 - tests of ADC and front-end completed, design of supporting circuitry (biasing, DACS,...)
- ❑ ~December 2008 - submission of complete front-end and ADC prototypes
- ❑ ~June 2009 - tests of prototypes completed