



BeamCal Electronics Status

FCAL Collaboration Meeting
LAL-Orsay,
October 5th, 2007

Gunther Haller, Dietrich Freytag,
Martin Breidenbach and Angel
Abusleme




Presentation Outline

- ◆ The BeamCal detector
- ◆ BeamCal electronics challenges
- ◆ BeamCal electronics operation
- ◆ High level design
- ◆ Amplifier design
- ◆ Filter design
- ◆ ADC and memory issues
- ◆ Fast feedback design
- ◆ Radiation hardness requirements
- ◆ Tentative design schedule
- ◆ People

The BeamCal detector

◆ Mission:

 - To provide feedback for instantaneous luminosity tuning via beamstrahlung pairs
- To extend the calorimeter hermeticity to the very forward region (low polar angles)



◆ BeamCal structure


- 2 end caps ×
- 30 Silicon – Tungsten sandwiched layers per cap ×
- 1512 channels per layer
- Total channel count: 90,720
- At 32 channels per chip, this implies 2836 chips



BeamCal electronics challenges

- ◆ 32 channels per chip
- ◆ Large input signals, up to 40pC
- ◆ High occupancy, all data is read out at 10 bits for science purposes; gated reset is necessary
- ◆ Low latency output, sum of all channels is read out after each bx at 8 bits for beam diagnosis (fast feedback)
- ◆ Dual-gain front-end (50× ratio), for normal operation and physical signals calibration
- ◆ Radiation hardness requirements
- ◆ Parasitics due to 15-cm wires between detector and chip, detrimental for front-end performance
- ◆ Minimum power dissipation
- ◆ Prototype in 0.18- μm TSMC CMOS technology

BeamCal electronics operation

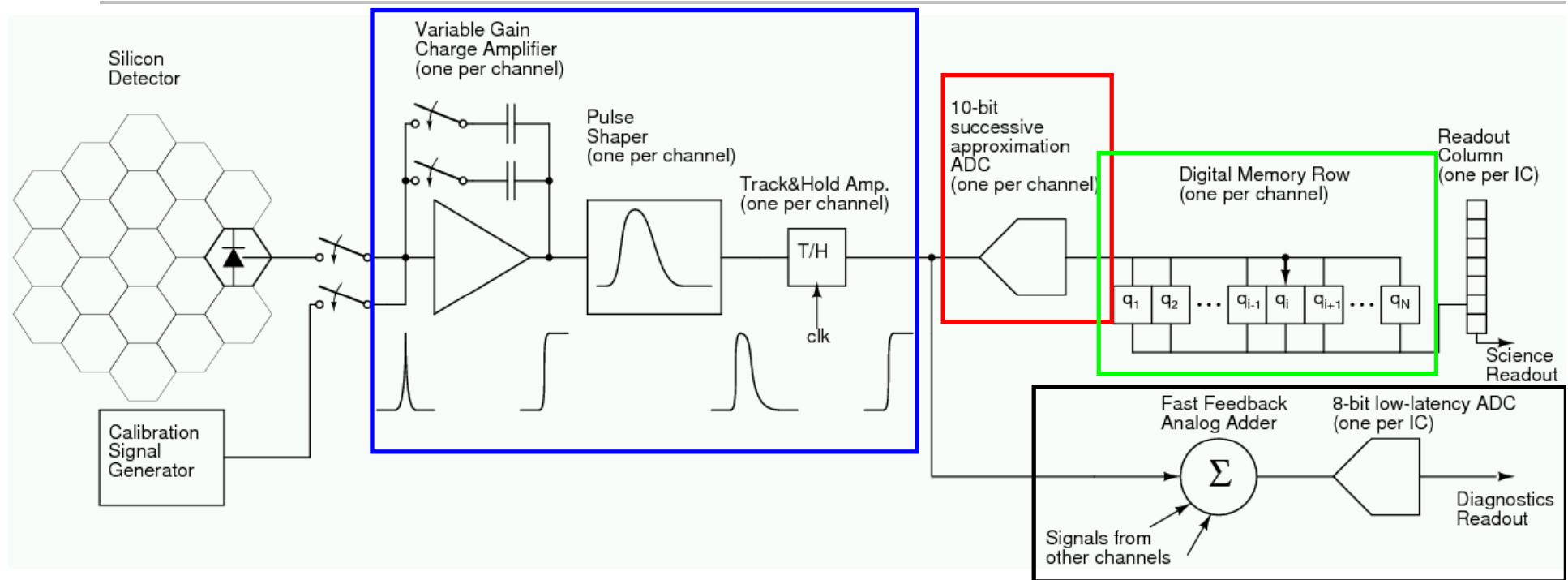


- ◆ Dual-gain front-end electronics: charge amplifier, pulse shaper and T/H circuit
- ◆ Successive approximation ADC, one per channel
- ◆ Digital memory, 2820 (10 bits + parity) words per channel
- ◆ Analog addition of 32 channel outputs for fast feedback; low-latency ADC



BeamCal electronics operation


Timing diagram: between pulse trains

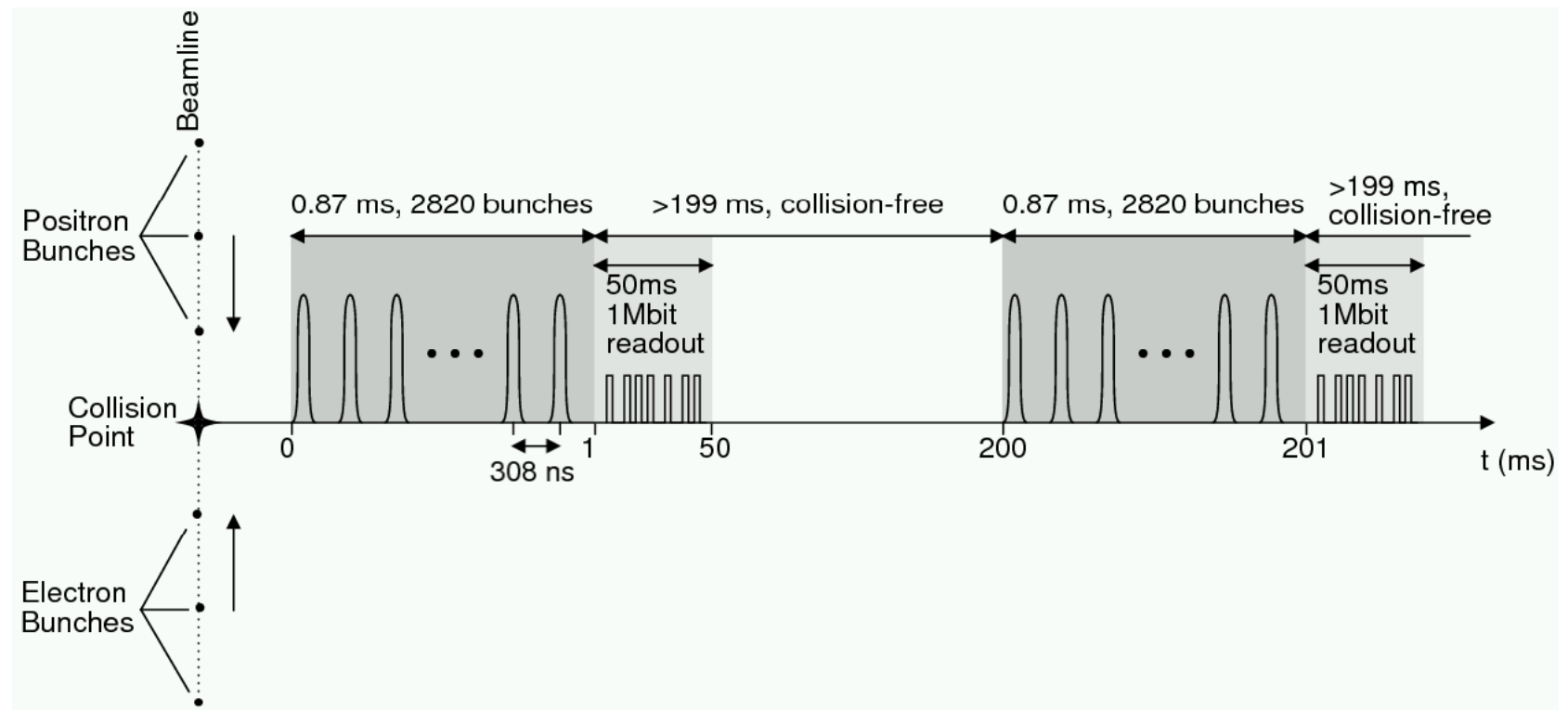



BeamCal electronics operation

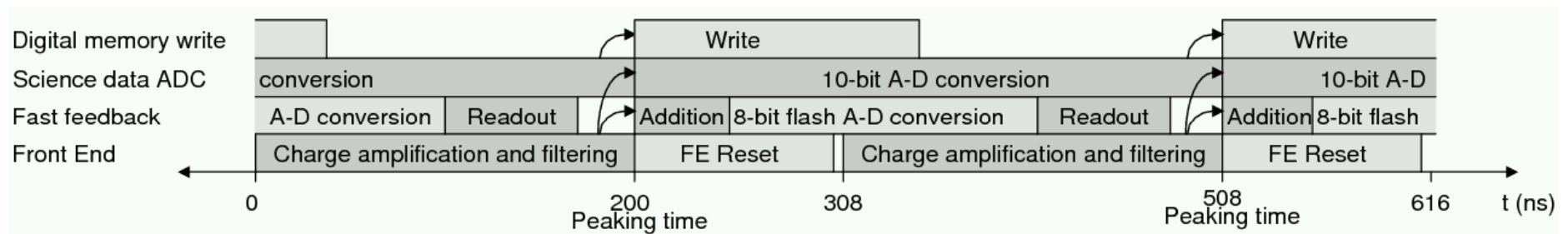Timing diagram: between individual pulses



- ◆ Pipelined timing
- ◆ Exact timing could be mode-dependent




High level Design

- ◆ Behavioral simulations carried out to find:
 - Best architecture
 - Expected performance
 - Expected power consumption
- ◆ Conclusions
 - Charge amplifier current: about $300\mu\text{A}$
 - Filter design: CR-RC (bandpass)
 - Peaking time: 200ns



High level design

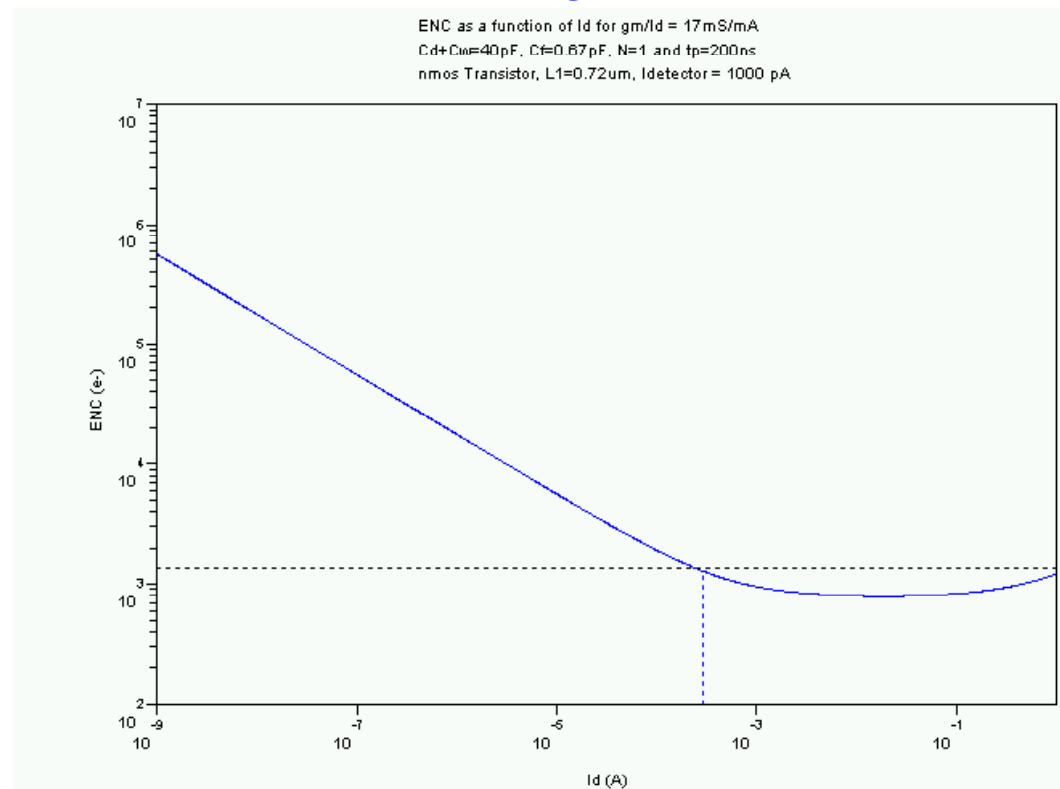
- ◆ Noise simulation, physics calibration mode





Amplifier design

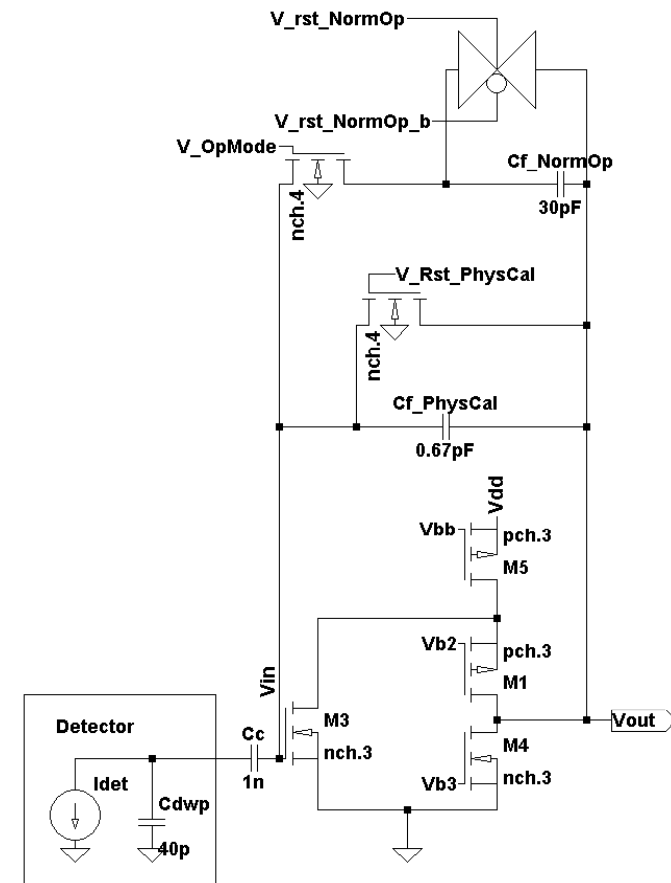
- ◆ Basic charge amplifier – a voltage amplifier and capacitive feedback
- ◆ Low noise design (input transistor, g_m/I_d approach)
- ◆ NMOS input device
- ◆ Two feedback capacitors for different gains
- ◆ Switches for mode selection and reset
- ◆ 1-V output swing





Amplifier design

 - ◆ SPICE output waveforms, normal operation and physics calibration






Filter design

- ◆ Filter domain
 - Continuous time: issues for τ calibration
 - Sampled time: precisely adjustable τ
- ◆ Filter topology
 - CR-RC: inadequate for gated reset
 - Biquad: perfect for gated reset
- ◆ Implementation details
 - Fully differential, switched-capacitor biquad implementation
 - Using SC inverting integrators (backward Euler integration)
 - Filters voltage across feedback capacitor – good PSR
 - 100MHz switching frequency does not affect frequency response in band of interest
 - 25MHz switching frequency does affect frequency response and requires an increase in charge amplifier current in order to meet noise specs



Filter design

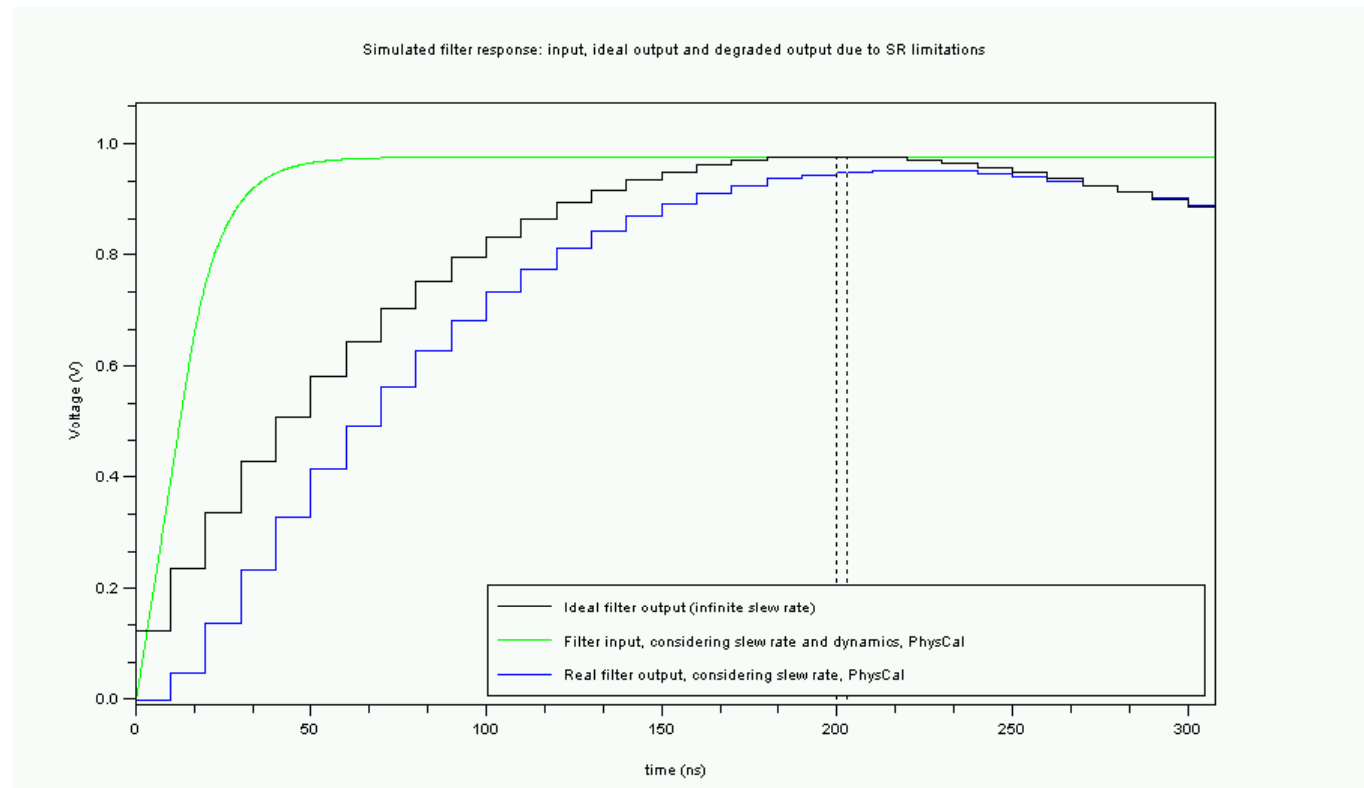
◆ Filter output waveforms, behavioral simulation






Filter design

◆ Amplifier and filter spectra

 

Filter design

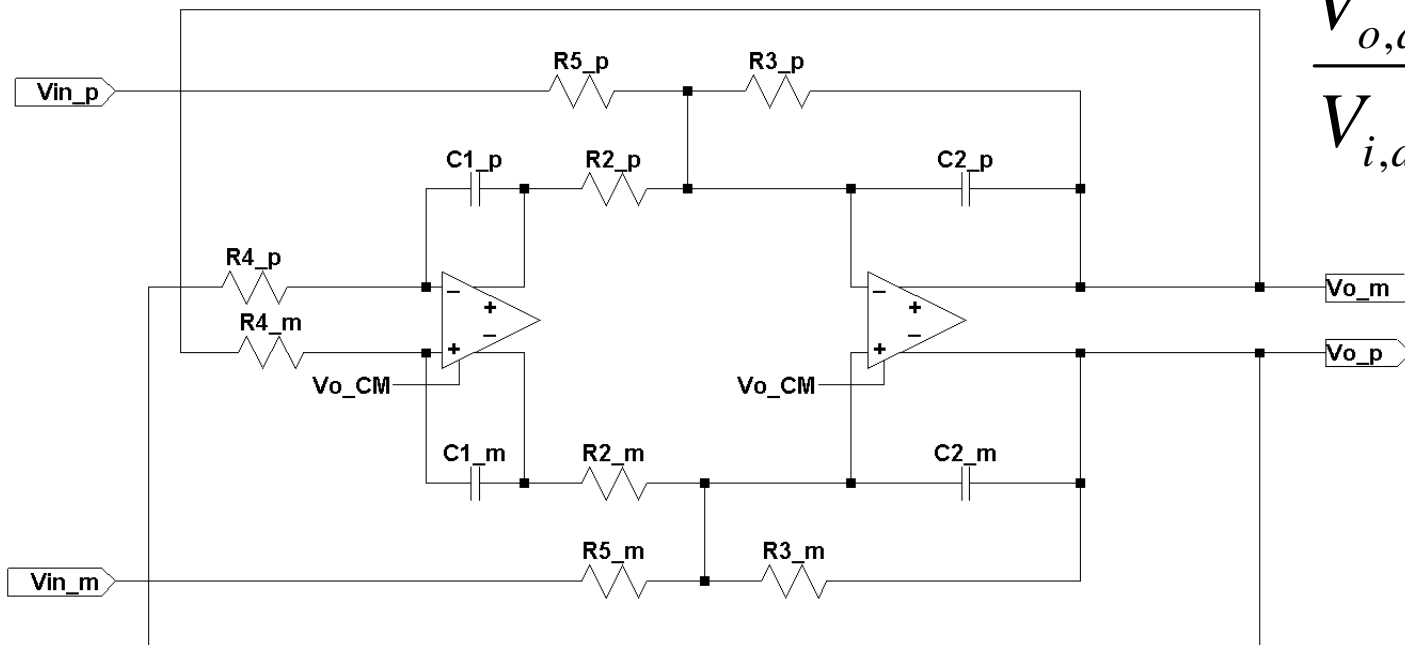- ◆ Differential, continuous-time biquad...




$$\frac{V_{o,d}}{V_{i,d}} = \frac{A_0 s \tau_p}{(1 + s \tau_p)^2}$$



Filter design


- ◆ Conversion to SC + reset transistors

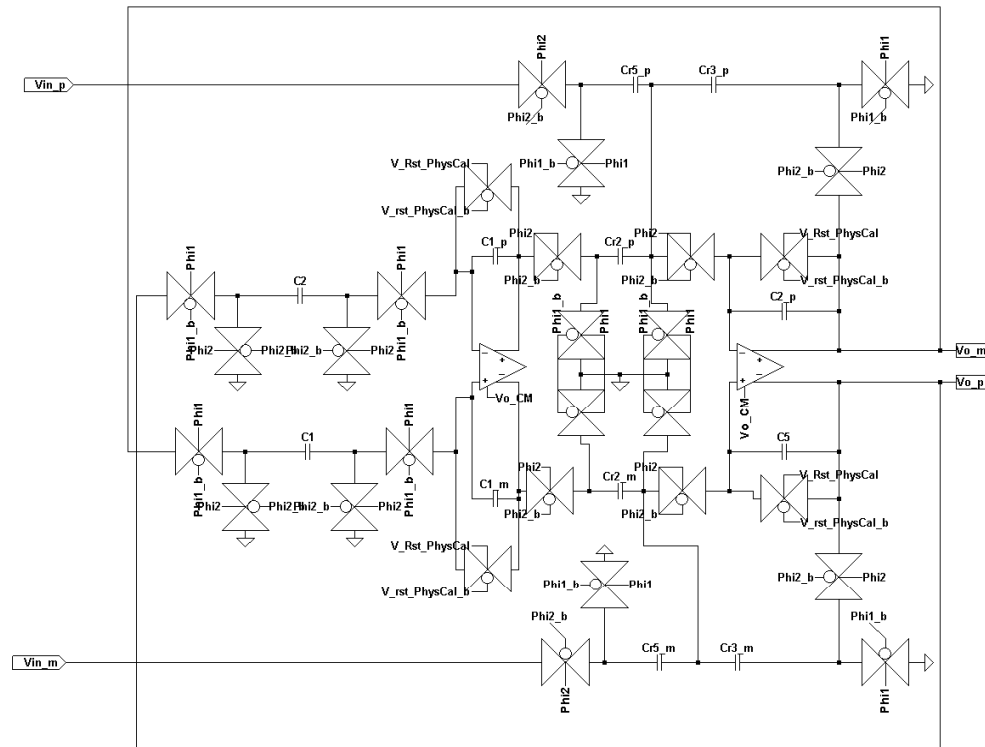



Filter design

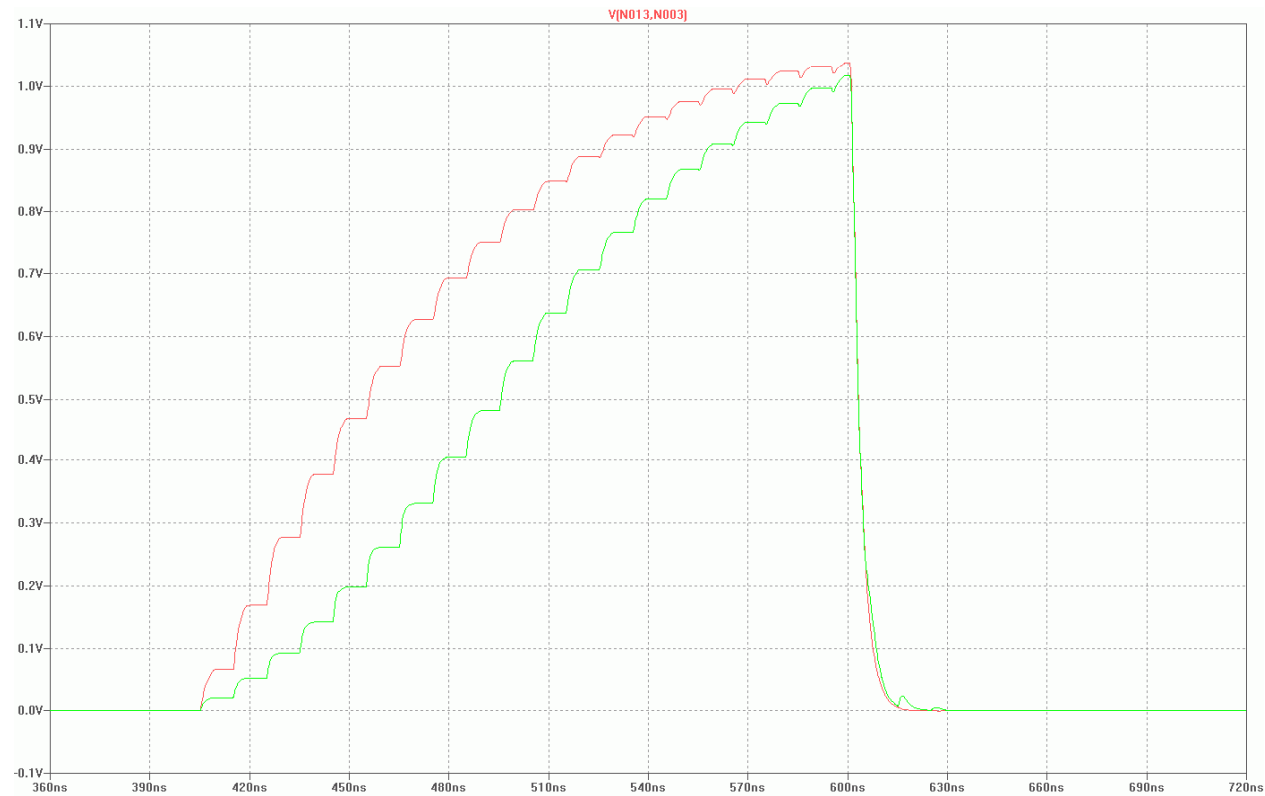- ◆ Output waveforms, normal operation and physics calibration






ADC and memory issues

- ◆ ADC power consumption is lightly dependent on the number of ADCs
 - one channel per ADC is simple in terms of operation
 - many channels per ADC are efficient in terms of area
 - successive approximation ADCs present a balanced tradeoff, could eventually assign a single channel per ADC without a significant increase in area
- ◆ Memory choice: analog or digital?
 - Analog memory problems:
 - ◆ high droop rate due to switch leakage in TSMC018 (especially after irradiation)
 - ◆ radiation-tolerance techniques are not simple nor flexible
 - Digital memory problems:
 - ◆ more area
 - Digital memory will be used mainly due to flexibility

Fast feedback design

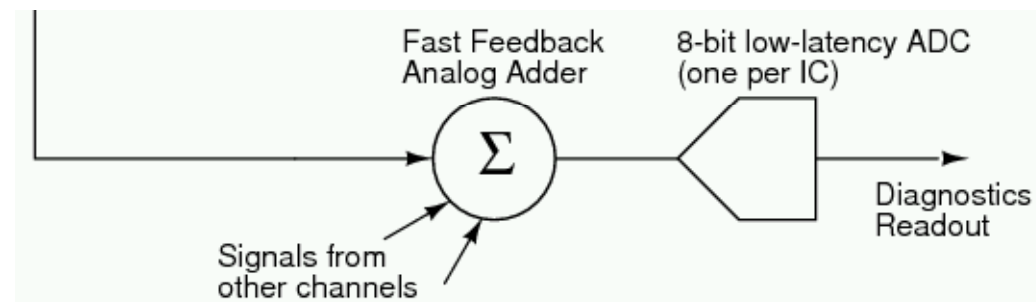- ◆ Each channel's analog signal is extracted at the track-and-hold circuit output
- ◆ Analog adder generates the chip fast feedback signal
- ◆ A fast (low-latency) ADC is used to produce the digital output





Radiation hardness requirements

- ◆ Chip must be able to tolerate 1Mrad(SiO_2) total ionizing dose (TID)
- ◆ TSMC018 is naturally tolerant to TID, but some sensitive circuits in the chip require additional protection
- ◆ This can be done by using mitigation techniques:
 - Enclosed-layout transistors
 - Guard rings
- ◆ Consequences in circuit design:
 - Power consumption increases by 2× or more, depending on the circuit
 - Chip area increases by 2.5× in some circuits
- ◆ First prototype will not be radiation-tolerant, but will allow to:
 - assess the technology tolerance to radiation
 - detect the most radiation sensitive circuits



Tentative design schedule

- ◆ April 2007: High level design complete
- ◆ July 2007: Charge amplifier designed
- ◆ October 2007: Filter designed
- ◆ January 2008: ADC designed
- ◆ February 2008: Memory designed
- ◆ March 2008: Fast feedback designed
- ◆ April 2008: Bias and supporting circuits
- ◆ July 2008: Circuit layout complete
- ◆ August 2008: Verification complete
- ◆ October 2008: Prototype ready
- ◆ January 2009: Prototype tests complete



People

- ◆ Angel Abusleme (PhD student)²
- ◆ Professor Martin Breidenbach¹
- ◆ Dietrich Freytag¹
- ◆ Gunther Haller¹
- ◆ Professor Bruce Wooley²

Affiliations

1. SLAC
2. Department of Electrical Engineering, Stanford University