

Fig. 1. The Diplexer LPF. Reflection.

Within the bandwidth (170MHz), the reflection is lower than (-24)dB. At higher frequencies, it is poor due to parasitic capacitance to GND in the HPF. The reflection (a derivative) of a step 170ps is 1/5. The reflection from a LPF without a HPF (shown dark blue) is about four times bigger.

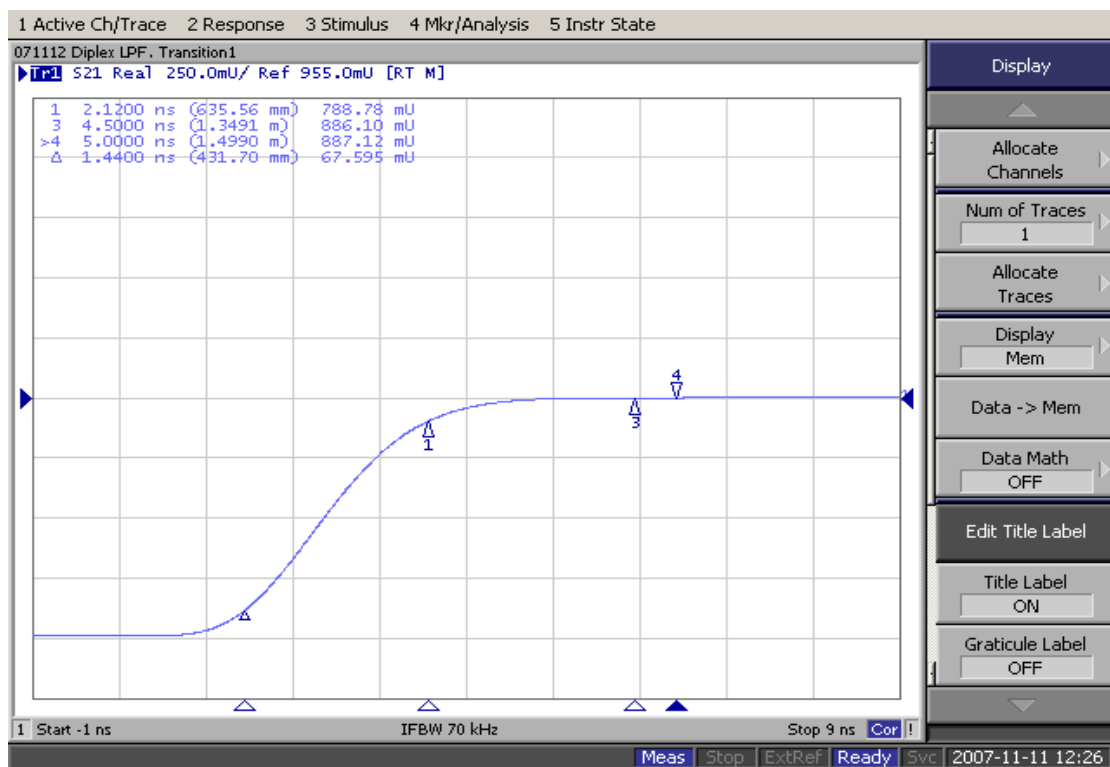
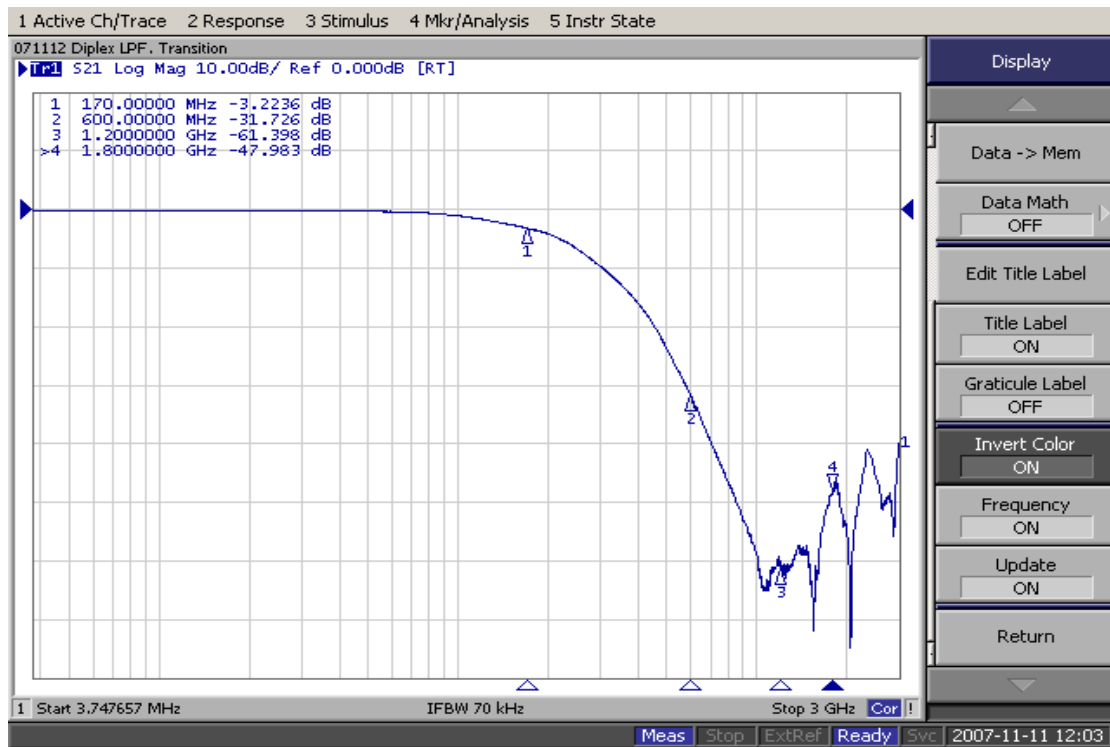


Fig. 2. The Diplexer LPF. The bandwidth and step response.

The bandwidth is 170MHz. At 600MHz, (-32)dB. At 1200MHz, about (-60)dB. At 1800MHz, about (-50)dB. The rise time is 2.1ns.

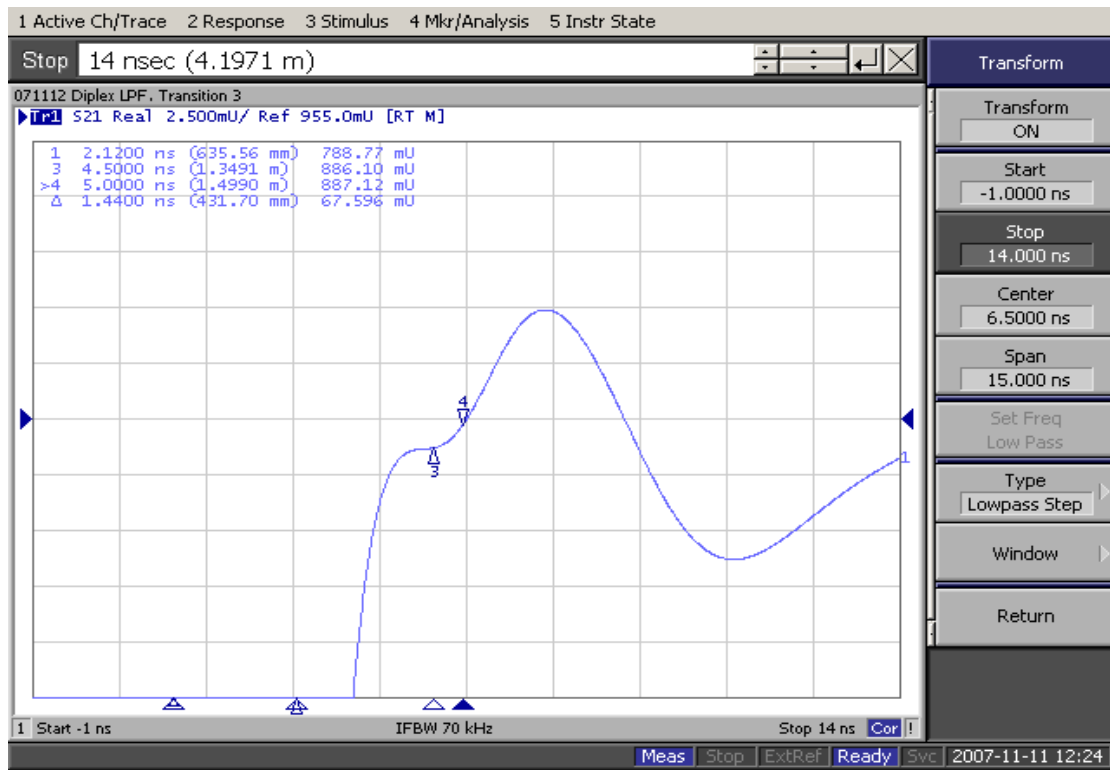


Fig. 3. The Diplexer LPF. Zoom of the step response.

One division is 0.25%. The ripple is lower than $\pm 1\%$. An inherent ripple of three cell Gaussian filter plus a ripple due to spread of component values.

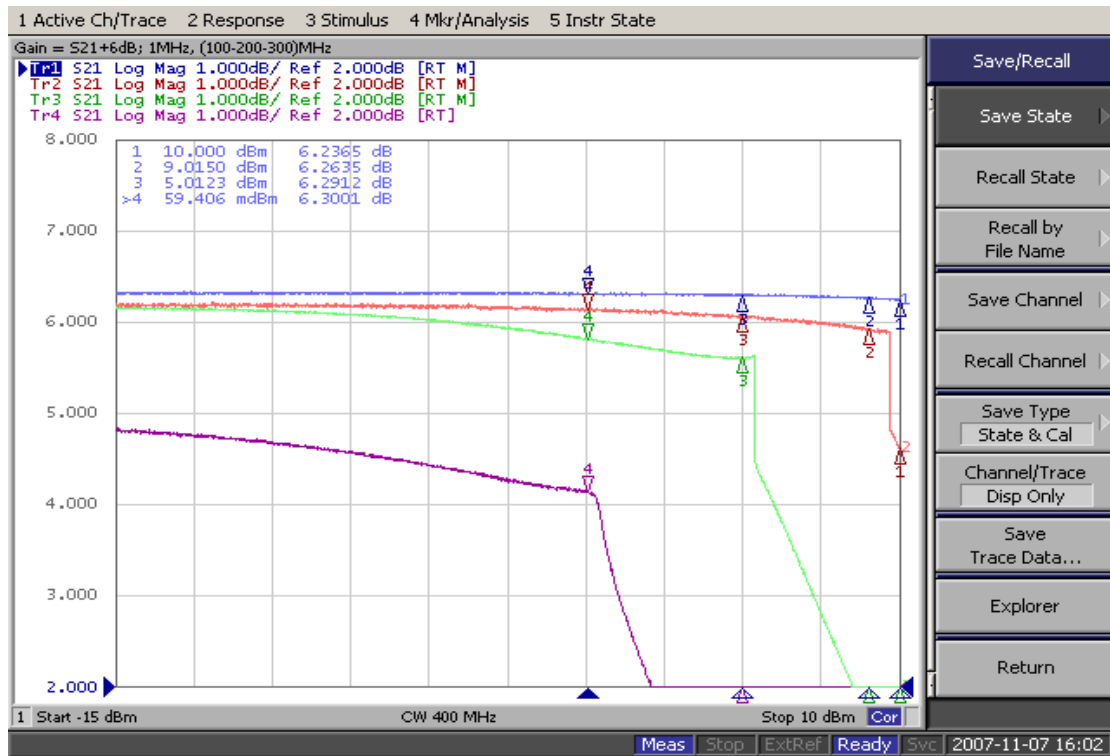
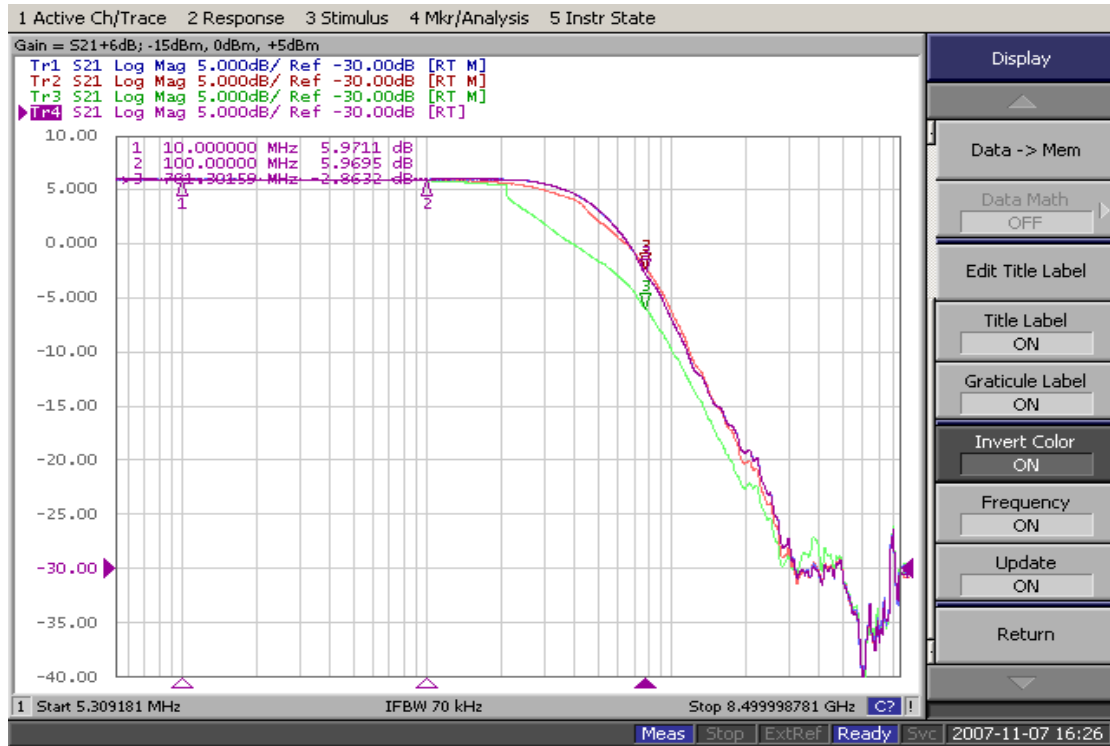


Fig. 4. A low noise AD8000. Gain = +4. The bandwidth and compression points.

The bandwidths for three input levels: (-15)dBm purple, 0dBm red, (+5)dBm green. A small signal bandwidth is about 500MHz. The compression points for four frequencies: 100MHz blue, 200MHz red, 300MHz green, 400MHz purple.

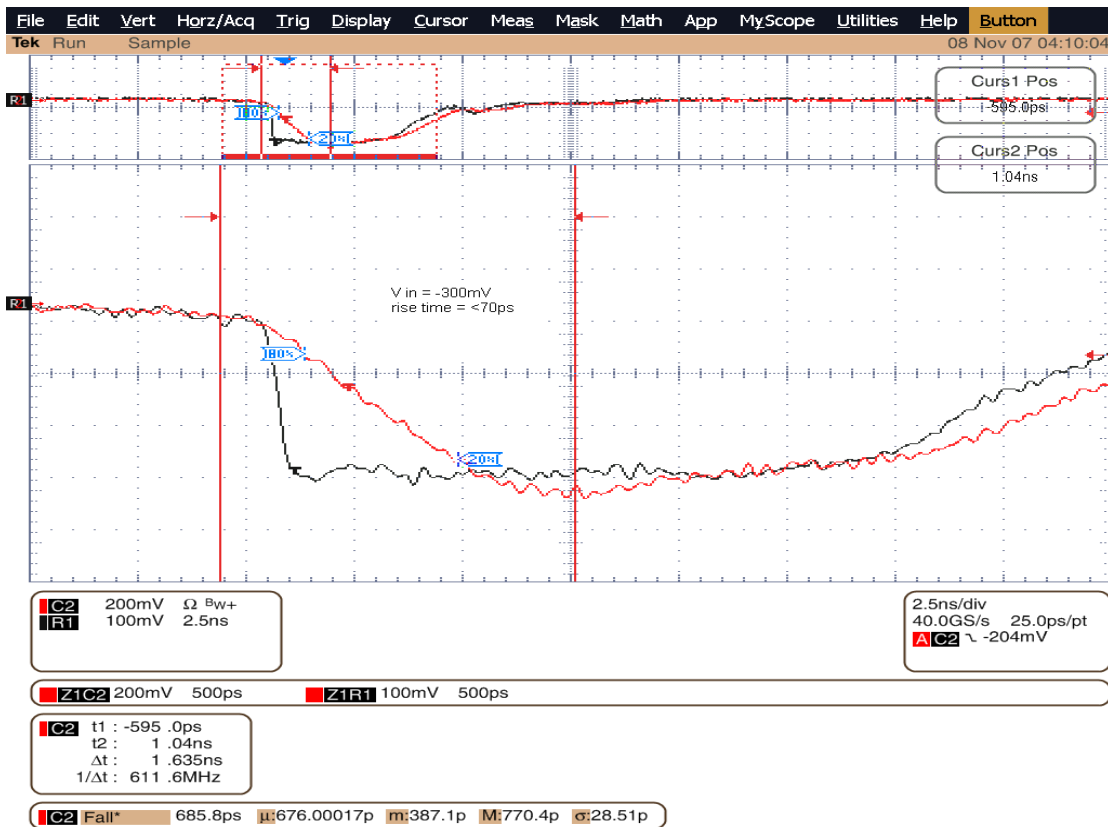
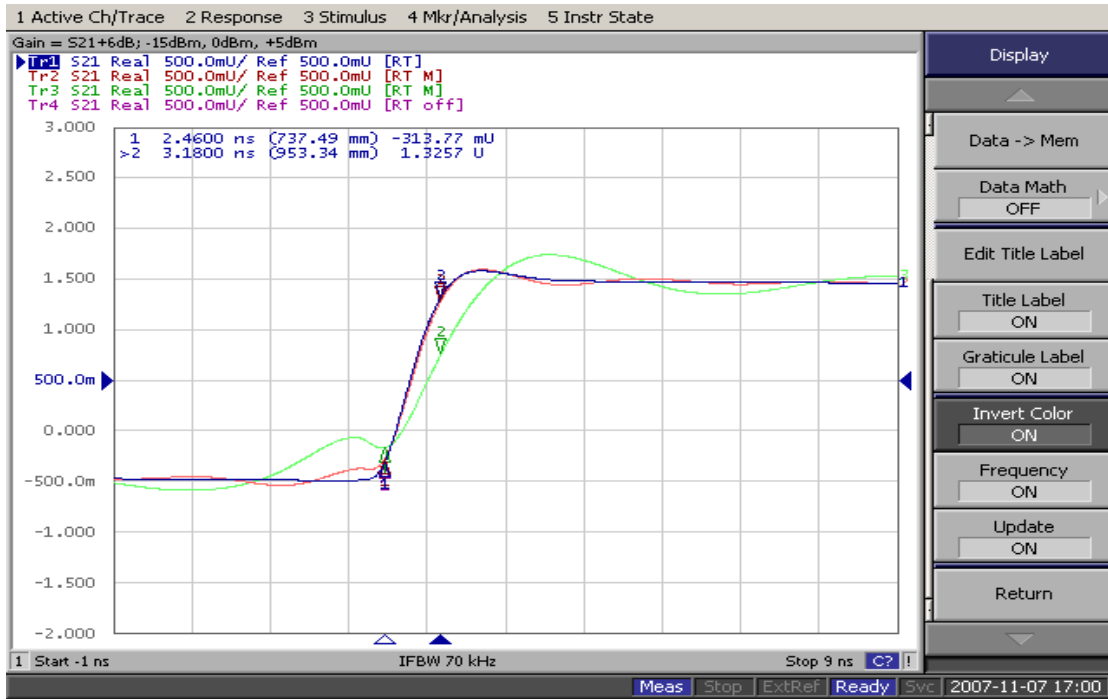


Fig. 5. A low noise AD8000. Gain = +4. The step response.

The step response for three input levels: (-15)dBm blue, 0dBm red, (+5)dBm green. At a high level, a feedthrough is seen.

The rise time for (-15)dBm is lower than 700ps. The oscillogram shows a 1.2V 690ps response to a 70ps step from a pulse generator. Same overshoot is seen.

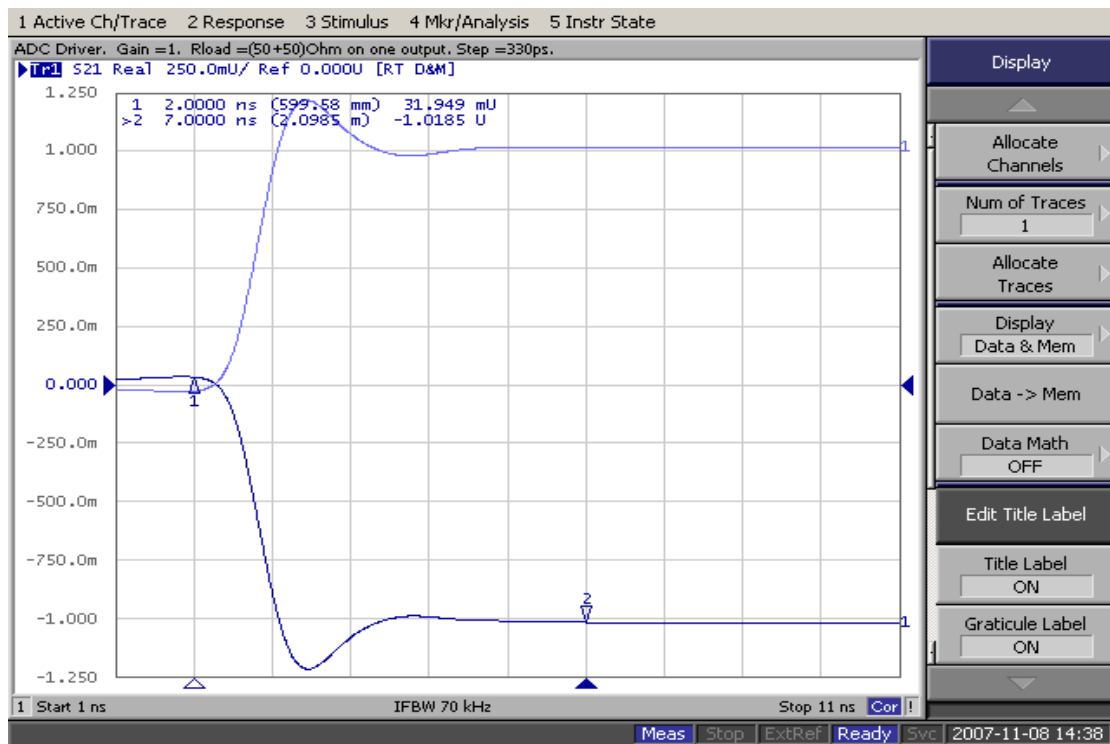
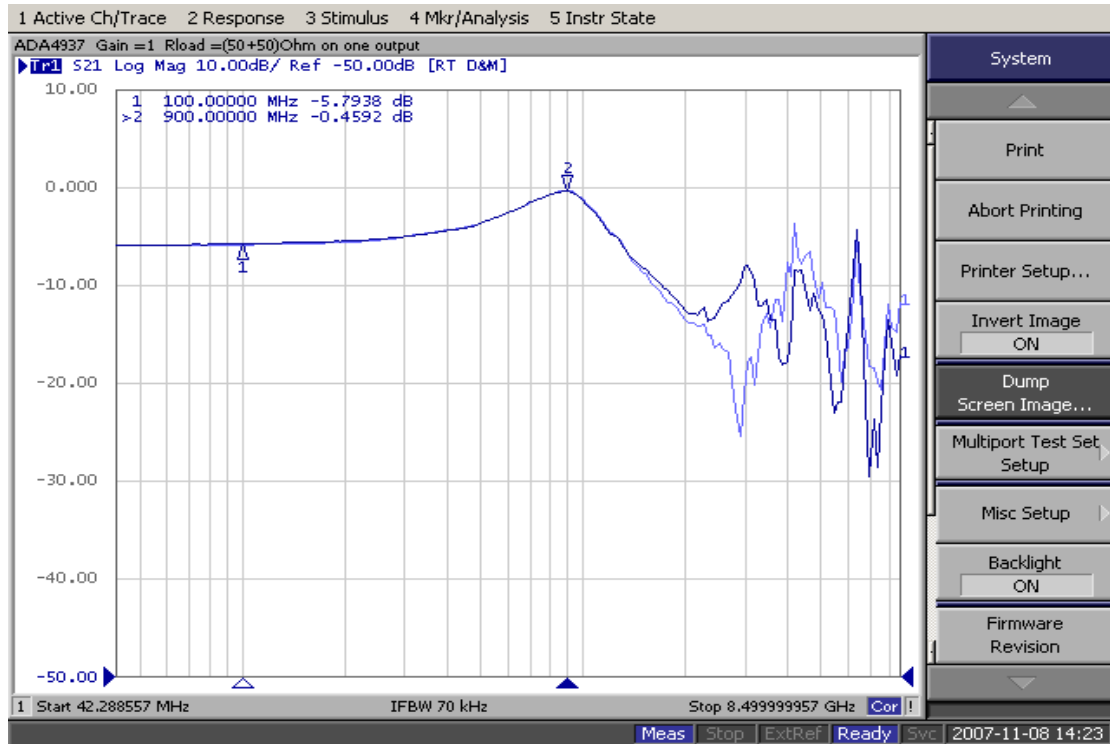


Fig. 6. A differential amplifier ADA4936-1. A single-ended to differential Gain = ± 0.5 . The bandwidth and step responses.

The bandwidth is about 1600MHz. Piking at 900MHz. A large feedthrough above 2000MHz. The step response about 400ps has a significant overshoot.

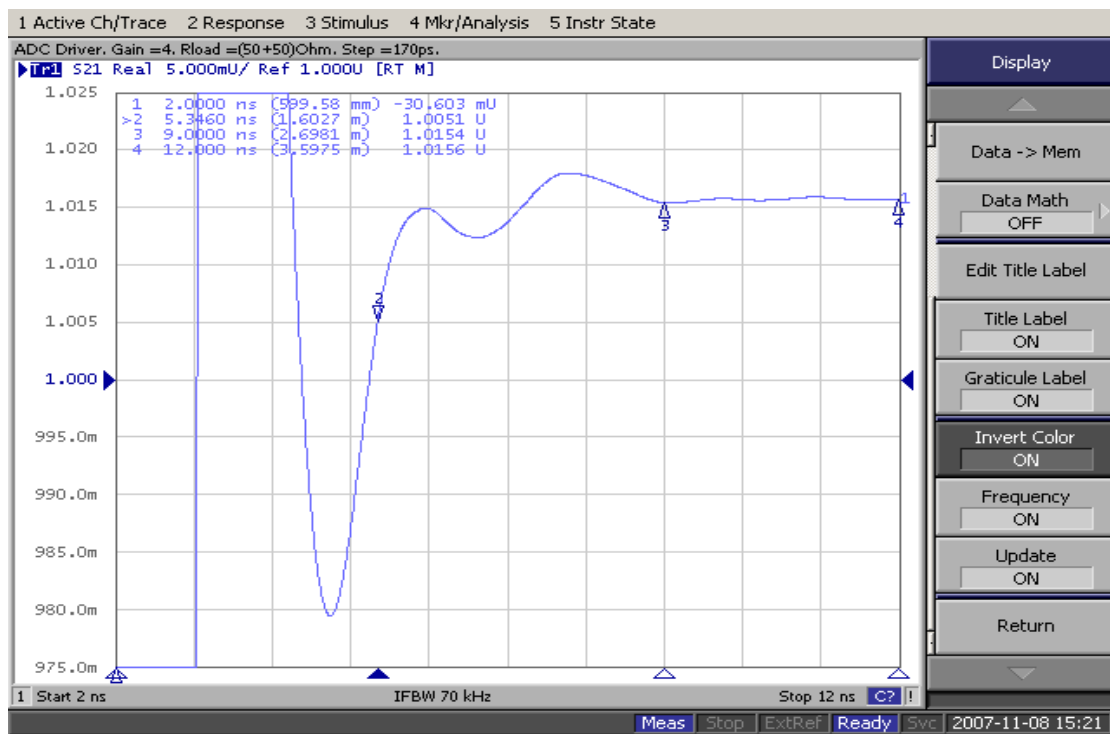
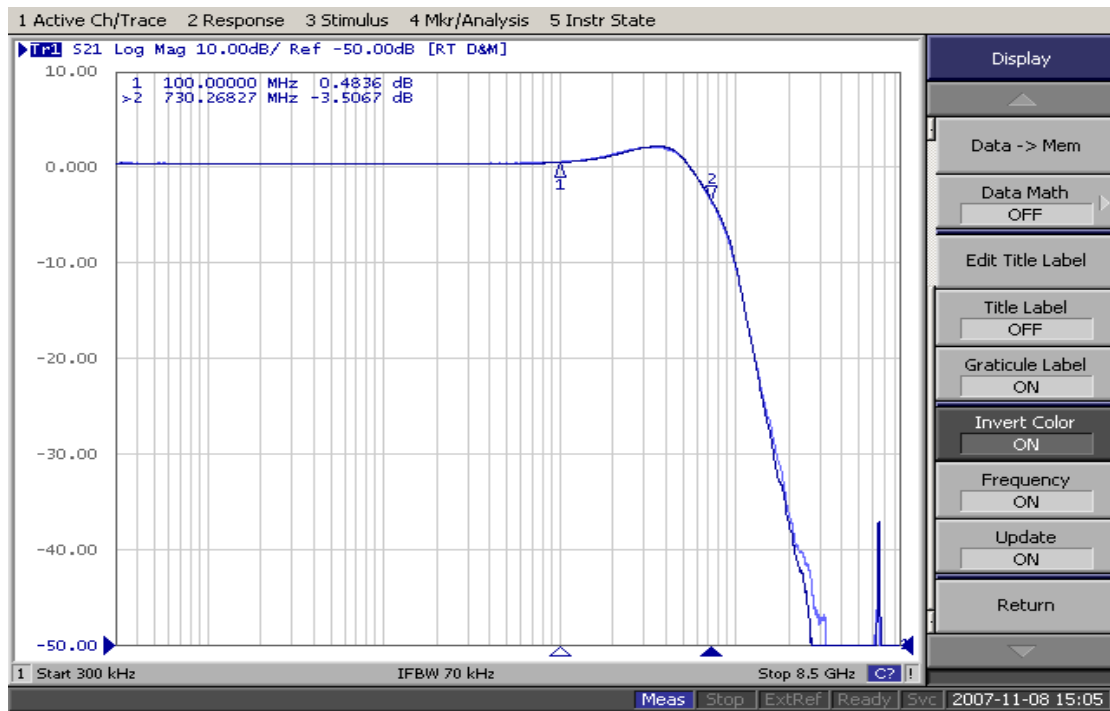


Fig. 7. AD8000 + ADA4936-1. A single-ended to differential Gain = ± 2 . The bandwidth and zoom of the step response.

The bandwidth is about 700MHz. Still piking, at 400MHz. The feedthrough is (-40)dB.

The step response comes to (-60)dB at 9ns (one division is 0.5%).

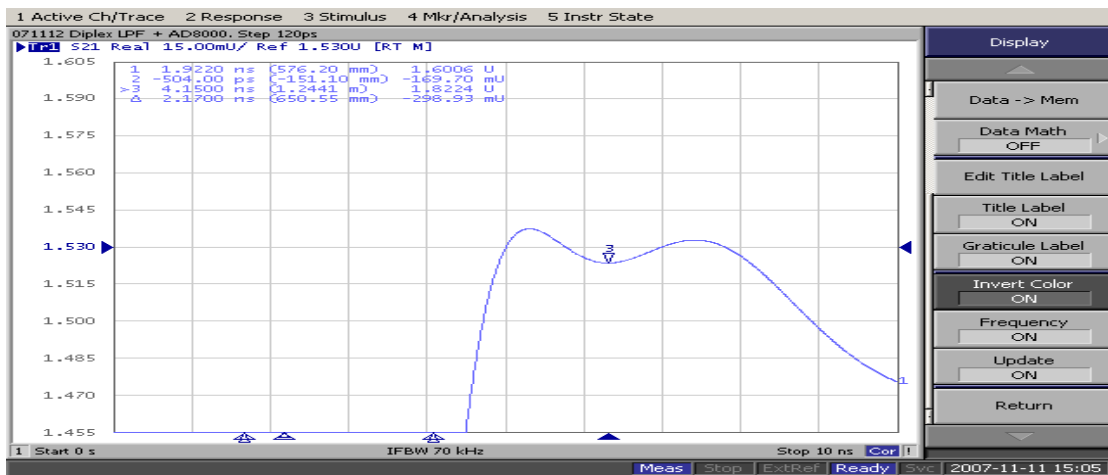
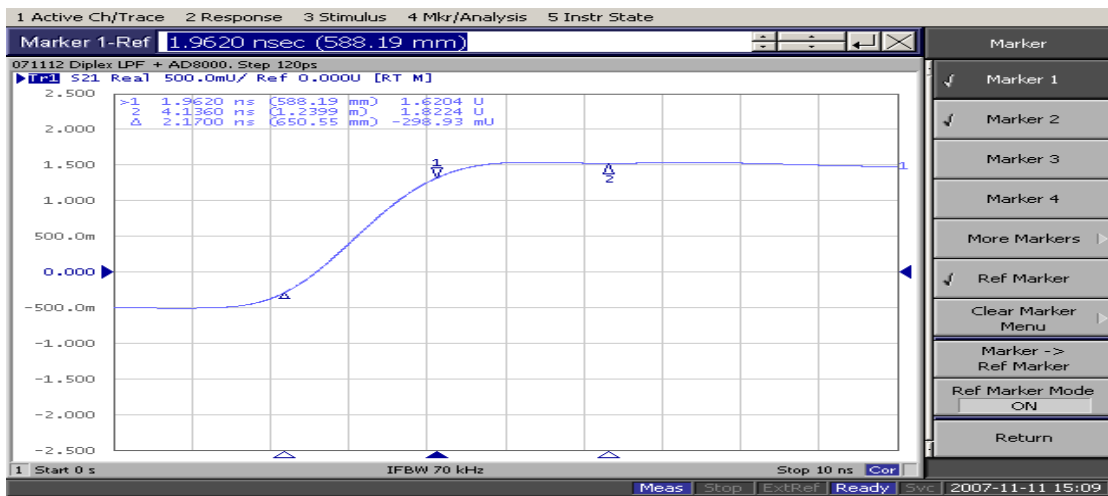
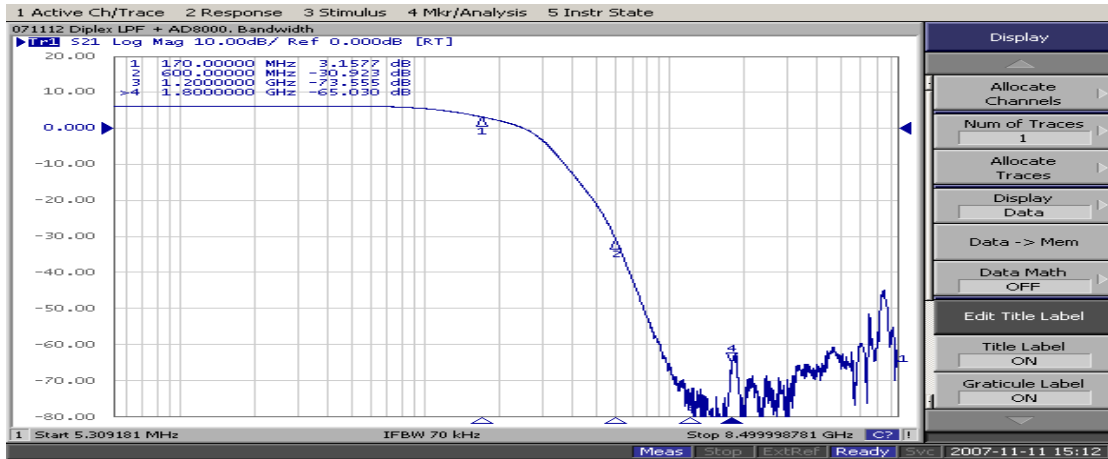


Fig. 8. A Driver for a single-ended ADC: Diplexer LPF + AD8000. The Gain = 4. The bandwidth and step response.

The bandwidth is the LPF bandwidth 170MHz. At the first harmonic 600MHz, (-36)dB. At 1200MHz, (-80)dB. At 1800MHz, (-70)dB. For a input pulse 5ns, at about 4ns there is a plateau about ± 1 ns, where the ripple is lower than $\pm 0.5\%$ (one division is 0.75%). The marker 3 is put there where the measurement point should be set.

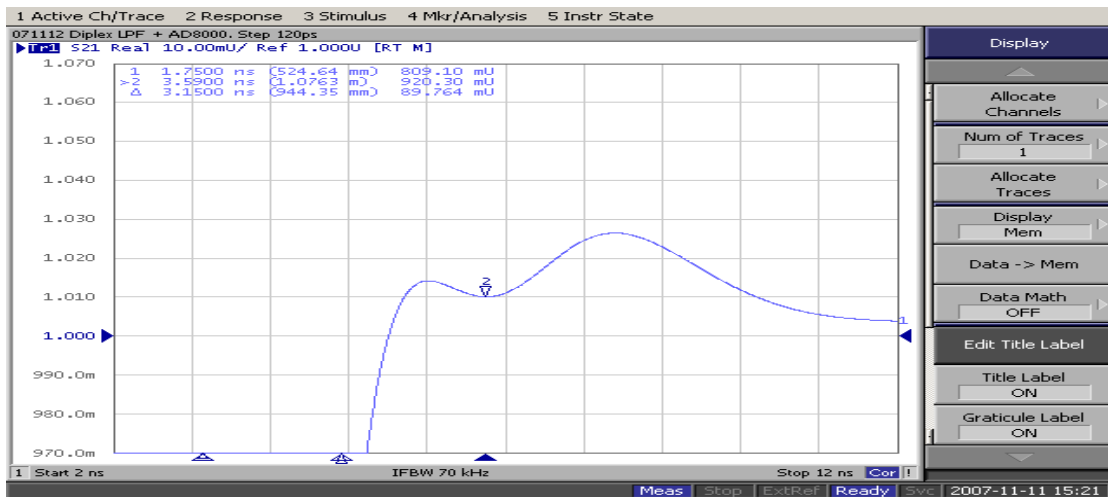
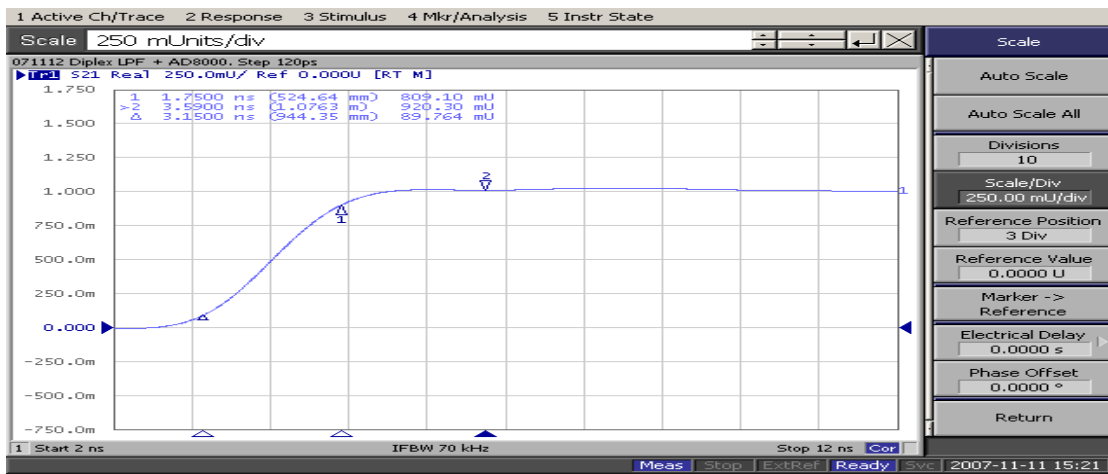
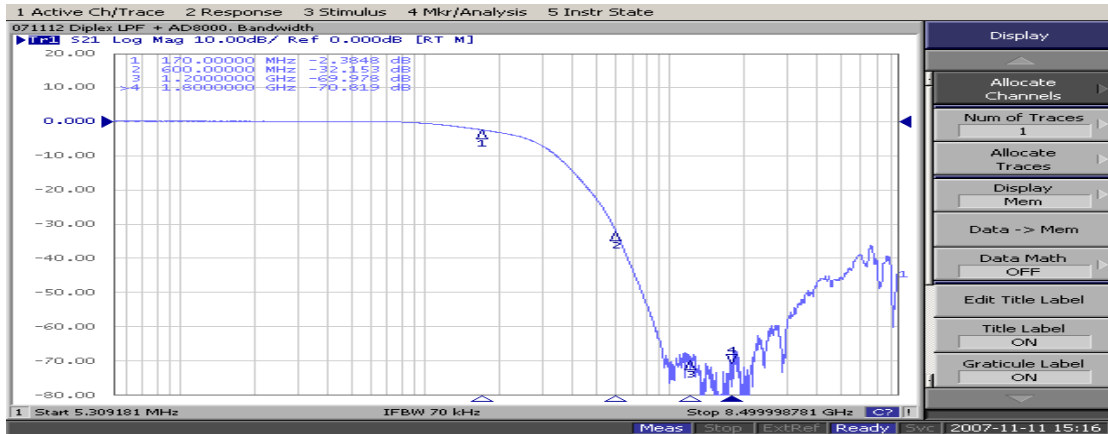


Fig. 8. A Driver for a differential ADC: Diplexer LPF + AD8000 + ADA4937-1.
The Gain = ± 2 . The bandwidth and step response.

The bandwidth is the LPF bandwidth 170MHz. At the first harmonic 600MHz, (-32)dB; at 1200MHz, (-70)dB; at 1800MHz, (-70)dB. A capacitive feedthrough over 2000MHz.

For an input pulse 5ns, at about 4ns there is a plateau about ± 1 ns, where the ripple is lower than $\pm 0.5\%$ (one division is 1%). The marker 2 is put there where the measurement point should be set.