

Omega



Digital Interface inside ASICs & Improvements for ROC Chips



Frédéric DULUCQ
02/06/2008


Orsay MicroElectronic Group Associated

 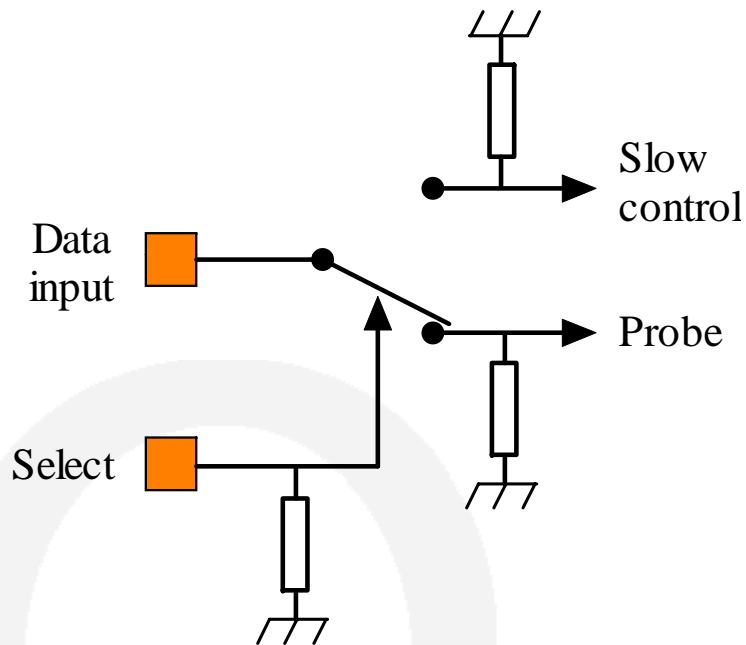- Multiplex these 2 registers (in, out, clock, reset) → save PADS (8 → 4+1)




- Select line added : default register is probe to prevent glitch on SC

 - Improve shift registers daisy chain between ASICs:
 - Add opposite edge FF at the end of shift registers



- Chip "N" sends data at falling edge and chip "N+1" captures at rising edge (time margin = half period clock)
- Inside chip → use clock reversing to prevent timing problem

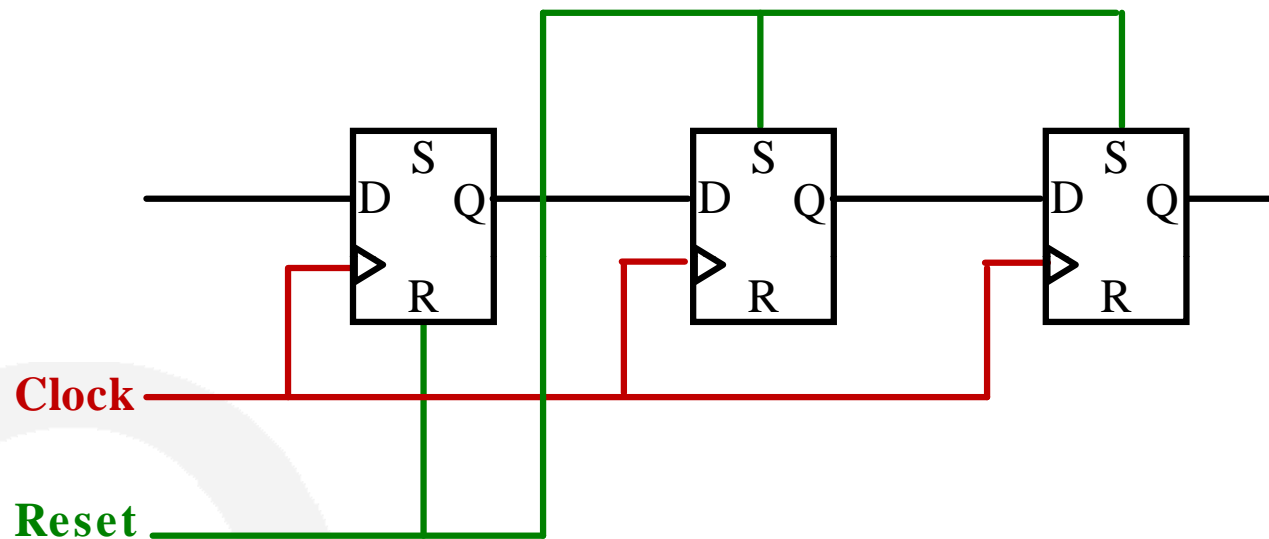
- Use Set / Reset of Flip-Flops for default configuration



 Example default configuration : "011"

- Implemented for digital interfaces (HARDOC2 and SPIROC2)

- During readout, remove “bad frame” (address pointer error when chip is not full)





First irrelevant
frame

- Capacity of 127 trigger instead of 128 → change digital memory limits

SPIROC → All ROC Chips : StartAcquisition

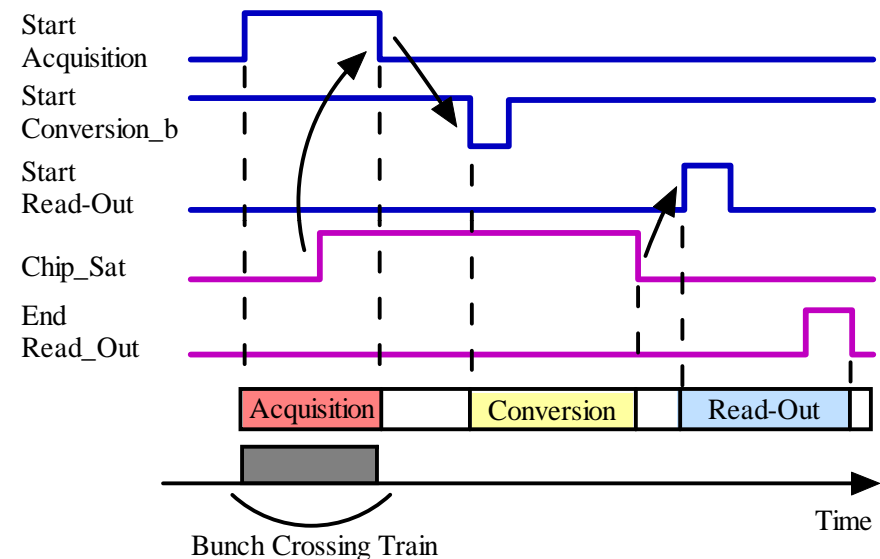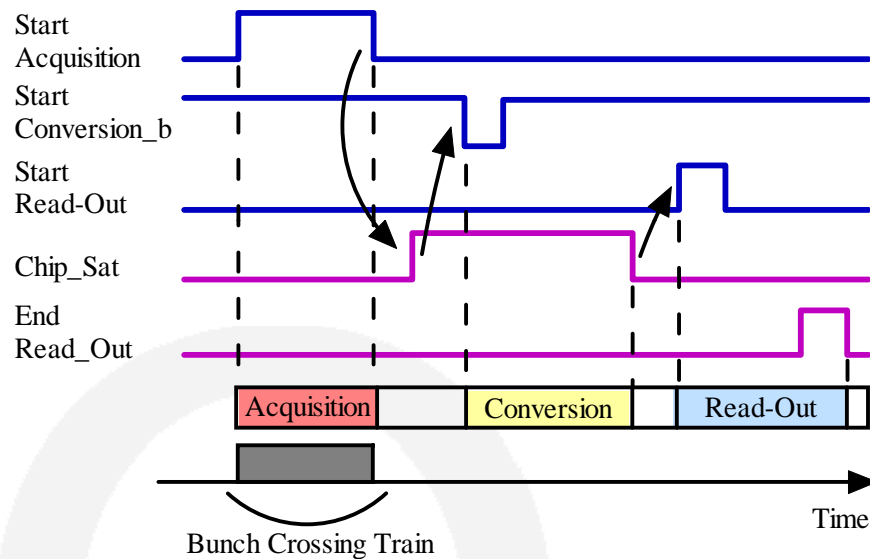- Change for SPIROC like → “StartAcquisition” active on level.




- RamFull → ChipSat (uniformity between ROC chips)
- Allow to remove “RamFullExt” signal (DHCAL) and to let DAQ stop acquisition

StartReadOut and EndReadOut: bypass



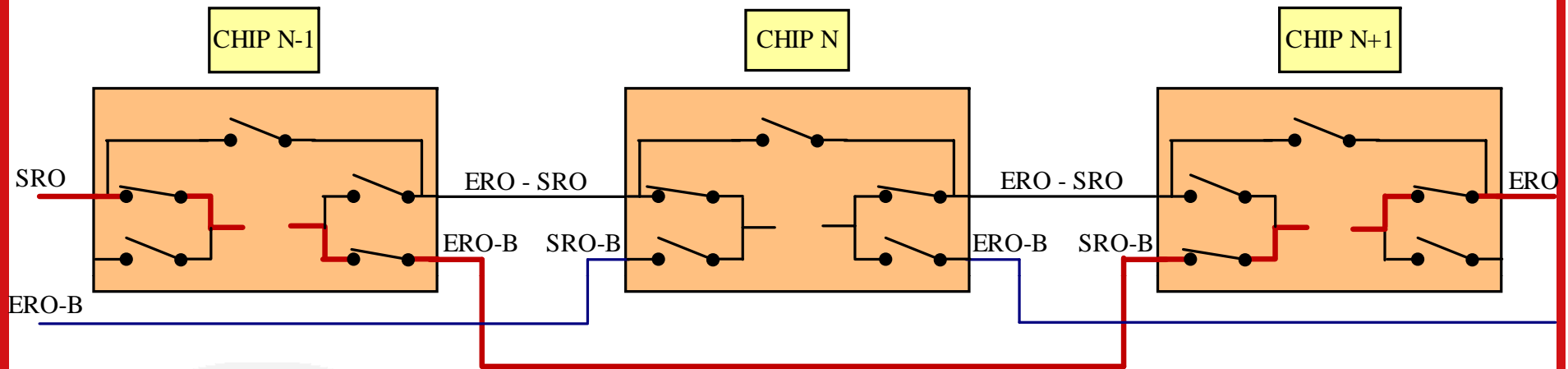- Add bypass for these 2 signals (SRO, ERO → SRO-B, ERO-B).




In red, StartReadOut and EndReadOut flow if chip "N" fails

- Chip N can bypass itself by SC
- Chip "N-1" and chip "N+1" can bypass chip "N" by SC
- If Chip N fails :
 - Chip N-1 sends EndReadOut signal on EndReadOutBypass
 - Chip N+1 reads StartReadOut signal on StartReadOutBypass

Slow Control: bypass

Omega

- Add bypass jumpers on PCB

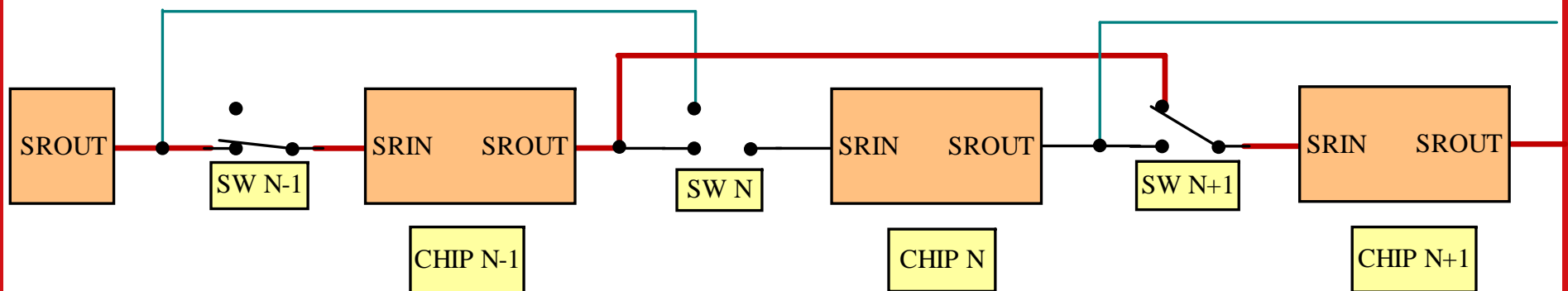


In red, SC flow if chip "N" fails


- Default position is chip "N" reads chip "N-1"
- If Chip N fails :
 - Switch N removed
 - Switch N+1 → in position to read chip "N-1"

Data and TransmitOn: extra buffers

 - Add 1 extra buffer on these 2 signals
- Each one is removable from bus line by SC




OR

 


- Allow to remove one buffer that stick the bus line

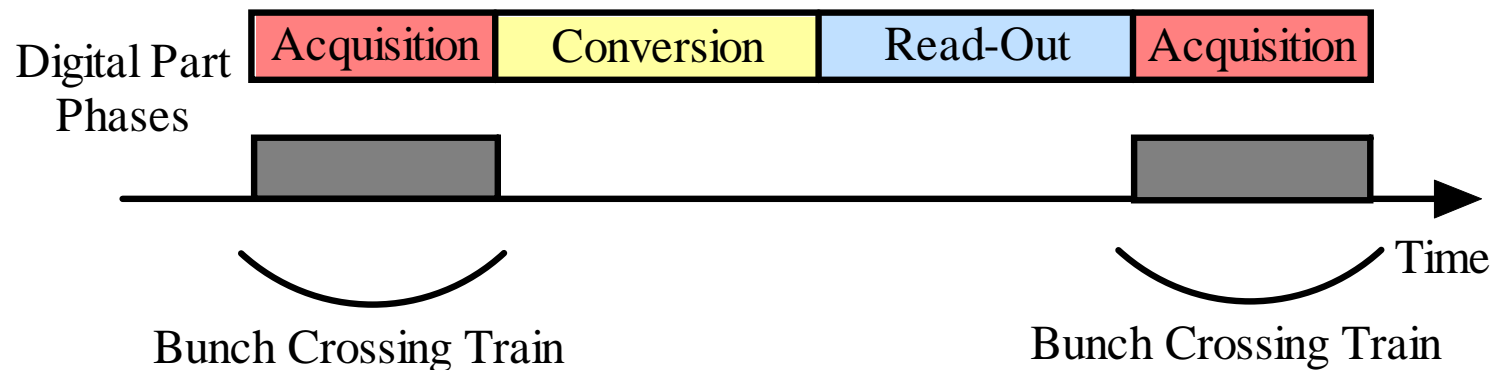- ILC based on a 200 ms bunch crossing period



- Timing aspect of each phases:
 - Acquisition: 1 ms (common)
 - Conversion : max 103 us = 12 bits ADC @ 40 MHz (common)
 - Readout (daisy chained) @ 5 MHz:
 - max 4 ms for 1 HARDROC
 - max 3.8 ms for 1 SPIROC
 - max 0.6 ms for 1 SKIROC
- Max working time for 1 chip < 5 ms (195 ms idle)


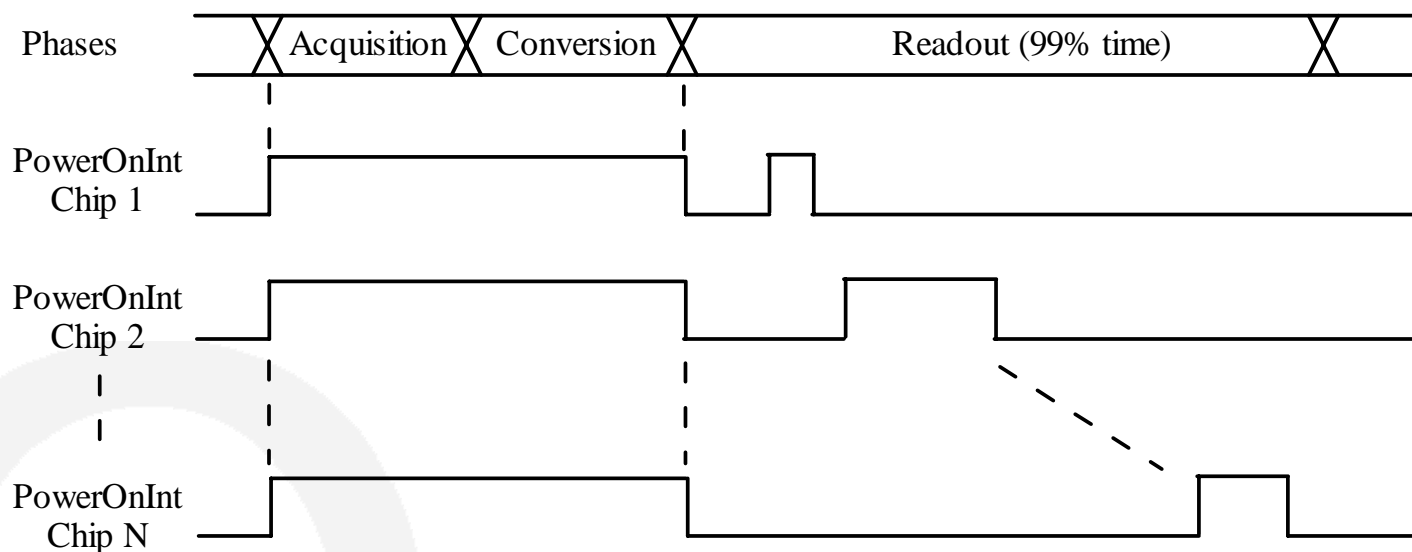
- PowerON start/stop clocks and LVDS receiver bias current to meet power budget.



- 2 working modes :
 - Acquisition, Conversion → common to all managed by DAQ
 - Readout → daisy chained managed by StartReadOut and EndReadOut


Power On Digital: POD block diagram

 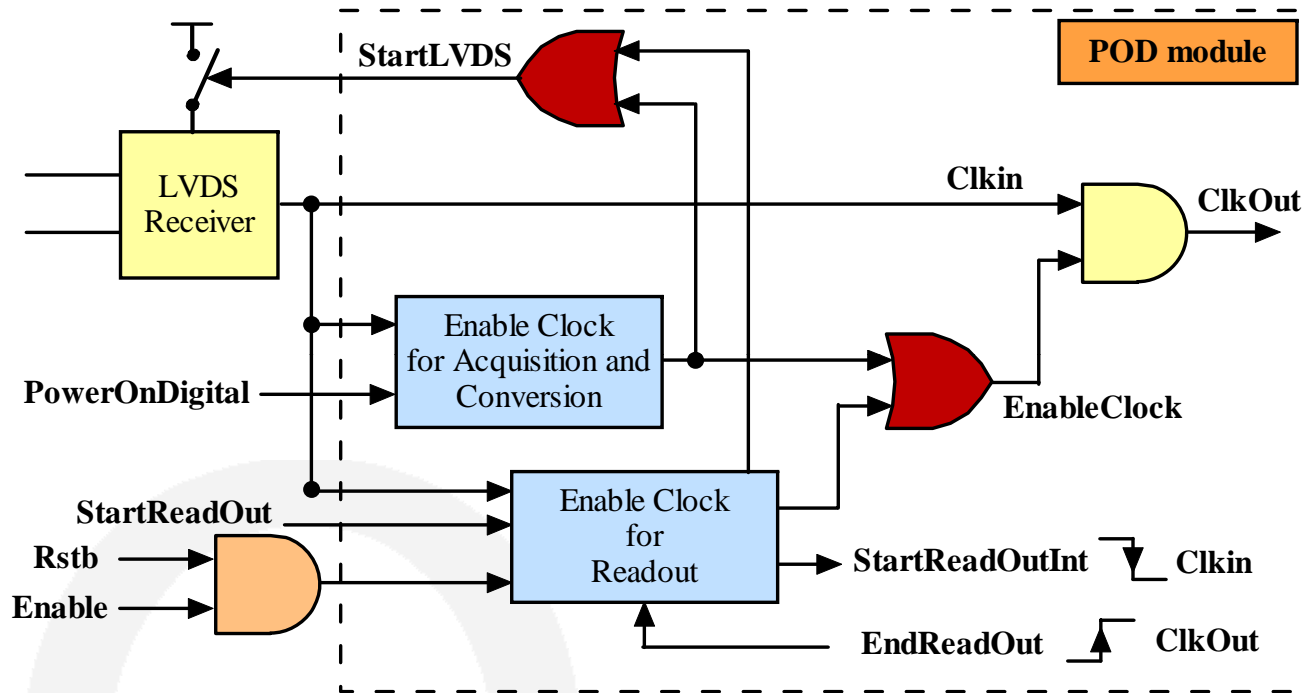- POD module inserted for the 2 clock LVDS receivers



- Clock is started asynchronously, enabled and stopped synchronously (at '0')
- 2 others LVDS receivers (RazChn/NoTrig and ValEvt) active during PowerOnAnalog (during bunch crossing)

Power On digital: sequence

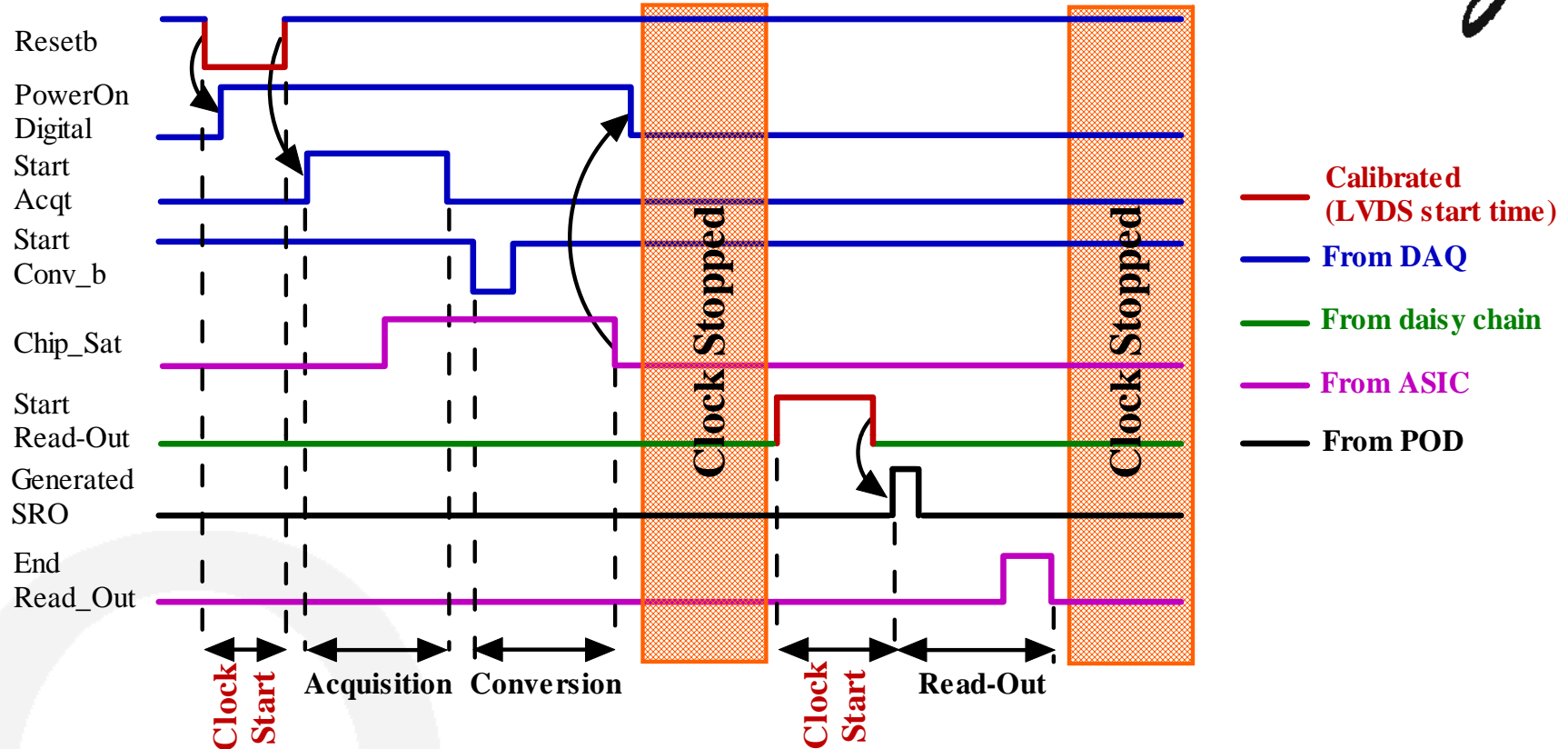

- Some security added:
 - StartReadOut managed asynchronously → low pass filter added
 - Possibility to use StartReadOut instead of the one generated by POD (like first prototype of ROC chips)
 - PowerOnDigital at '1' can force the clock


CONCLUSION



- Next run for SPIROC2 and HARDROC2 is 9 June 2008
- Many improvements already inserted for the run:
 - Shift registers improvements (multiplex, default, extra FF)
 - Bypass signals
 - Extra buffers
 - Bug correction for DHCAL
- 1 Major improvement for digital is POD module (in progress):
 - Start / Stop clocks
 - Start / Stop LVDS receivers
- POD should be implemented carefully but it is needed
 - Only way to meet power budget
 - Bypass signals have been added
 - 1 signal can overtake all the others




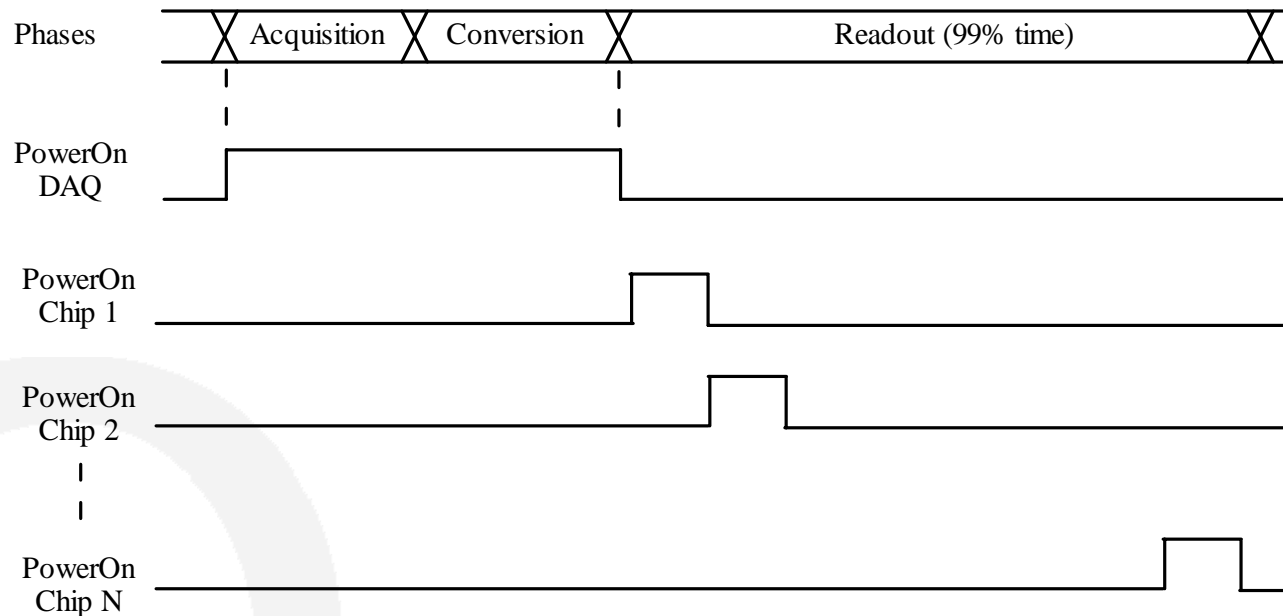- PowerON must start/stop clocks and LVDS receiver to meet power budget.




- 2 working modes :
 - Acquisition, Conversion (common to all) → managed by DAQ
 - Readout → managed internally
- Internal PowerON → OR of “PowerOnDAQ” and “PowerOnChip”

 - PowerON set during a reset phase before each acquisition



- Completely managed by DAQ
- Reset pulse > LVDS start time

 - PowerON release at the end of conversion




- Synchronized internally to properly stop clocks
- Effective PowerOn release → after max 2 ticks of Slow Clock

- PowerON DAQ is asynchronously set and synchronously release (internally in each chips)

Power On digital for Readout : 3/3




- PowerON of Chip N set by chip "N-1"

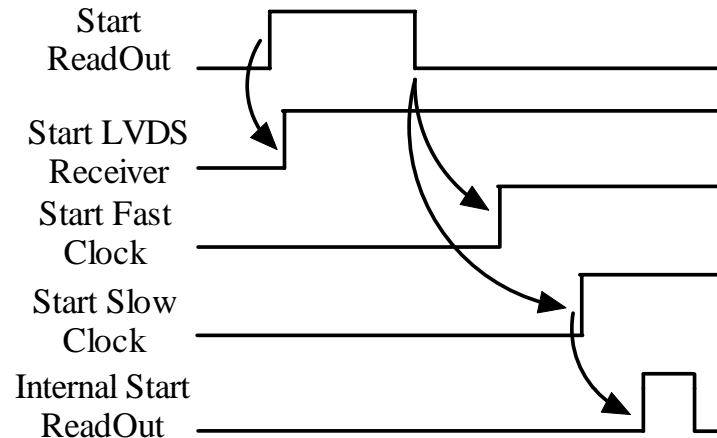

- Internally managed by ASIC
- StartReadOut pulse > LVDS start time
- Synchronous clocks start
- Internal StartReadOut starts state machine

 - PowerON release at the end of Readout of chip N



- Synchronized internally to properly stop clocks
- Effective PowerOn release → after max 2 ticks of Slow Clock
- PowerON stops LVDS and clock at the same time synchronously

- PowerON split into 2x"StartLVDS" and 2 x"StartClock"