



# SLAC ILC Damping Ring Kicker High Availability Modulator R&D Program

TILC09

April 17, 2009

C. Burkhardt, A. Krasnykh, R. Larsen, T. Tang

---





# SLAC DR Kicker Modulator R&D

- SLAC program is investigating two approaches
  - Adder topologies: array ultra-fast MOSFET switches
  - Opening switch topologies: DSRD switch
- Adder Program
  - Hybrid MOSFET/driver
    - ~1 ns switching time (FY08)
    - Improve assembly technique
    - Evaluate thermal stability
  - Investigate high bandwidth adder topologies
    - “Scale assemblies” using MOSFET/Driver hybrid switches
    - Verify preservation of pulse fidelity
    - Inspect for reflections/residual energy
- Opening Switch Program
  - Functionally similar to DSRD systems marketed by FID GmbH
  - “Open source” design
  - 2-ns prototype demonstrated (FY08)
  - Developing 4-ns modulator for ATF2

# High Bandwidth Adder Test



- Transmission line (TL) adder configuration
- Inductive isolation (alternative inductive adder configuration)
- Modules incorporate MOSFET/driver hybrid
  - 1 kV
  - 50  $\Omega$
  - ~1 ns switching time
- 5 stages
- Output
  - 5 kV (uni-polar)
  - 250  $\Omega$
- Status
  - Undergoing assembly
  - Initial results at PAC09

# TL Adder Assembly

   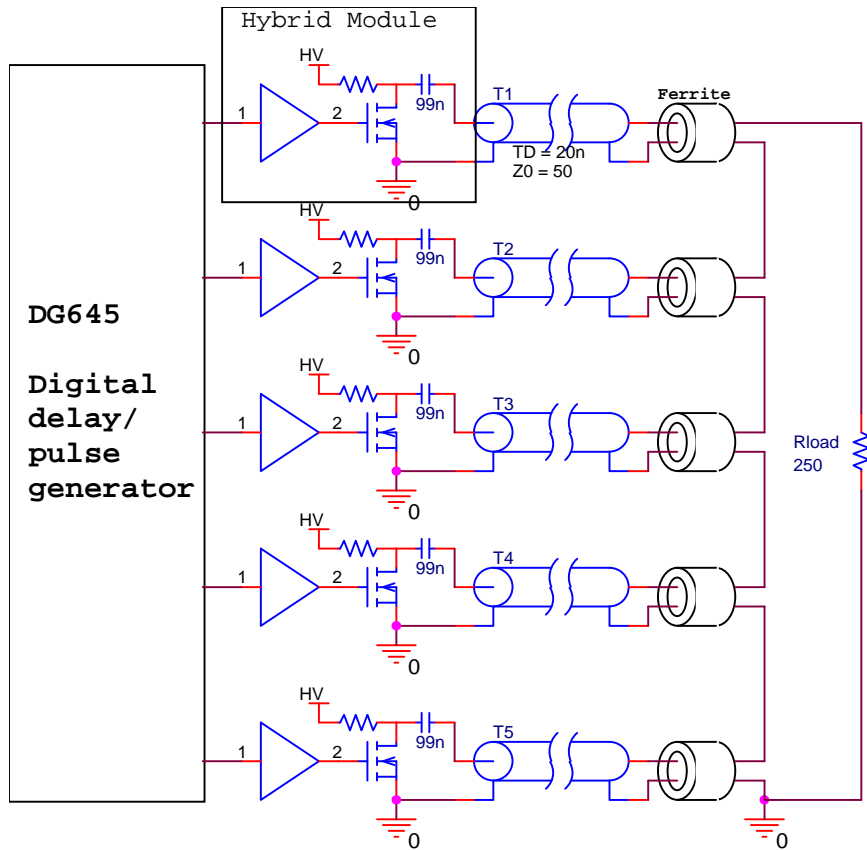


# DSRD 2-ns Prototype Tests

Amplitude	kV	4.4
Impedance of Feeder	Ohm	50
Rise Time	nsec	<1
Pulse Width	nsec	2.9


 
 


Waveform  
detail:  
1.25 ns/div

 


Pre/post  
pulse:  
20 ns/div
   
# DSRD Modulator Energy Transfer Sequence




- Voltage (left) and current of L1 during charging period (SW closed)
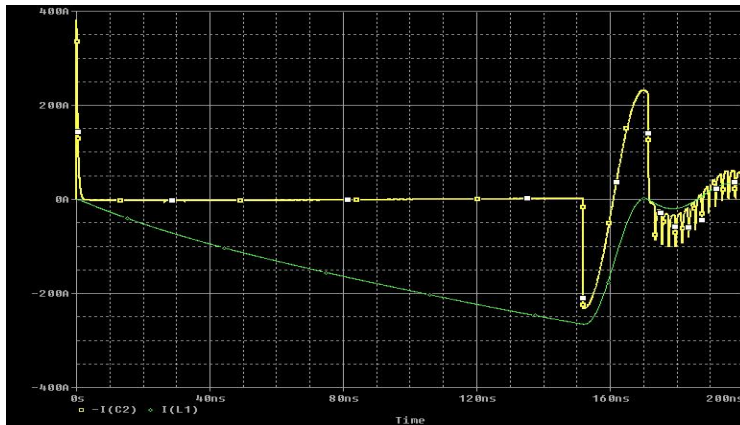
# DSRD Modulator Energy Transfer Sequence



(a)

 

(b)

(a): Current in L1 (green) and C2 (yellow) during charging of L1 ( $t < 154$  ns) and transfer to T1



(b): Detail of C2 current during energy transfer to T1 ( $t < 170.5$  ns) and discharge into load, note current through C2 until halfway through T2 discharge ( $t = 171.5$  ns)

(c): D1 current (green) and T1 current, load end, (yellow)



(c)
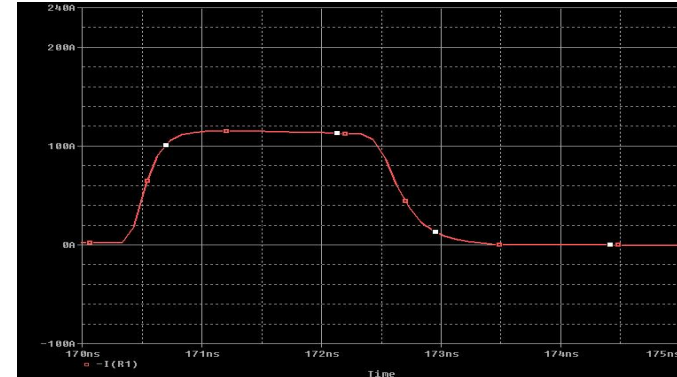 
# DSRD Modulator Energy Transfer Sequence




- Detail of D1 current (green) and T1 current, load end, (yellow) during transfer of energy to load (above right)
- Load current during discharge of T1 (above left)
- Challenges
  - Pre-pulse: finite DSRD turn-on time and forward-voltage
  - Post-pulse: residual energy will “bounce around” and come out at later time
  - Optimum timing dependent on precise DSRD properties that depend are temperature dependent



# ATF2 DR Kicker Modulator

- Parameters
  - Kicker: 60 cm, TEM, bi-polar
  - Output Voltage:  $\pm 5$  kV
  - Impedance: 50  $\Omega$
  - Pulse Length
    - Flattop: 4 ns
    - Rise/Fall Time:  $\sim 1$  ns
  - PRF
    - Burst: 3 MHz (1/308 ns nominal, 1/313.6 ns every 3<sup>rd</sup> pulse)
    - Pulses per Burst: 30
    - Burst PRF: 1.5 Hz
  - Residual Voltage:  $< 50$  V (1% of max) after 103.6 ns
- Schedule
  - Brass Board: - 4/09
  - Prototyping: - 7/09
  - Modulator: - 12/09
  - Delivery to KEK: 2010

# Circuit Modifications: 4 ns Output

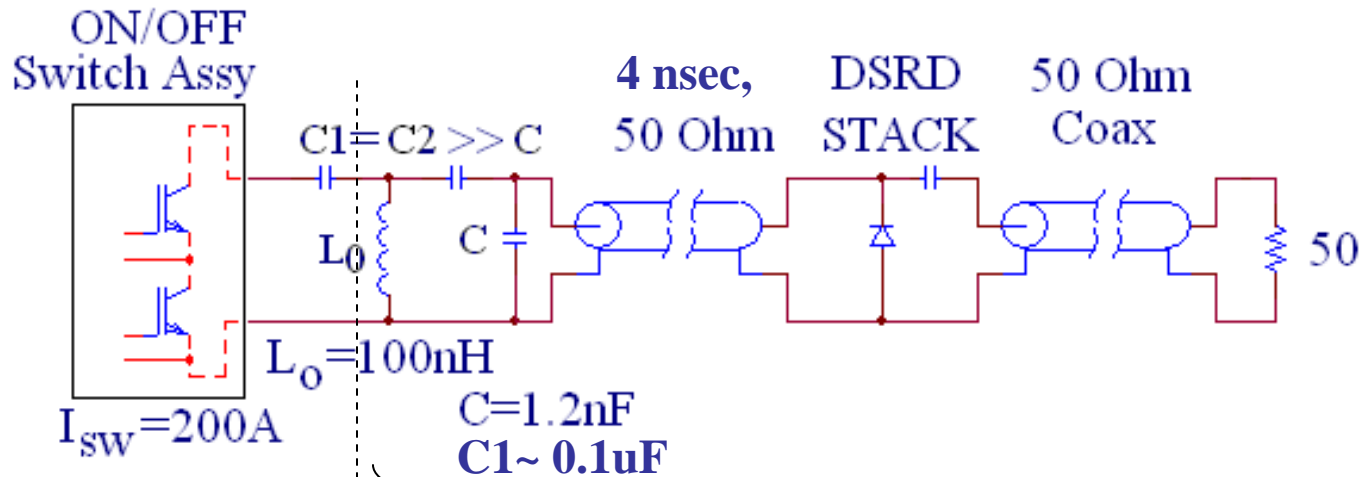

Increase TL to 4 ns, re-tune to minimize pre/post pulse

- MOSFETs Drivers
- Storage Capacitors
- Charging PS
- Array of MOSFETs in series and parallel
- Reliability of Switch Assembly

# Recent Progress

- T. Naito visit to SLAC
  - ATF2 parameters
  - KEK participation
- Derived circuit parameters for 4 nsec flattop circuit
- Developed series MOSFET switch for HV pump
  - Opto-coupled trigger (floating deck)
  - Transformer coupled trigger
- Acquired key components



# Summary

- Adder Program
  - Ultra-fast switching: hybrid circuit achieves fundamental MOSFET limit w/ excellent control
  - Scale adder system under assembly
  - Test results during Q3 (PAC09)
- DSRD Program
  - Promising results with 2 ns prototype
  - Purchased optimized DSRDs and other required components
  - Focusing on higher power pump development
  - Prototype development Q3/Q4