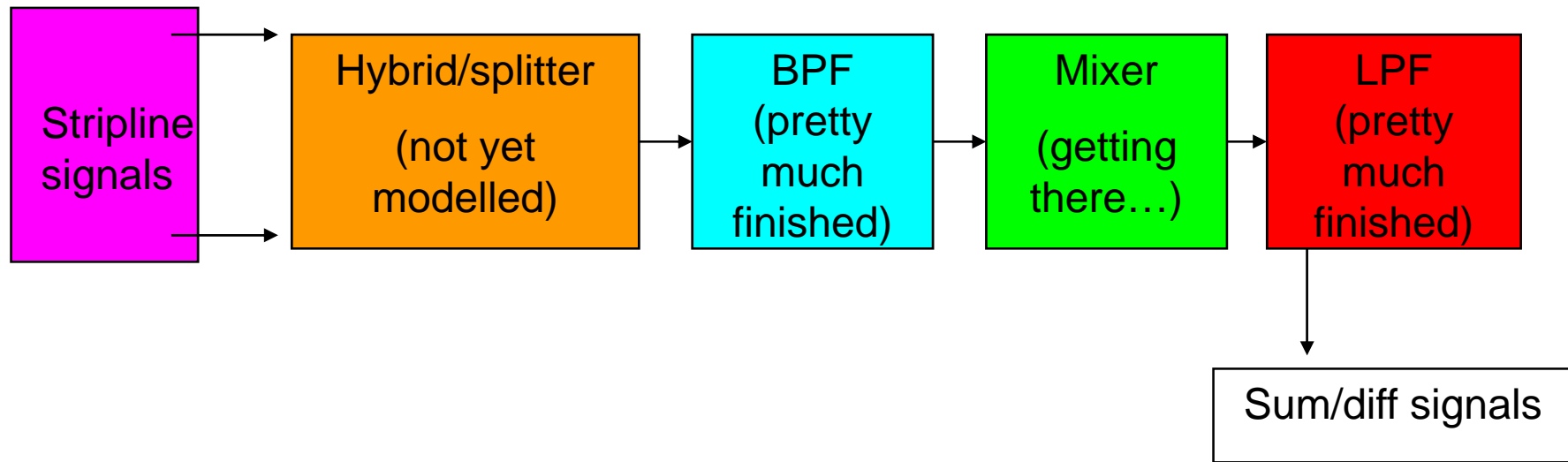


BPM processor simulation update


Robert Apsimon

09/01/09

Basic processor layout




BPF

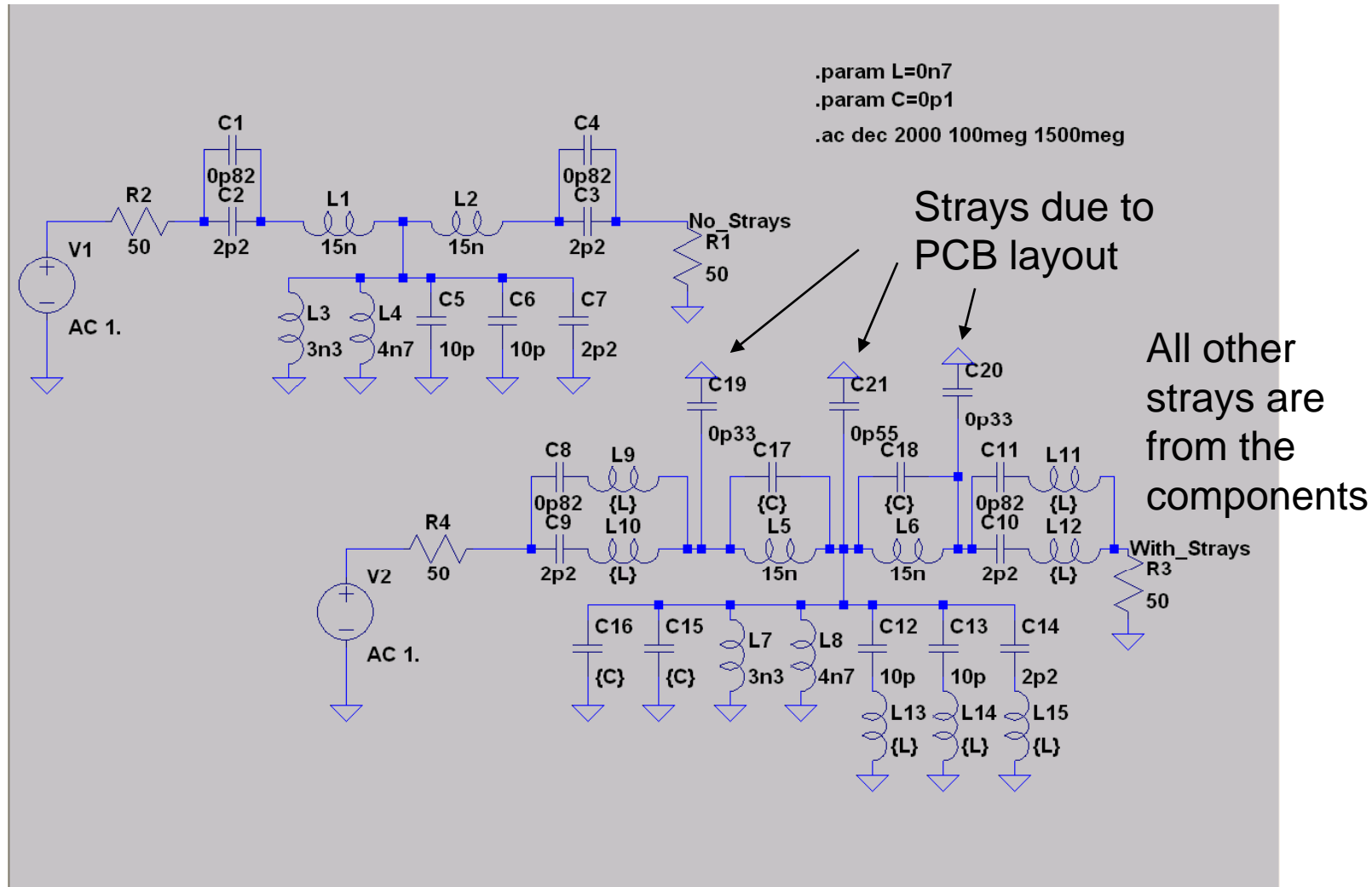



Strays due to PCB layout

All other strays are from the components

BPF

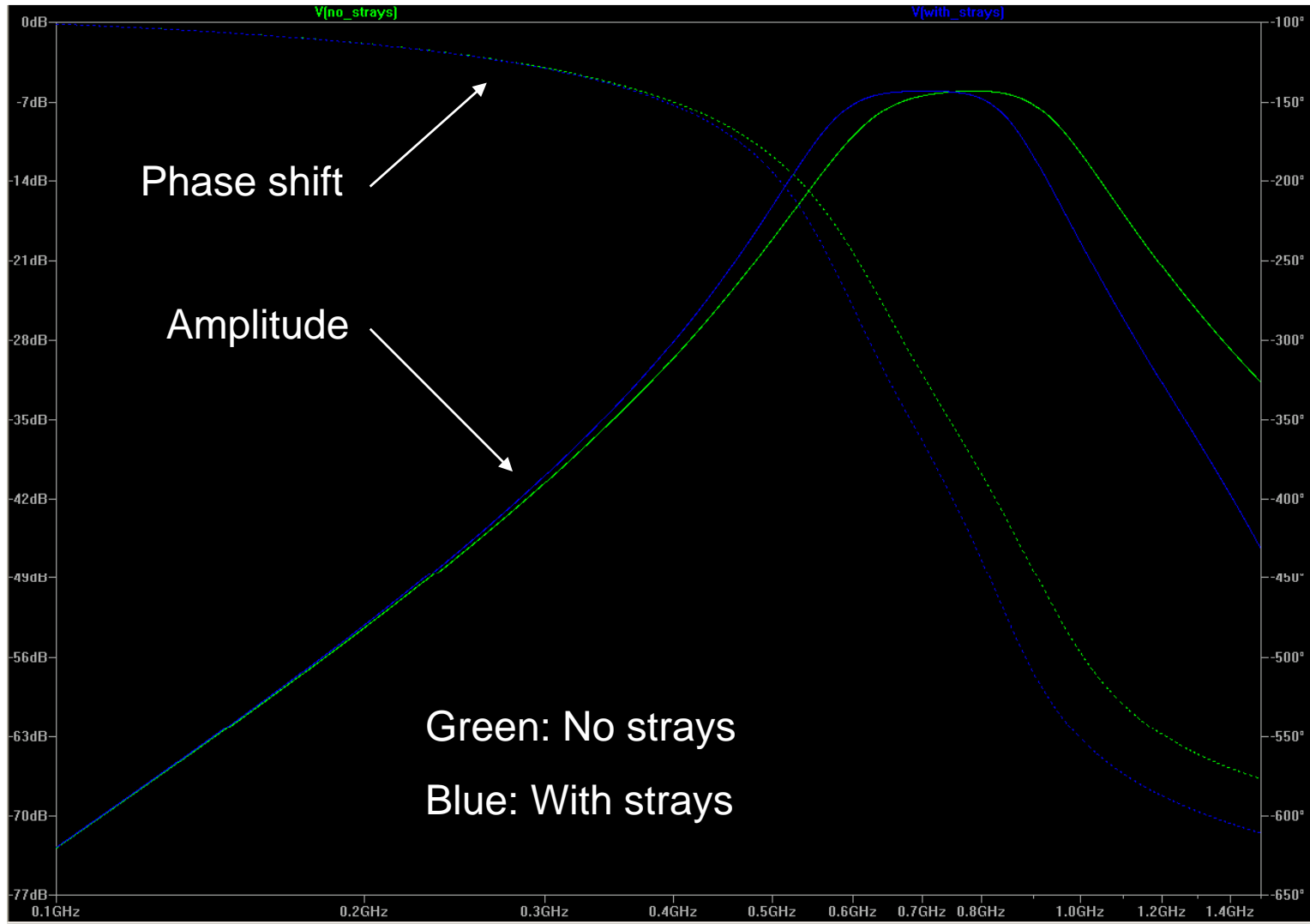


LPF

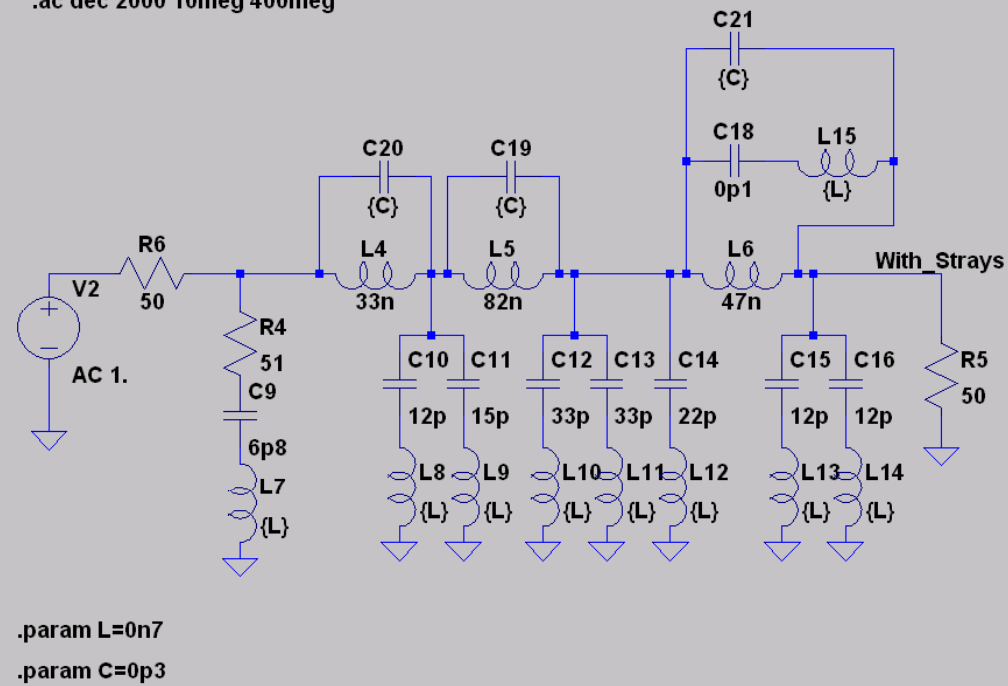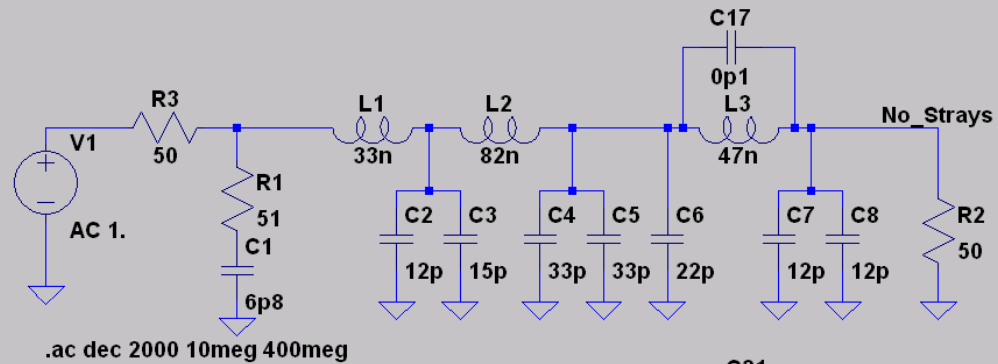

Effect of strays small, so haven't considered strays due to PCB layout


LPF

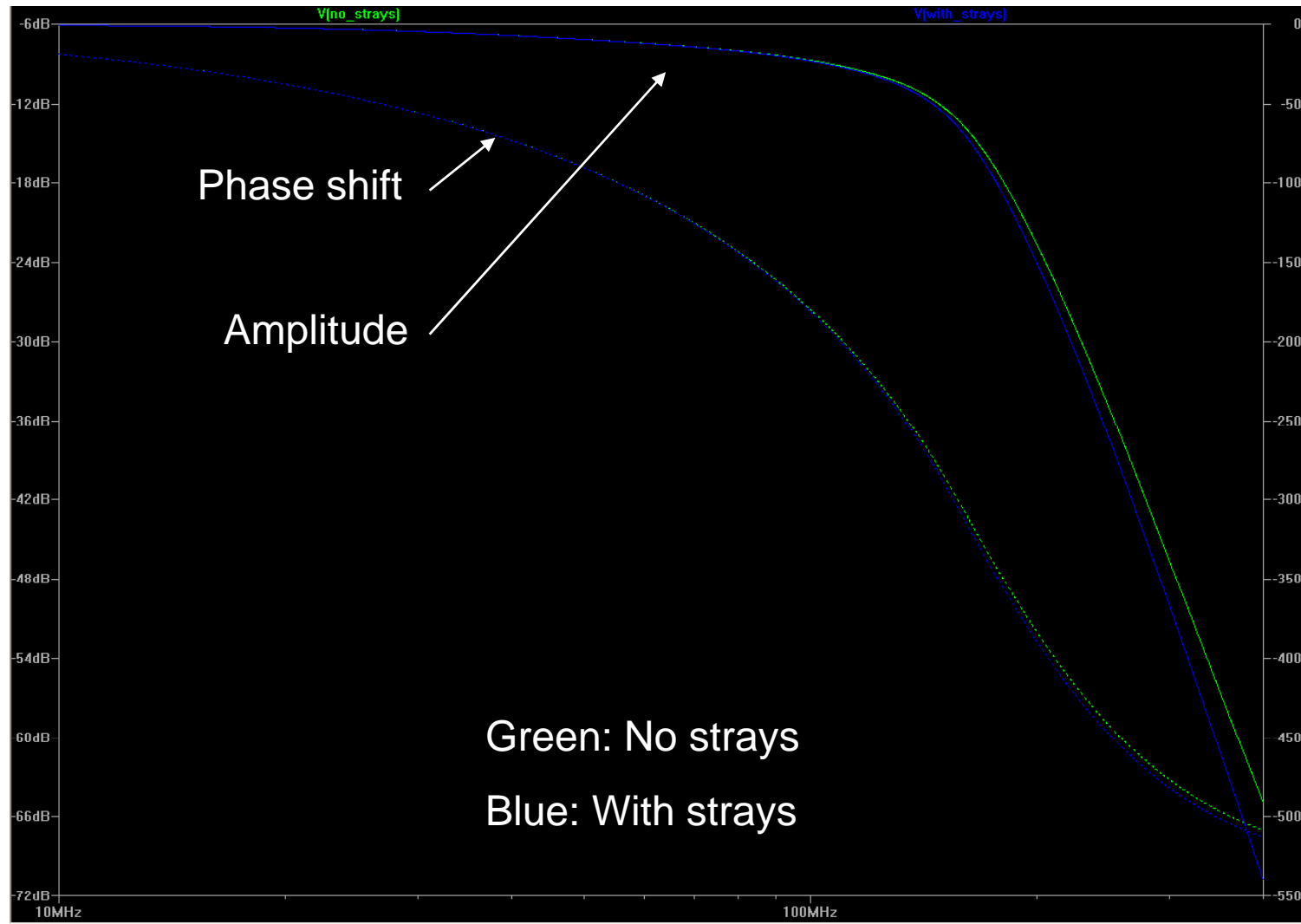


Mixer-linearity study

- Plotted RF input amplitude vs. mixer output amplitude for 2 diode models and an “ideal” mixer
- Ideal mixer is RF signal multiplied by LO signal

Mixer-linearity study

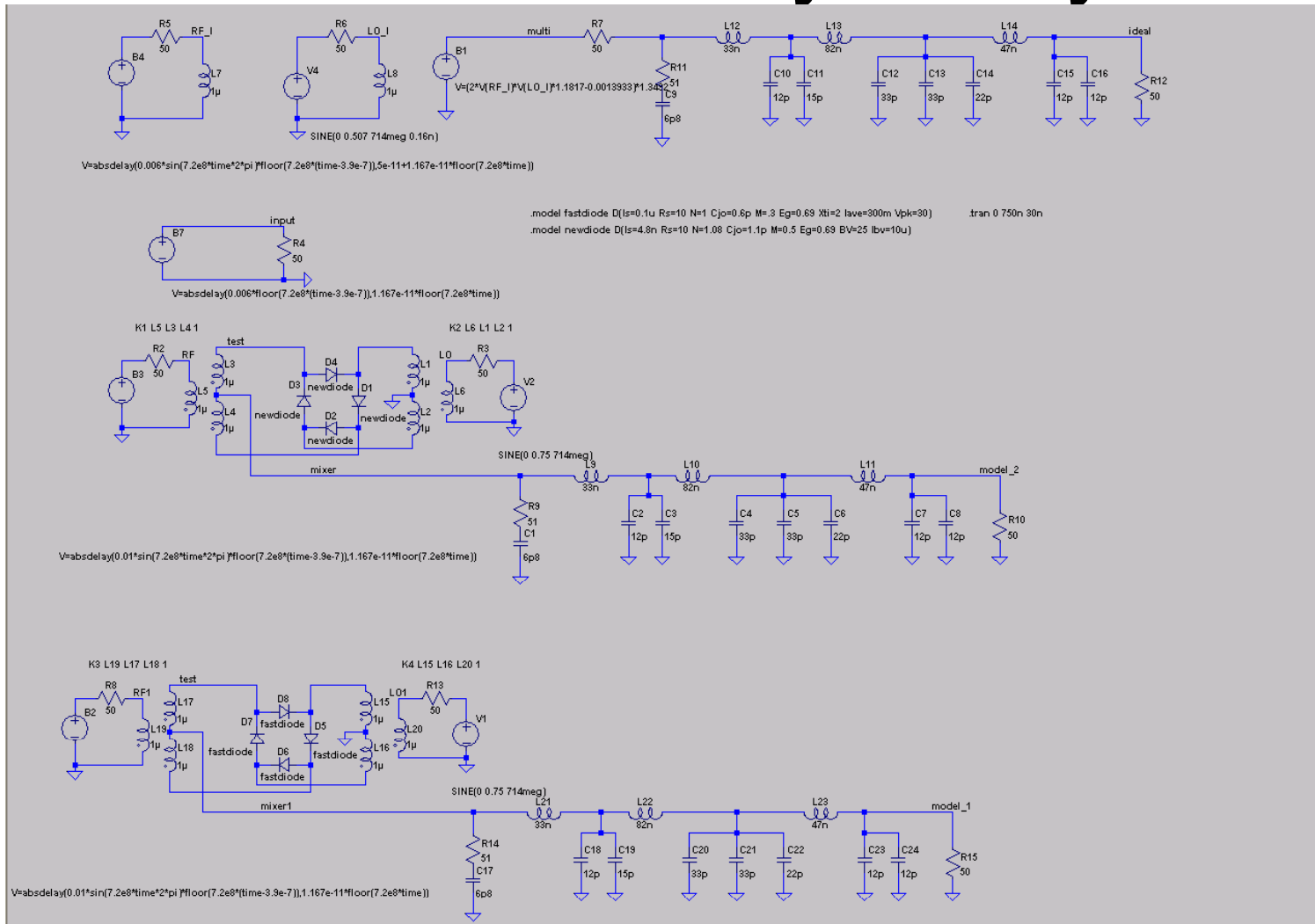


Mixer-linearity study

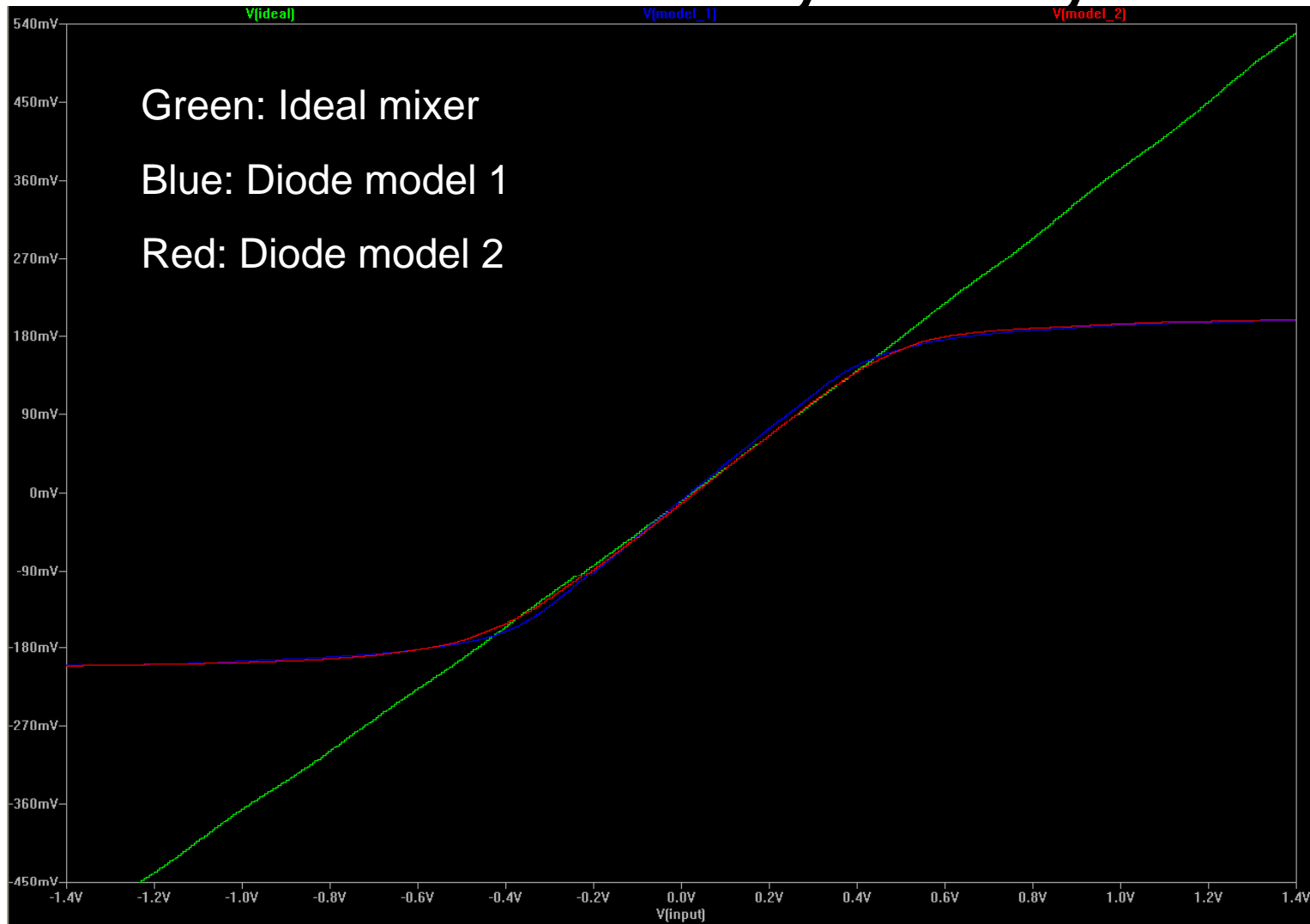


Mixer-impedance study

- Input impedance
 - Divide voltage across input inductor by current passing through it for RF and LO ports
 - Measured input impedance for both maximum and minimum voltage and current for the two diode models, as shown on next slides...


Mixer-impedance study

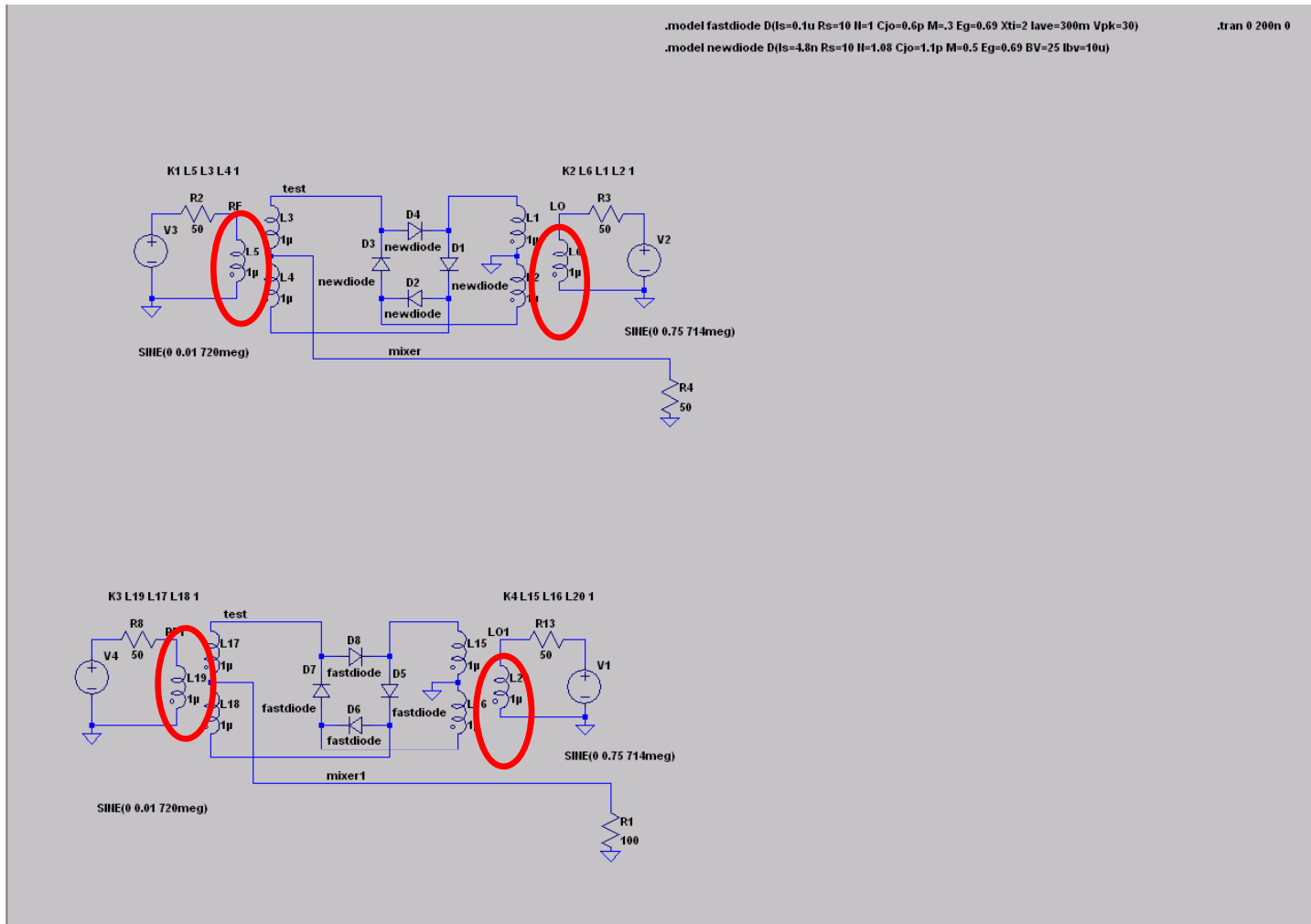


Mixer-impedance study

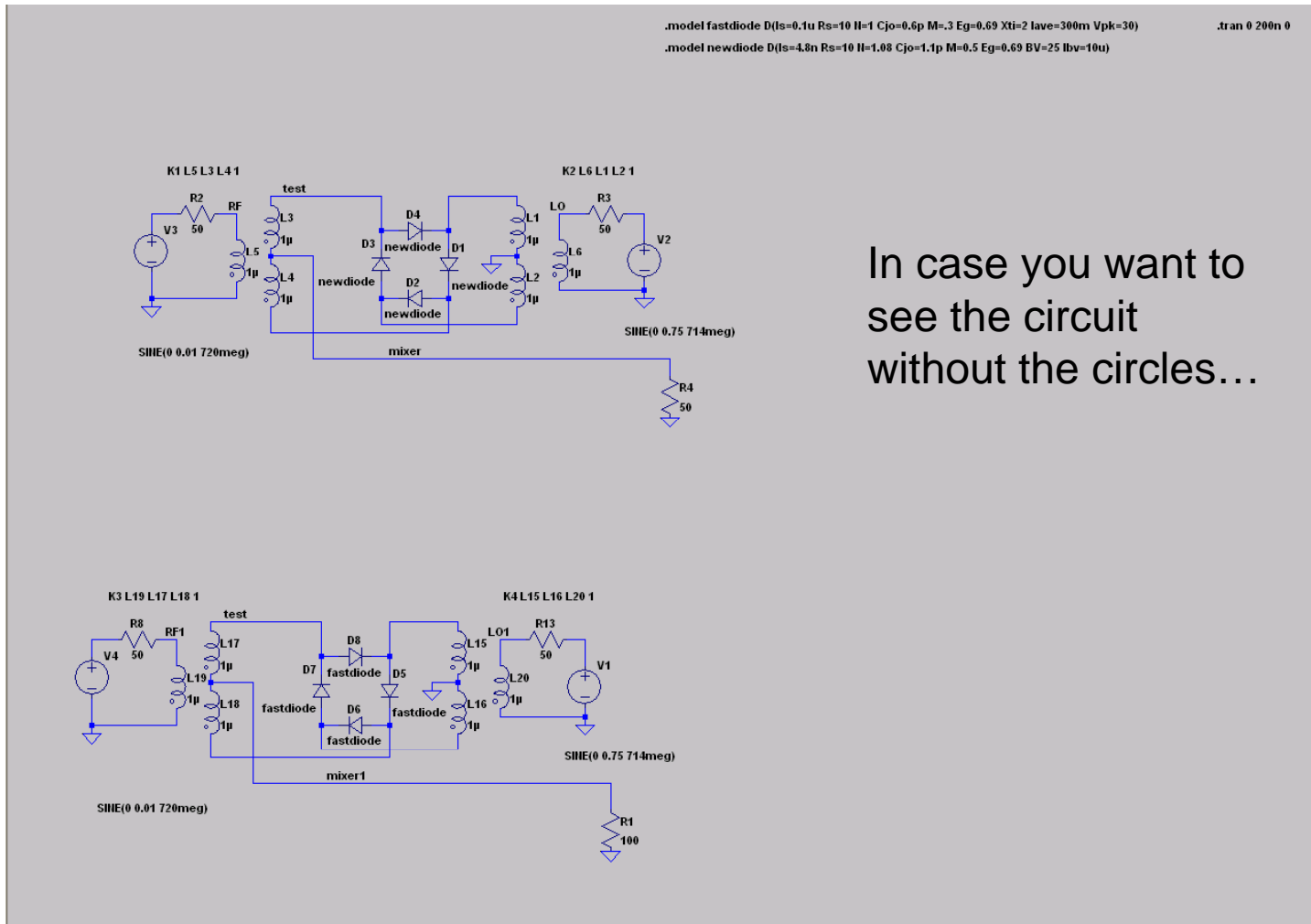

Mixer-impedance study

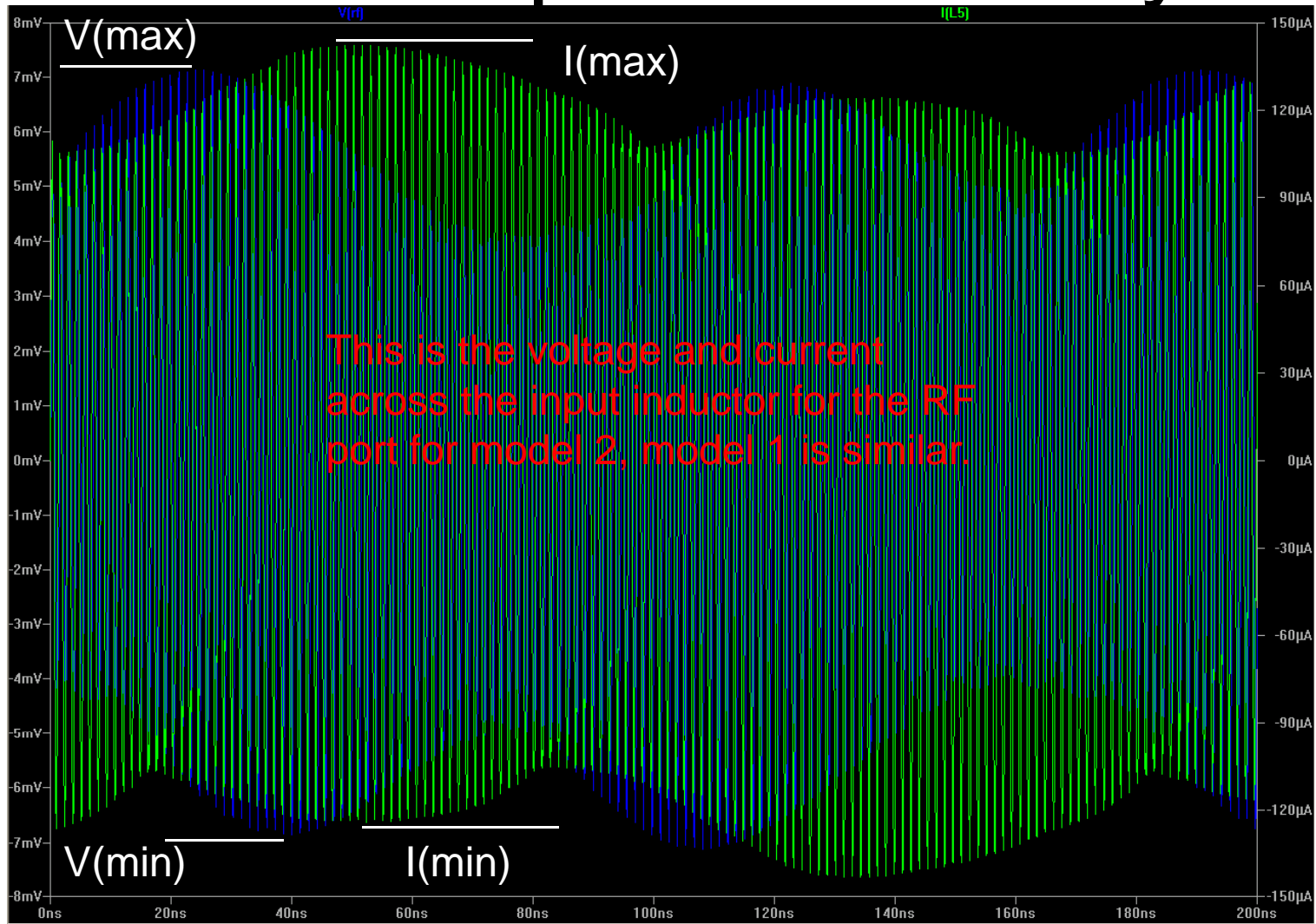


Mixer-impedance study

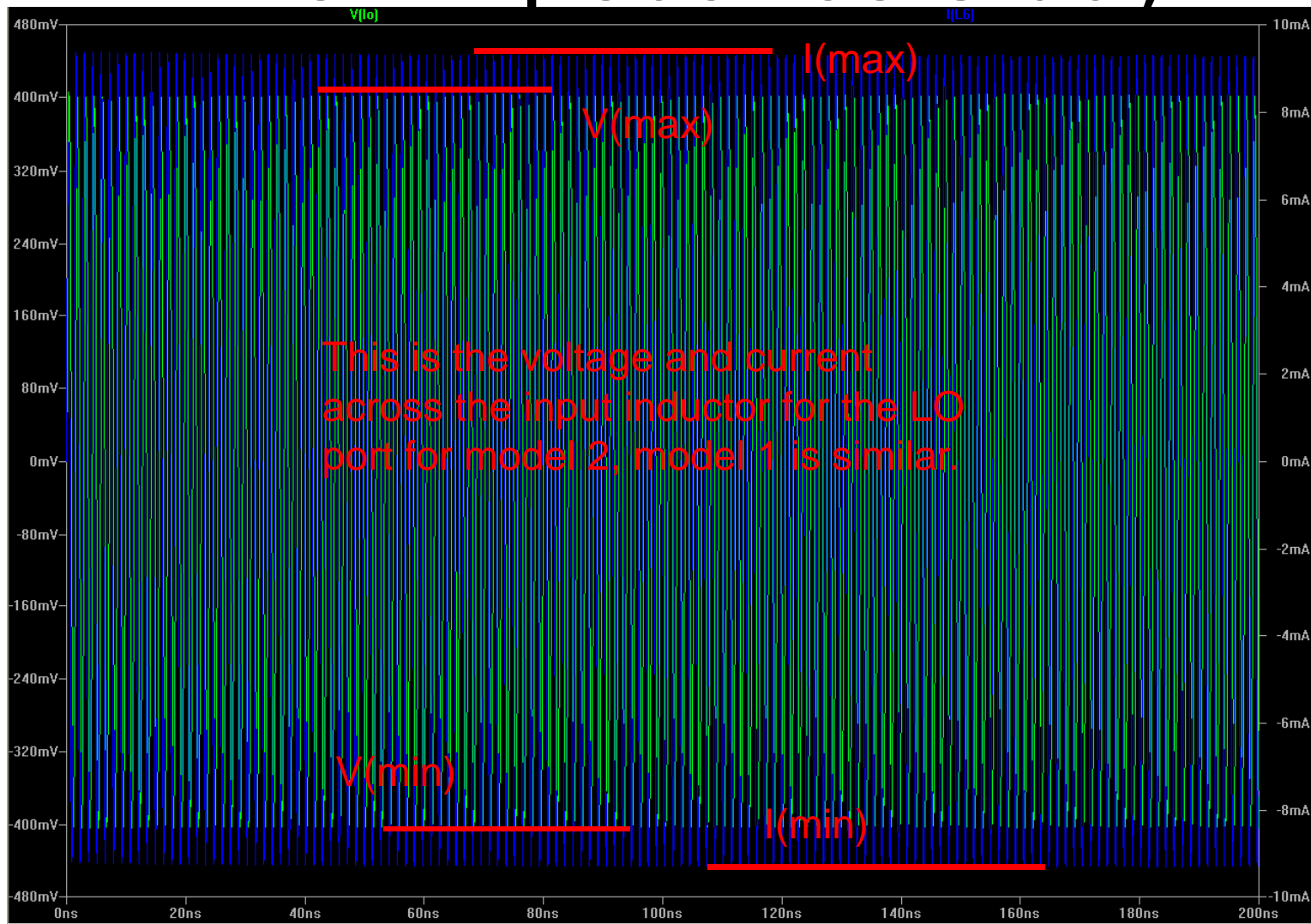


Mixer-impedance study

- Output impedance
 - Assume mixer is a device with some impedance across is (maybe too simple...)
 - By measuring output voltage across 2 different termination impedances, one can determine Z_0 .
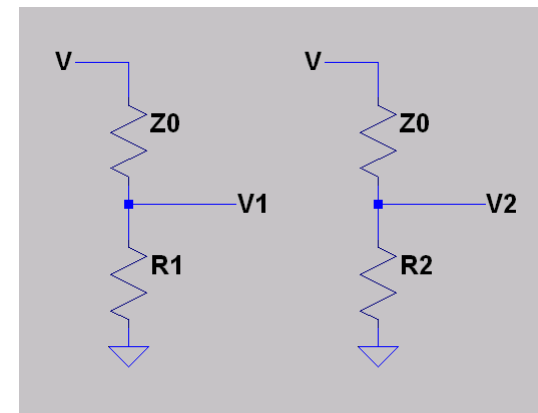
$$Z_0 = \frac{R_1 R_2 (V_2 - V_1)}{V_1 R_2 - V_2 R_1}$$



Mixer-impedance study

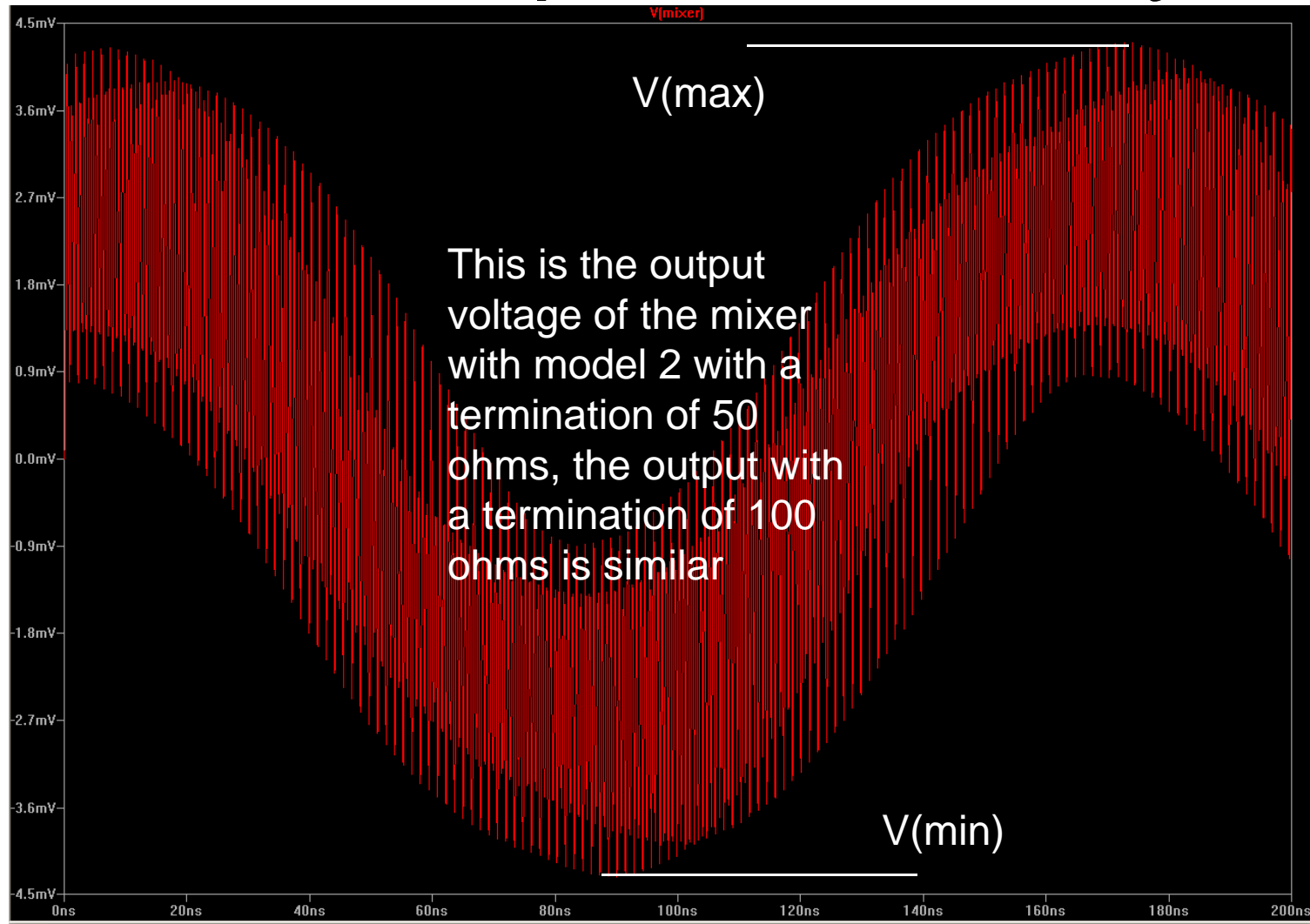

Mixer-impedance study

- $VSWR = Z_0/Z_L$
- The following results should be taken with a rather large pinch of salt...

Impedance measurements

	Input impedance RF		Input impedance LO		Output impedance		VSWR RF		VSWR LO	
	max	min	max	min	max	min	max	min	max	min
Model 1	61.56	58.57	36.02	37.19	30.53	29.28	2.016	2	1.18	1.27
Model 2	49.94	55.63	42.93	43.54	16.14	15.78	3.094	3.525	2.66	2.76
Data sheet	~50		~50		~50		1.34 - 1.4		2.04 - 2.13	

Max and min mean that the impedance or VSWR were calculated using either $V(\max)/V(\min)$ and $I(\max)/I(\min)$