Comprehensive KLauS measurements & other issues

Wei Shen
Universität Heidelberg
CALICE Meeting, Matsumoto



outline

- KLauS reminder: channel diagram
- Steady state characterization:


 DAC, dynamic range scan, trigger ...
- Power Pulsing


 noise, spectra quarlity
- Other issues

Reminder: KLauS channel

12 channels in AMS Sige 0.35um


Designed in Nov. 2010

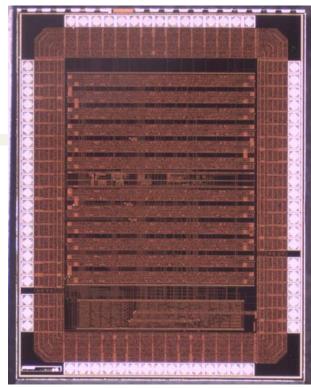

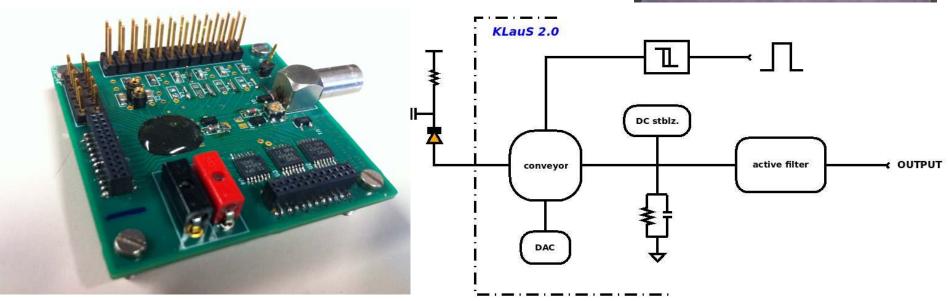

Input Digital to Analog Converter


Input voltage DAC

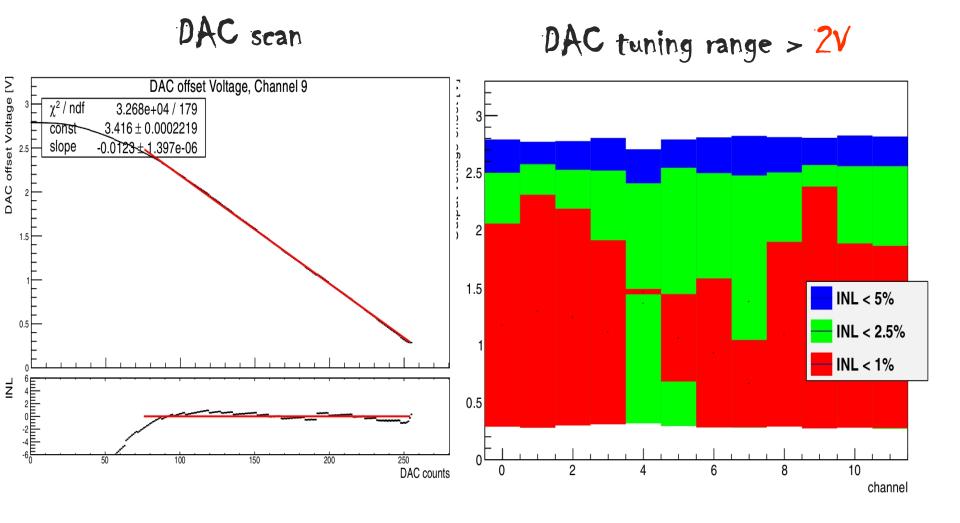

Input voltage DAC, linearity and slope





Channel slope uniformity

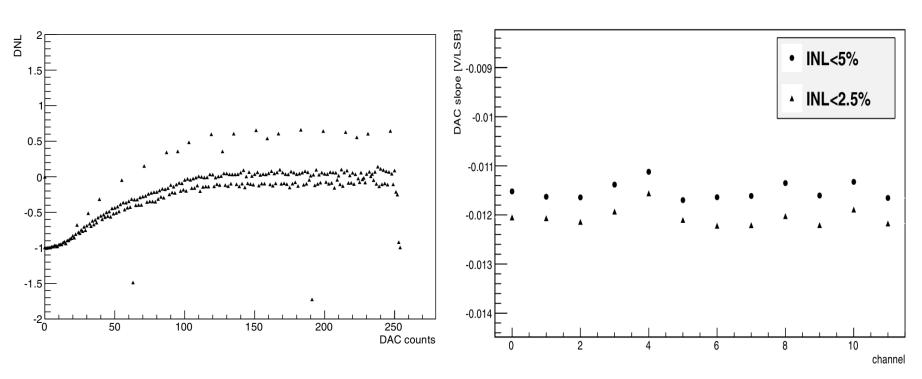


a Convertion factor

Input Stage and Q collection

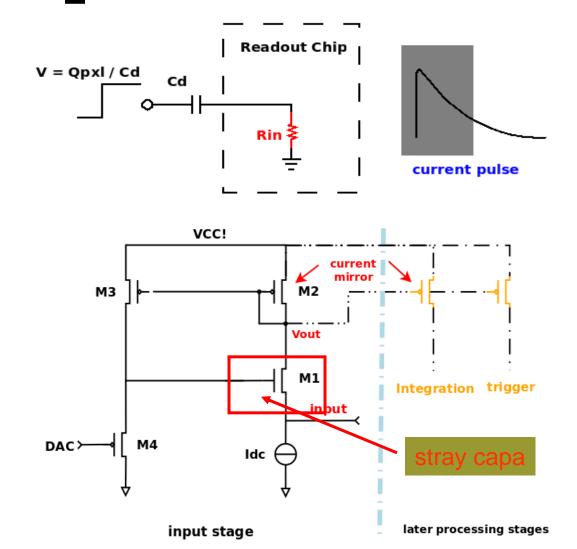

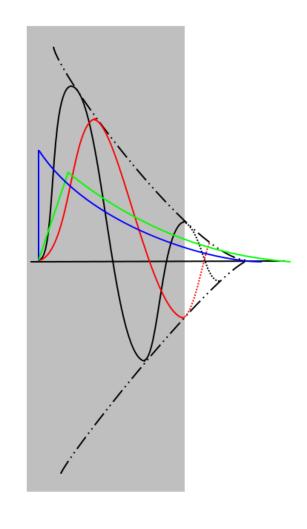


a convertion factor

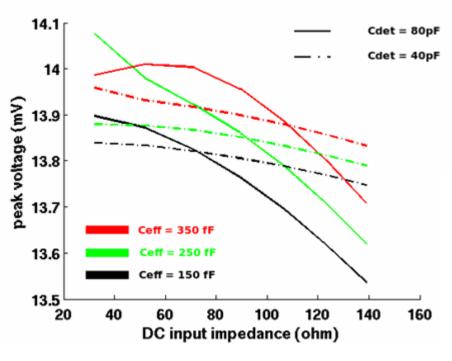

a convertion:

Cdet, stray capa, input impedancee




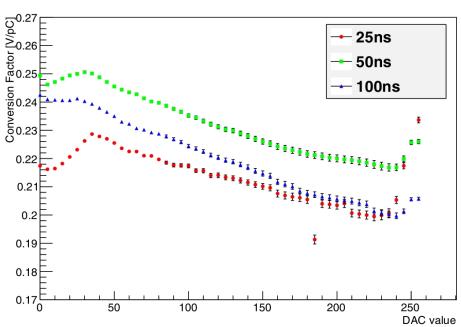


Gain factor and uniformity

Gain factor scan


3 gain setting
(Scalling down)

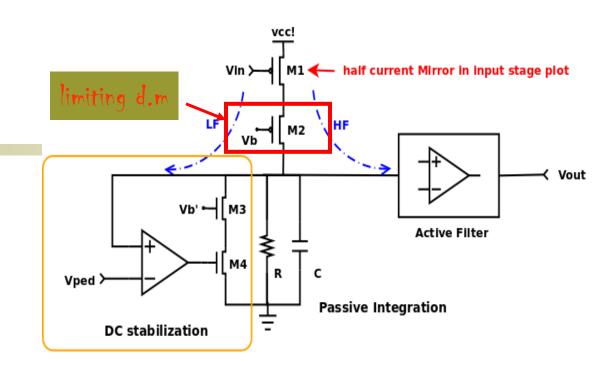

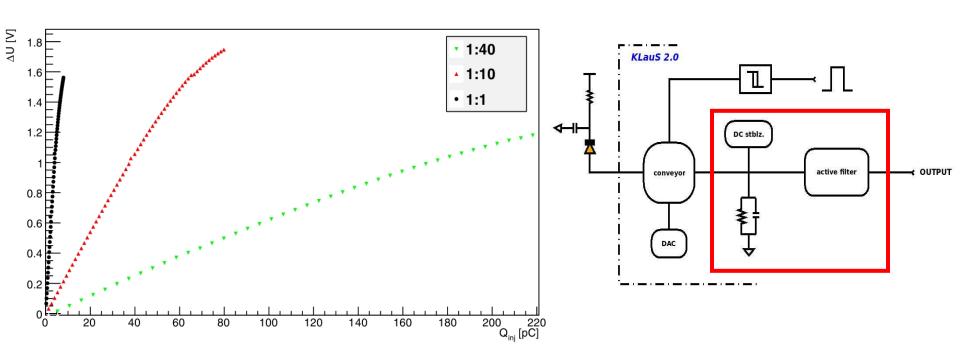

Gain uniformity

12 channels, gain uniformity (DAC 100)

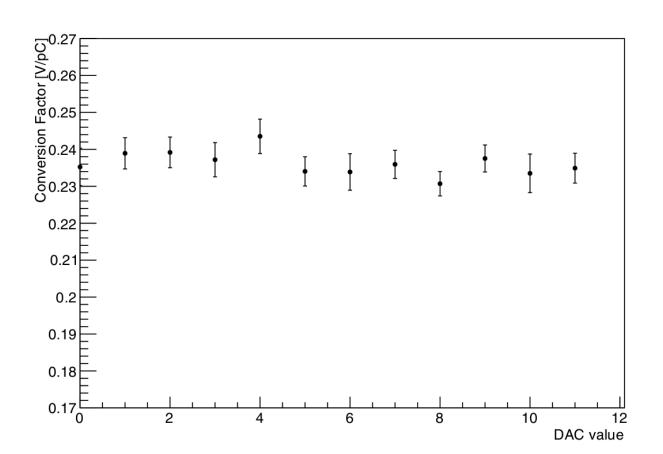


Trigger Quality


Threshold Uniformity & Trigger noise

M.I.P resolution: 50ps (1/4 Mio.), 13 ps (1 Mio.)


Threshold Uniformity

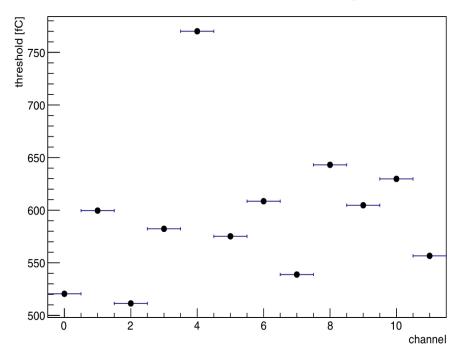


Trigger noise for 12 channels

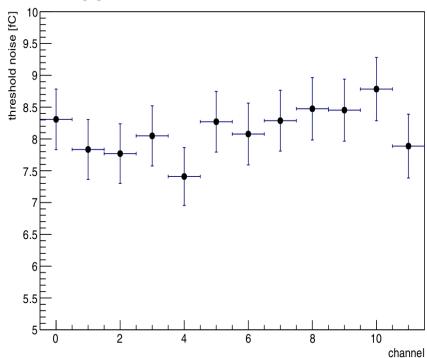


Power Pulsing

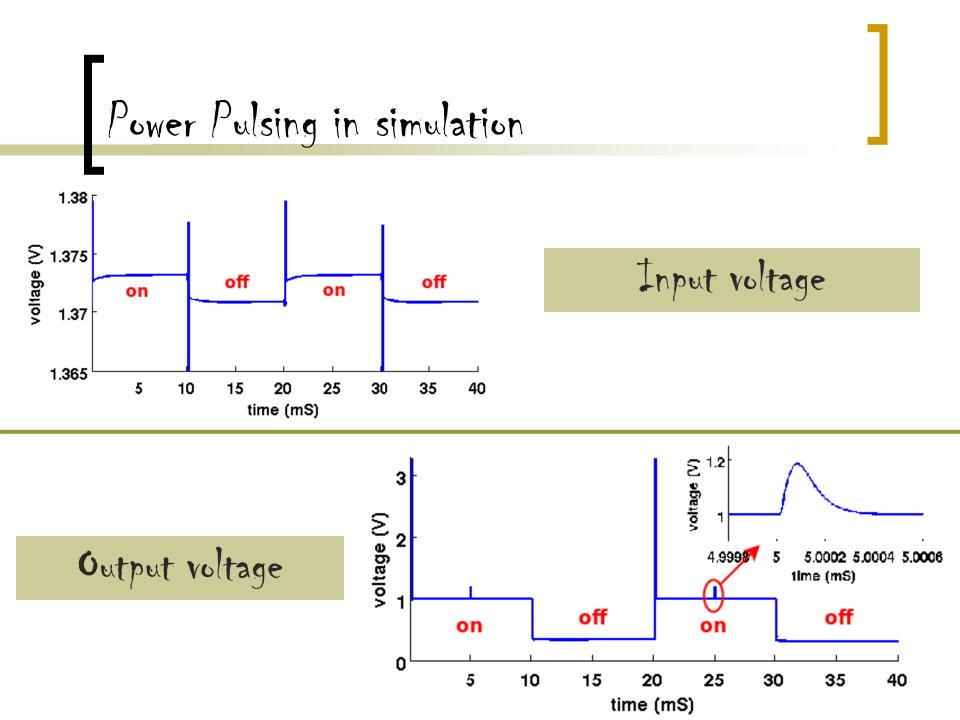


Power Pulsing (i) - recovery time

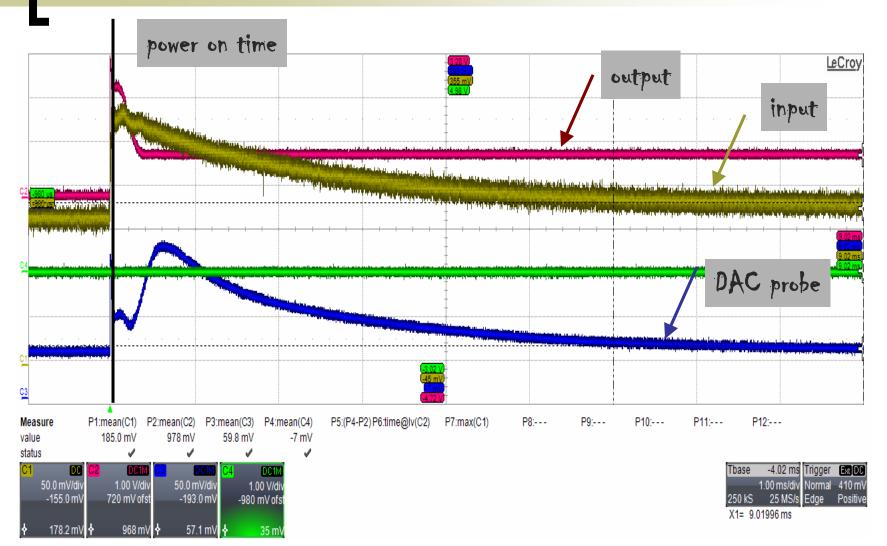

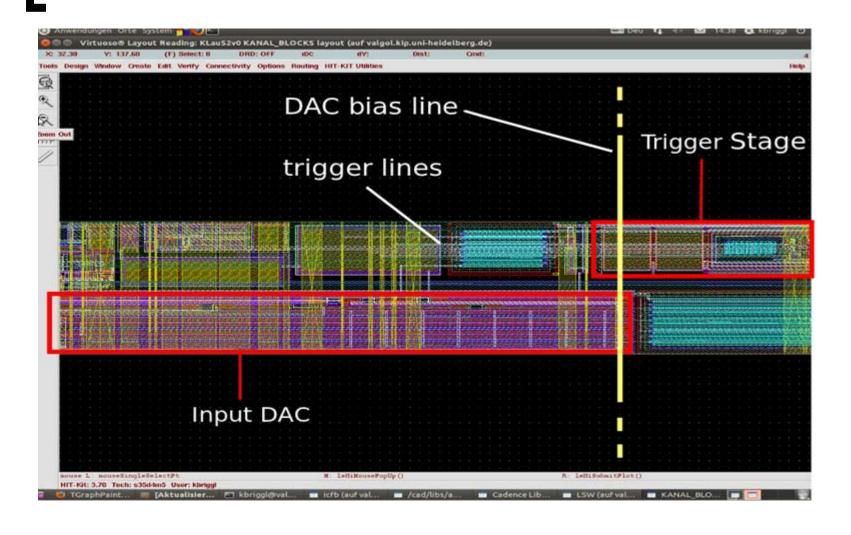Power Pulsing (i) - recovery time, layout




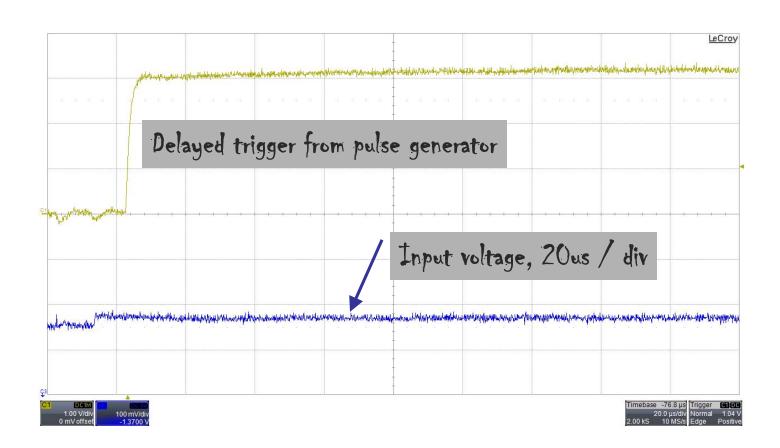Power Pulsing (i) - recovery time, trigger off




Power Pulsing (ii) - Vin offset

"OFF" state

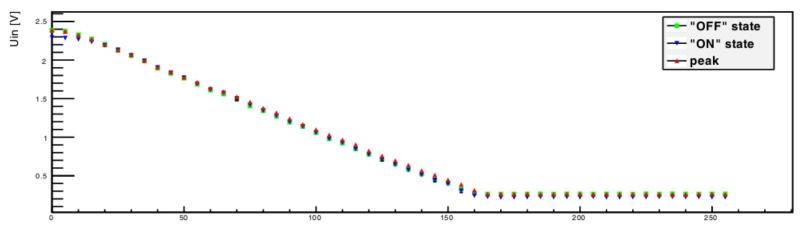


"ON" offset substracted

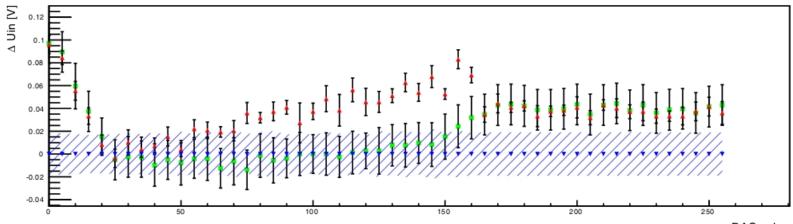

DAC value

Power Pulsing (iii) - noise

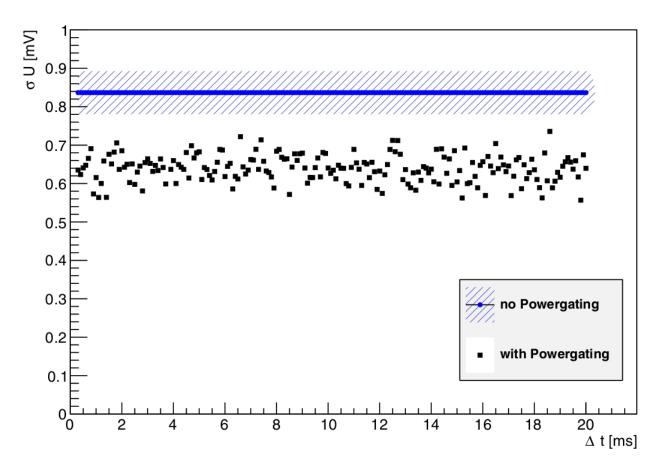Noise aliasing effects confirmed, noise vs measurment time




Pixel SNR

MPPC 1600 (1/4 Mio.) ~ 15


MEPHI SIPM (1 Mio) ~ 60

Power Pulsing (iv) - SiPM spectra

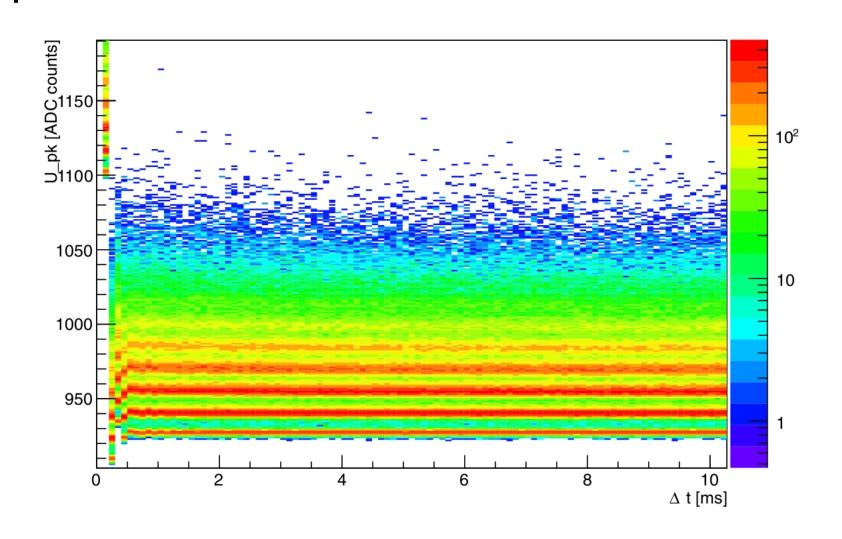


Power Pulsing (iv) - SiPM spectra

MPPC s10362-11-1600 (1/4 Mio. Gain)

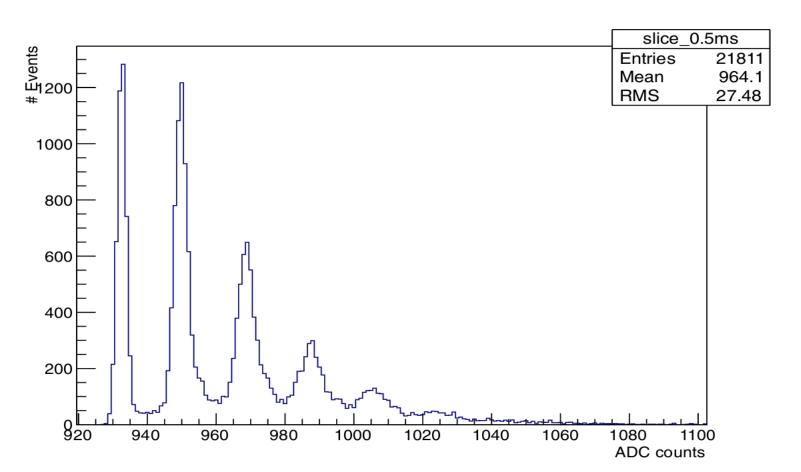

Power Pulsing (iv) - SiPM spectra noise


circles are power pulsing results

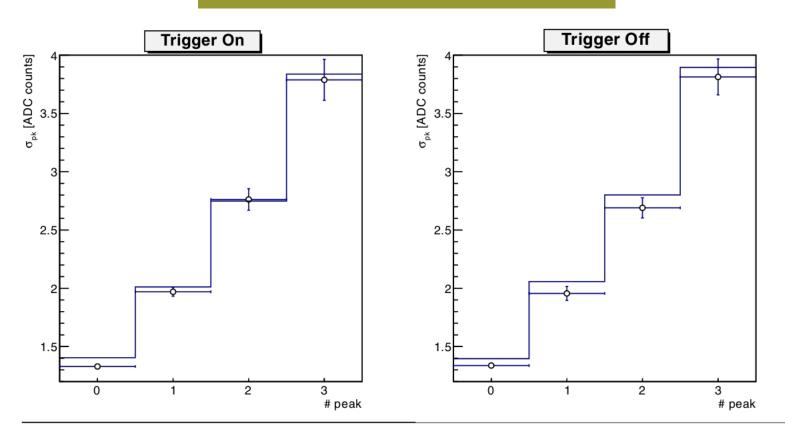

Remaining Issue


Process variation caused issue

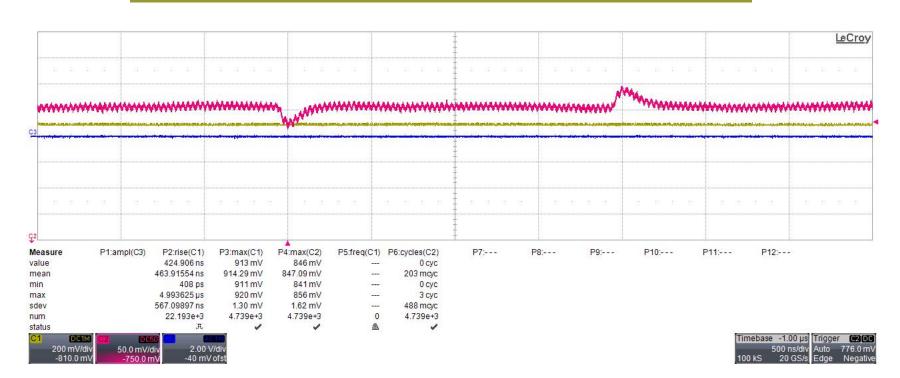Instability in a few channels for a few detectors



Process variation: reason & remedy

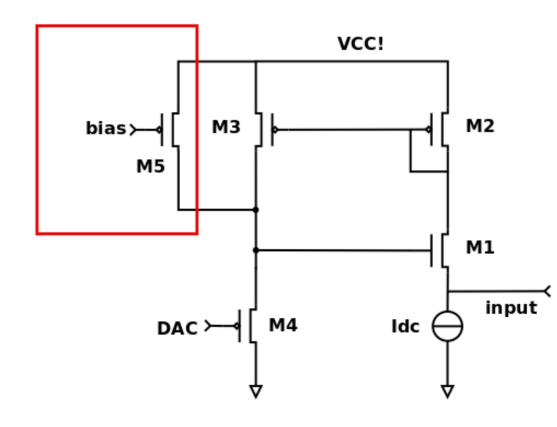- Input impedance becomes negative
- $= \frac{1}{gm_1} \frac{1}{gm_2} + \frac{1}{gm_4}$
- PMOS outweighs NMOS
- Compensation path



Summari

- KLauS characterization finished
- Power pulsing works successfully
- 3 issues to be modified in next version cascode votage to enhance dynamic range DAC layout input stage compensation
- Ready for integration into new SPIROC