

Pipelined SAR ADC for SiPM readout

Tobias Harion

Kirchhoff Institut für Physik
Universität Heidelberg



Outline

- Motivation & Requirements of the ADC
- ADC structure
 - Track / Hold, SAR ADC, etc...*
- Parameter Calculation and Estimation
- Summary & Time Plan

Motivation and Requirements

- Quantization (one ADC per channel):
 - charge integration
 - timing voltage ramp
- Resolution - **12** bits ? - **SiPM Optimization**
 - 3** different types of signal to quantize:
 - calibration signal, only a few pixel fired
 - physical MIP-like signal, large fluctuation
 - timing voltage ramp

Resolution Requirements

- **Calibration signal**

- i. clearly separated peak - **1 mV** electronic noise - **12** bits
- ii. up to **10** pixels, range of $\sim 300\text{mV}$ (small range)
- iii. only a small portion of the total signals

- **Physical signal - Much larger uncertainty - Less resolution**

- i. large fluctuation due to Landau Distribution
- ii. signal uncertainty due to the detector pixel uniformity
4-5mV (15 pxls , MPPC 50um pitch device)
- iii. most time, **8 bits** sufficient - Quantization noise (**3.7mV**)

- **TAC ramp signal**

- i. same ramp speed by SPIROC
- ii. 10 bits - 400ps bin size - $< 100\text{ps}$ quantization error
- iii. if **ns** resolution sufficient, only **8 bits** required

Requirements


- Resolution : **8 bits** for most of time
12 bits for calibration only (shortly)
10 bits necessary for precise timing

Other Requirements

<i>Performance</i>	<i>Parameter</i>
<i>Area</i>	~ 100μm * 700 μm
<i>Sampling Rate</i>	> 1 MHz
<i>power</i>	μW w/ pulsing
<i>SNDR, SFDR</i>	descent


ADC Structure

 - 8 bits low power (!) , small size ADC, **SAR** is the perfect choice
- sampling rate easily exceeds **1 Mhz.**
only **μs** needed for analog memory, less distortion
- the **extra 2 bits (10bits)** required by timing can be **pipelined**
- the additional **2 bits (12bits)** can be **cyclic (only shortly)**




Peak Sensing - Track/ Hold

 Peak sensing using a **peak detector and holder (PDH)**




 Peaking time is input pulse shape dependent, easier to control with PDH



Memory capa can be merged to SAR capa

Succussive Approximation Register ADC

 


In order to counteract the Mismatch Error and Nonlinearity

According to the AMS datasheet, the minimum of unit capa is $7\mu\text{m} \times 7\mu\text{m}$, at the moment $10\mu\text{m} \times 10\mu\text{m}$ is chosen

The capa total size is $100\mu\text{m} \times 32\mu\text{m}$,
Memory Depth of 4, $100\mu\text{m} \times 150\mu\text{m}$, **very small in size**

Simulation for the 8b SAR

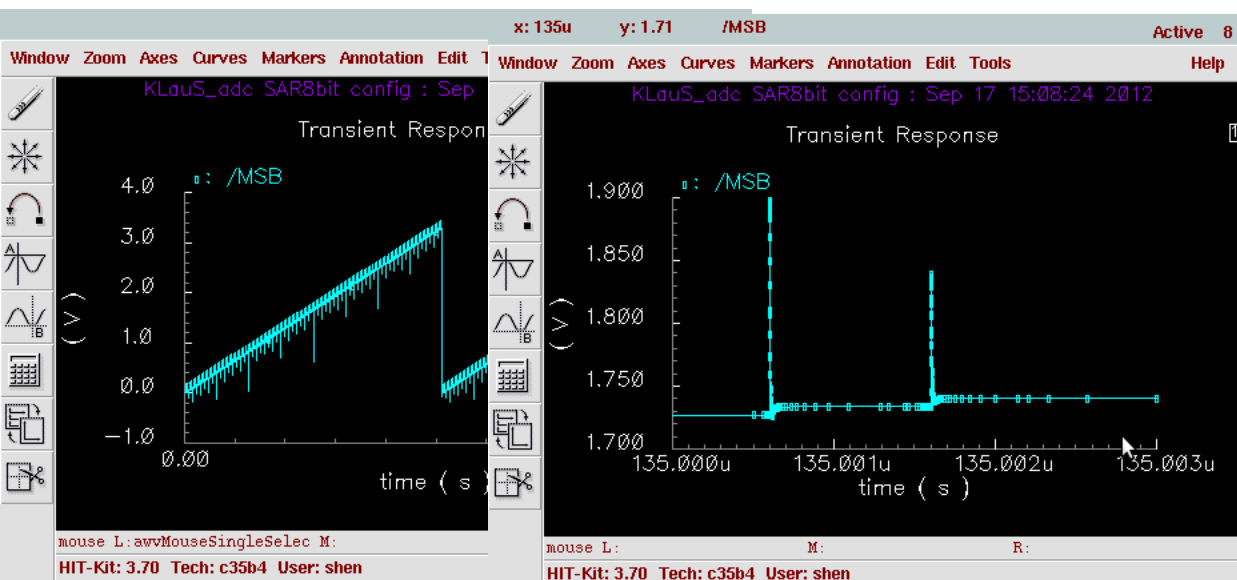

8 bits Scan MC
DNL/INL < 0.5 LSB

Zoom of each step,
response fast enough

Summary

- SAR ADC structure chosen
- 8 bits for physical signal, 10 & 12 bits can be pipelined
- Size estimation $100\mu\text{m} * 600\mu\text{m}$
- Pulsed power consumption μW
- Design started, Tapeout estimation Apr. 2013