



Front-end Chip: From CMOS 180nm to 130nm

- Introduction
- Circuit in 180nm technologies
- Challenges in 130nm technologies
- Circuit architecture
- Perspective


Introduction

- Encouraging result from front-end in 180nm CMOS
 - Design the new front-end chip in 130nm process
 - Less on- Si detector material, less parasitics, less power

  Front-end Prototype chip in 180nm technologie



17 channels (one test Channel)

 

1. Low noise amplification
2. Pulse shaper
3. Sample and Hold
4. Buffer
5. Comparator

Results in 180nm

Preamp Results


- Gain: 8mV/MIP OK
- Dynamic range: 50 MIP OK
- Linearity: +/-1.5% expected: +/-0.5% -
- Noise @ 70 μ W power, 3 μ s-20 μ s rise-fall times:
498 + 16.5 e-/pF 490 + 16.5 e-/pF expected OK

Pulse Shaper results


- Peaking time: 2-6 μ s tunable peaking time vs 1-10 expected -
- Linearity: 6%, 3.5% expected -
- Noise @ 3 μ s shaping time and 70 μ W power:
325 + 10.1 e-/pF vs 274 + 8.9 e-/pF expected OK

Results in 180nm

- Process spreads: 3.3%

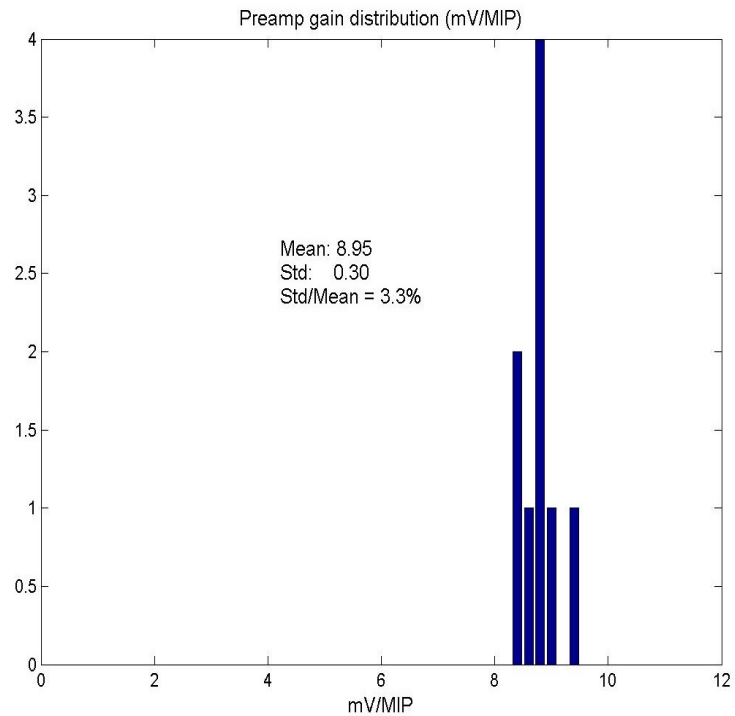

Preamp gain distribution

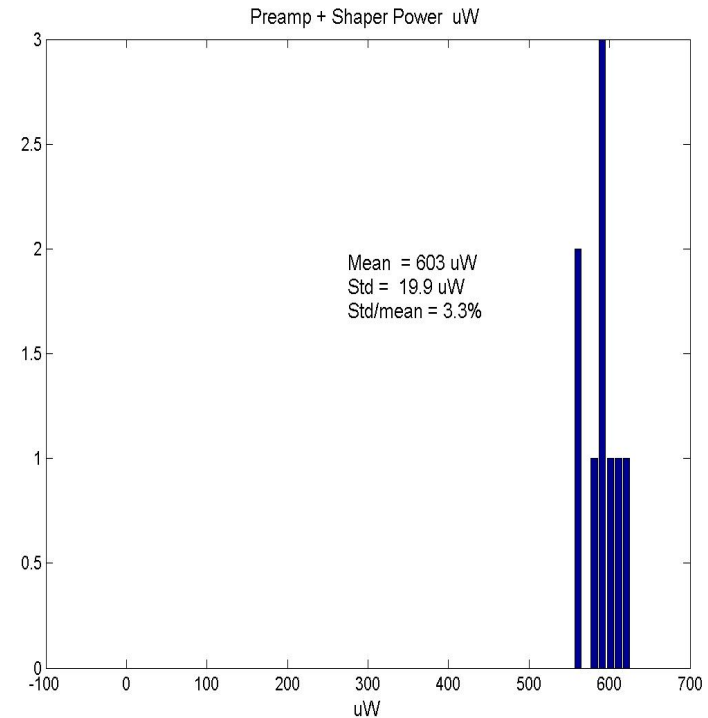

(Preamp + shaper) power distribution

Front-end in 130nm

Cooperation between LPNHE and LAPP Annecy

Why 130nm ?

VLSI

Will be dominant in industry in the next few years

Faster

Low power

But, it is also more difficult for low noise analog design

Technologies parameters

180 nm Mixed-mode process (including 3.3V transistors)


- 6 metals layers
- $C_{ox} = 0.0049 \text{ F/m}^2$ (Low voltage 3.3V transistor)
- Gate's minimum width = $0.5 \mu\text{m}$
- Metal/Metal capacitance = $1 \text{ fF}/\mu\text{m}^2$
- Various V_t options

130nm Mixed-mode process (including 3V3 transistors)

- 8 metals layers
- $C_{ox} = 0.0048 \text{ F/m}^2$ (Low voltage 3.3V transistor)
- Gate's width minimum = $0.34 \mu\text{m}$
- Metal/Metal capacitance = $1 \text{ fF}/\mu\text{m}^2$
- Same V_t options


Noise: 130nm vs 180nm (simulation)

- PMOS:

 

130nm
W/L = 2m/0.5u
Ids = 38.79u, Vgs=-190mV, Vds=-600mV
gm=815.245u, gms=354.118u, gds=4.44907u
1MHz → 7.16nV/sqrt(Hz)

 Thermal noise hand calculation = 3.68nV/sqrt(Hz)




180nm
W/L=2m/0.5u
Ids=38.28uA, Vgs=-337mV, Vds=-0.6V
gm=944.4uS, gms=203.1uS, gds=10.2uS
1MHz --> 3.508nV/sqrt(Hz)

Thermal noise hand calculation = 3.42nV/sqrt(Hz)

Noise: 130nm vs 180nm (simulation)

- NMOS :

 

130nm

W/L = 50u/0.5u


Ids=48.0505u, Vgs=260mV, Vds=1.2V

gm=772.031uS, gms=245.341uS, gds=6.3575uS

1MHz --> 24.65nV/sqrt(Hz)

100MHz --> 5nV/sqrt(Hz)

 Thermal noise hand calculation = 3.78nV/sqrt(Hz)



180nm

W/L=50u/0.5u

Ids=47uA, Vgs=300mV, Vds=1.2V



gm=842.8uS, gms=141.2uS, gds=16.05uS

1MHz --> 4nV/sqrt(Hz)

10MHz --> 3.49nV/sqrt(Hz)

Thermal noise hand calculation = 3.62nV/sqrt(Hz)

Architecture of 130nm chip

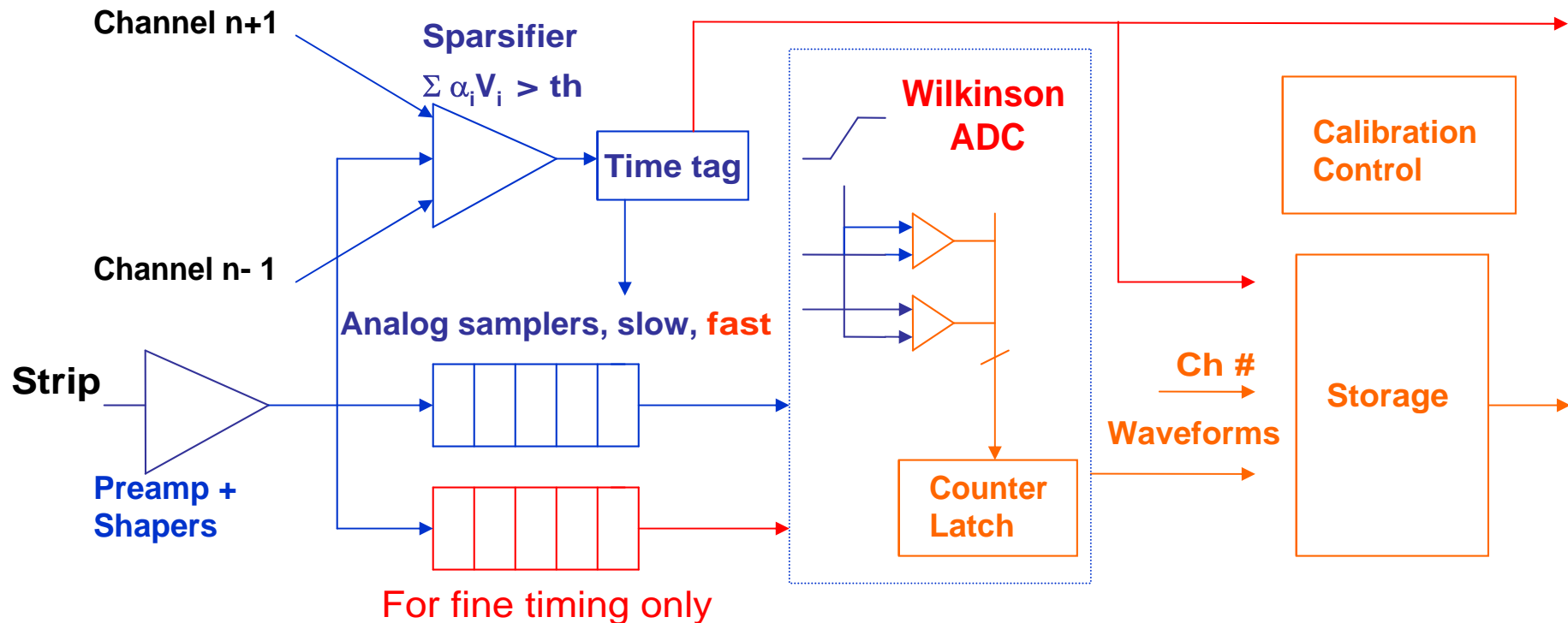 

Charge 1- 40 MIP, S/N~ 15- 20
Time resolution ~ 2ns

Time-stamping on all detector layers
fine time resolution
on some layers: under study

Perspective

- The noise problem is under investigation
- If a solution is found, the chip is expected to be submitted mid-April
- Otherwise, goto:
 - CMOS IBM (less noise according to people from NIKHEF and Pavia) or
 - SiGe (1/f far better, thermal OK)

This document was created with Win2PDF available at <http://www.win2pdf.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.