



# News on the KLauS ASIC



- New KLauS prototype
  - The ASIC
  - Power consumption
  - Digital part & IO

- Test board



Konrad Briggl,  
Huangshan Chen,  
Yonathan Munwes,  
Wei Shen

KIP, Uni Heidelberg



*This project has received funding from the European Union's Horizon 2020 Research and Innovation programme under Grant Agreement no. 654168.*



**AIDA**<sup>2020</sup>

# New multi-channel prototype

**Taped out first multi-channel prototype in May 2016**

Expected back in next weeks

1.5 x 4.5 mm<sup>2</sup> miniASIC (Final 36 channel chip size 5x5mm<sup>2</sup>)

Initially planned 10 channels, limited space did not allow this, so:

**7 Front-End + ADC + digital channel control modules**


1 TDC-only channel (external time reference)

1 ADC test channel (separate)
 
## Digital part

Structured as future 36 channel version

Different readout options: Fast LVDS (160Mbit/s), slow I<sup>2</sup>C link



# Front-end: Blocks

Input stage:

Distribute current signal to 4 processing branches:

Analog processing

“High gain” - *SiPM gain calibration:*  
*Small range, low noise (ENC)*  
*Expected noise  $\sim 3fC$*

“Low gain” :  
*Full SiPM dynamic range*  
*Expected range  $\sim 160pC$*


Comparator branches

Event trigger


*initiate ADC conv., time stamp*  
*Lowest threshold*  
 *$\sim 1-2p.e.$  for  $10\mu m$  MPPC ( $20fC$ )*

HG/LG selection

→ **1 to 1 coupled to ADC**

 
 
# Front-end connection to ADC & Digital part



Front-end outputs in automatic  
HG/LG selection mode

One ADC reading / event  
No analog memory  
Direct conversion to digital

ADC input Selection:

- Force HG readout
- Force LG readout
- Automatic HG/LG
- External source (ADC calib)

2 ADC modes

- 10bit for MIP quantization
- 12bit for single photon spectra

Time stamping

- 12Bit coarse counter (25ns bins)
- TDC with fine bins in future versions



# Power consumption & gated operation

## DC power consumptions (when switched on)

Channel  $\approx 2.9$  mW

Shared bias block  $\approx 2.4$  mW

## Power pulsing control

Single CMOS control pin

Internal power-up delays tunable using the slow control interface

Pedestals stable after  $\sim 10$ - $15\mu\text{s}$

Duty cycle can be reduced towards 0.5%


## Power consumption, pulsed operation

*Extrapolated to 36 channel chip*


*Front-end & ADC, Bias block ; no digital part*

1% duty cycle: **37  $\mu\text{W}/\text{ch}$**

 0.5% duty cycle: **22  $\mu\text{W}/\text{ch}$**



# Digital part: Overview

 

- ① Hit processing in analog stage
- ② Channel digital part: control ADC conversion of peak voltage, storage of TDC data & flags
- ③ Storage in internal buffer (2 levels of FIFOs)
- ④ Serialization through LVDS or I<sup>2</sup>C interfaces

Channel hit counters read out by I<sup>2</sup>C transaction (SMBUS block read)  
 Slow control via SPI, will be replaced by I<sup>2</sup>C later (SMBUS block r/w)



# Digital part: Data flow

Event data only stored in buffer when hit

## 3 Levels of data storage

(L0) – Channel digital part:

For each channel, 2 hits depth

(L1) – First level FIFO buffer:


3 Groups of channels, 64 hits depth

(L2) – Second level FIFO buffer:

For all channel groups, 128 hits depth

→ **Total buffer size 330 hits**

 
Possible to adjust as needed in later versions



# Digital part: Event validation


 
## In first level FIFO:

- Keep events until validation decision
- Drop non validated events in window
  
- Larger matching window
- Configurable width and offset
- External source


  
## During ADC conversion:

- Cancel ADC conversion if not validated
  
- 25ns-200ns window
- External source, or
- Neighboring channels  
(basic coincidence building)



# KLauS4 test board

**New test board is being designed by the KIP electronics workshop**

## **Allows to validate chip in lab-setup**

- Charge injection connectors
- Single SiPMs (pin headers)
- ADC test channel connectors
- Test both read out options (I<sup>2</sup>C, LVDS), analog monitor outputs

→ *Validate chip in lab setup*

Noise, Dynamic range, Powergating behavior ...


*Test performance under realistic conditions*



# KLauS4 test board
 
## Compatibility with CALICE HBU dimensions

- Possibility to participate in future CALICE testbeam campaigns
- SMD MPPC pads distribution similar to HBU
- Form factor & overall height (*PCB thickness, component height*) allow insertion into *EUDET stack*
- LED system design taken from HBU3  
Thanks Mathias & Katja for the input!



# Summary & further development

- 7 channel chip will arrive this month
- Full characterization until end of Q1 2017
  
- Participation in following test beam campaigns planned
- 36 Channel version available until end of 2017 / beg. 2018



Backup slides

# SAR ADC development for KLauS

1 ADC per front-end channel

Development of low power,  
fully differential SAR-ADC

**Two operation modes:**

MIP quantization – **10bit resolution**

9+1(sign) bit SAR ADC

SiPM gain calibration – **12bit resolution**



Additional pipelined stage (8 bit SAR)

Residual amplification & digitization

First prototype:

DNL larger than expected (layout bug)

→ **Improved layout in new version**

  



# Front-End, ADC & channel digital control

## Digital sources from front-end:

- External / self generated trigger
- Gain selection result
- Hold & Start signal for ADC
  
## FE hitlogic block:

- Initiate conversion after peak sampling
- Handshake with ADC control: start, busy
- Mask trigger pulses while ADC is busy



# L0 & Coincidence event validation

## First level event validation:



No validation flag - ADC conversion canceled  
→ Also reduces dead time

## Validation signal sources:


- External source
- Internal validation:
  - Coincident events between channels
  - Configurable OR of group of 12

→ Validation window 1..8 Clock cycles

  → External validation:  
maximum delay: ~300-500ns




# Trigger branch: Threshold setting

 

 **Two DACs to tune threshold:**

- Global 6 bit DAC + scaling (for all channels)
- 4 bit DAC for fine-tuning (each channel)



→ Charge noise: 8fC typ.

→ Threshold configuration resolution (4b DAC): 5fC

# Data structures

**Channel hit information** comprised of 38 bit

To send the data byte-wise, two bits are appended at the end → 5 byte / hit

GRP ID	CHAN_ID	Gain select	ADC busy hit	Main ADC	PIPE ADC	TDC CC
2 bit	4 bit	1 bit	1 bit	10 bit	8 bit	12 bit

## LVDS interface:

- 160Mbit/s, 8b10b encoded data stream
- Frame structure consist of  
Header (clock synchronization, frame size, frame ID), event data and Trailer (CRC16)

## I<sup>2</sup>C interface:

- Raw I<sup>2</sup>C read access from the chip,
- When buffer empty: Invalid events flagged by Channel number == 63