

ILC Modulator Charging supply comments

Richard Cassel SLAC

ILC Modulator Power supply Requirements


- Maximum charge Voltage 12 kV
- Pulse Rate 5 Hz
- Average power Per modulator 150kW
- Input line Voltage AC 3 phase 33kV
- Power Factor 94%?
- Harmonic Content unknown?
- Real Power Variation unknown?
- Total line Voltage Variation a 5-10Hz <0.25%?



Power Lines harmonics or waveform distortion

- Harmonic waveform distortion derives from rectifying the AC line.
- Rectified filter **must have inductor filter** to reduce the unwanted 3rd harmonics on the power line waveform.
- Harmonics can be reused at the source by using a high phase number for the rectifiers
- Although the individual chargers could be 6 phase rectification the total system should have a minimum of 24 phase rectification
- This can be accomplished by phase shifting the step down transformers in groups
- Harmonic filter capacitors may be needed on AC line.
- **(Overall phase number must be at least 24 phase Rectification)**

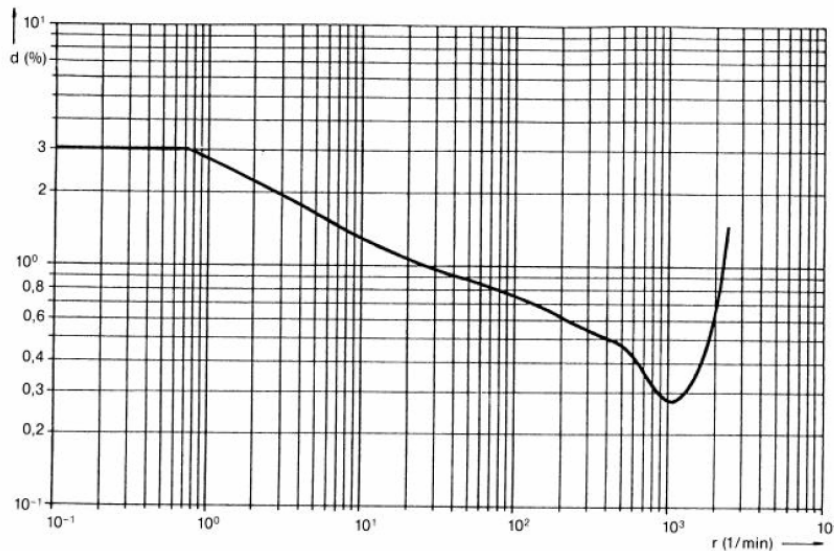Voltage Variations on overall power Lines



From
German standard VDE 0838
Power Supplies for TESLA Modulators
Hans-Jörg Eckoldt, Niels Heidbrook
DESY
TESLA 2000-36

- 3 % Maximum of voltage variation to the public mains Maximum voltage variation allowed at 5-10 Hz < 0.25%
- Actual Variation depends mainly on reactive power and source impedance.
- (Real and Reactive power variation must be minimized)



Voltage Variations Control

- Most transformer in the distribution system will have a real impedance of from 1-2% of full load so that means that the real power must not change by more than 13% of full load over the 0.2 second charge time to meet a 0.25% voltage variation requirement.
- The reactive power is usually the more severe voltage variation problem because the reactive impedance of most transformer (not oversized) is between 4 to 6 % resulting in a reactive power variation of not more than 4% full load over the 0.2 second charge time.
- (Note even a 94% power factor results in a 34% reactive power component.)
- (Overall power Variation during recharge must be less than 10% of the total load)




Voltage Variations Corrections methods

- Use Switching (Bridge, Buck, or Boost type) supply running in constant power mode.
- Provide switching capacitors or synchronic motor to correct or overcorrect reactive power.
- Use series capacitors to correct reactive power
- Use Constant voltage transformer to correct voltage variation
- Use motor- Generator set to isolate pulsed power from the utility lines
- (Switching supplies use to provide constant real and reactive power is the practical solution)



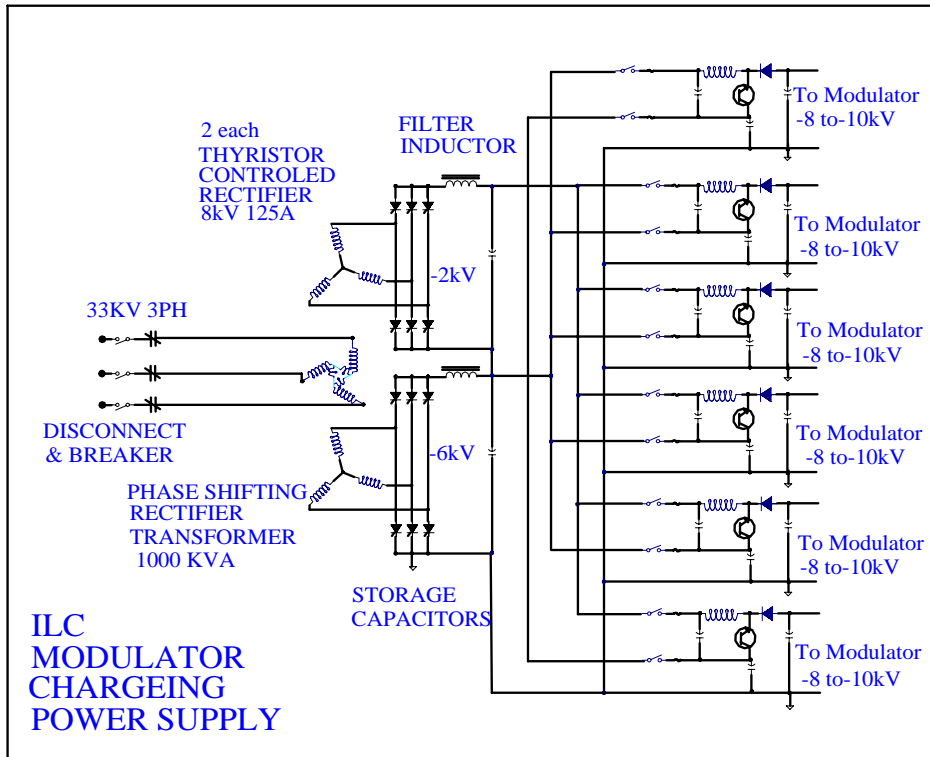Proposed power charging system to reduce costs and utility Line problems



- Drive at least 6 modulator from one step down transformer.
- Use SCRs to initially charge capacitors to 80% of voltage
- Use Boost switching supply to charge from 80% to 100%
- Use phase shifting step down transformer for harmonics
- **Control as constant power charge (Not constant current)**



Conclusions

- 1) Specification should be determinant for power line distortion, and voltage variations for ILC.
- 2) Pulse number of rectification for total system should be at least 24 to reduce harmonic on utility line.
- 3) Filter inductors should be use on every supply to reduce third harmonic
- 4) Switching type supplies should be used to minimize real and reactive power variations during charging of the capacitor banks of the modulators.
- 5) Supplies should be operated in constant power mode to reduce utility line variations.