Lecture B2: Superconductive RF


RF Test of Cavity Homework

T. Saeki (KEK)

LC school 2015

27 Oct. - 6 Nov. 2015, Whistler, Canada

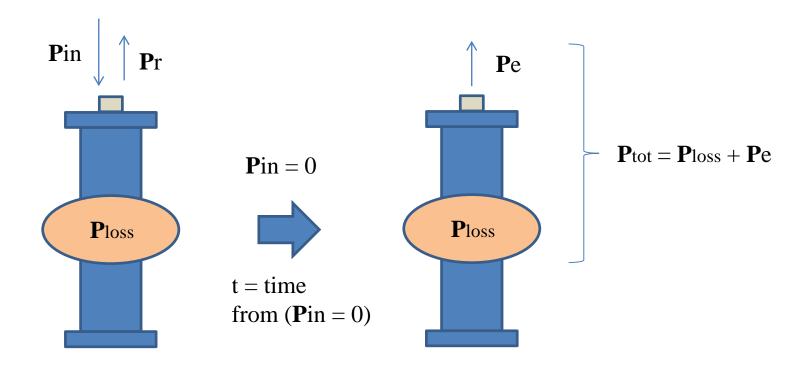Solve this problem and confirm following pages by yourself.




 \mathbf{U} (t) = Stored energy in the cavity, $\mathbf{Q}L$ = Loaded \mathbf{Q} , $\boldsymbol{\omega}$ = Frequency. Think the meaning of following equation.


And find U(t) by resolving the equation with the initial condition: $U(0) = U_{0}$.

$$\frac{d\mathbf{U}(t)}{dt} = -\mathbf{P}_{tot} = -\frac{\boldsymbol{\omega}\mathbf{U}(t)}{\mathbf{Q}_{L}}$$

Theory of Measurement

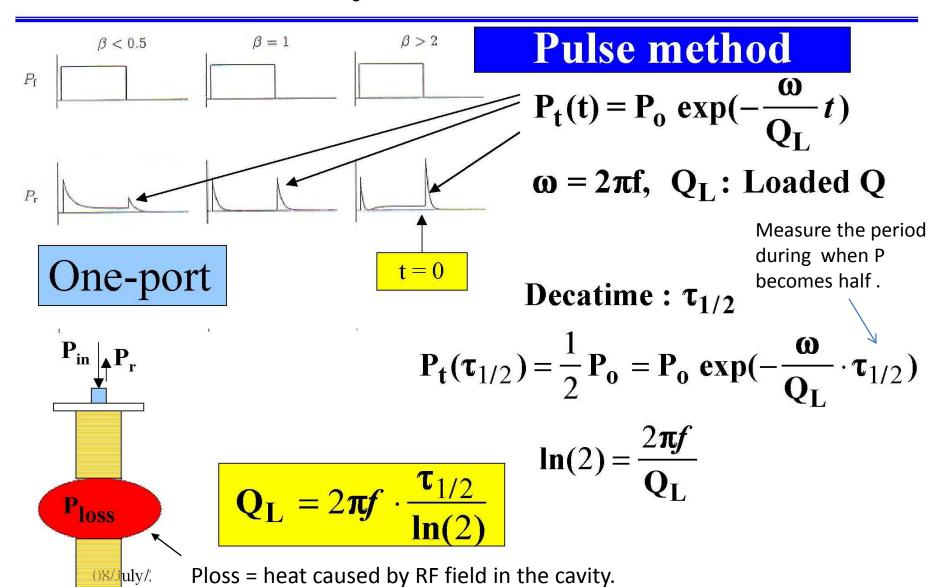

One-Port Cavity

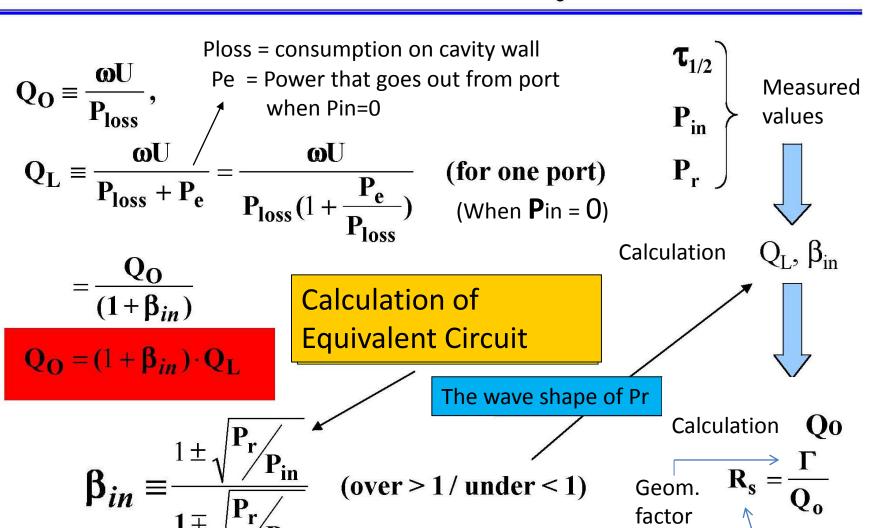


(When \mathbf{P} in > 0)

 $\beta_{in} \equiv \frac{P_e}{P_{loss}}$ (When $P_{in} = 0$)

Surface resistance

Two-Port Cavity

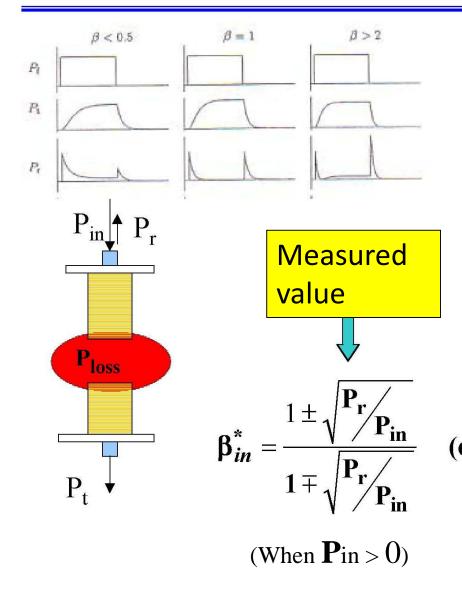

$$\begin{split} & P_{loss}^* = P_{loss} + P_t \quad \text{Ploss of one-port} \\ & Q_o^* = \frac{\omega U}{P_{loss}^*} = \frac{\omega U}{P_{loss} + P_t} \\ & = \frac{\omega U}{P_{loss} \left(1 + \frac{P_t}{P_{loss}}\right)} \quad \text{Measured value} \\ & = \frac{Q_o}{(1 + \beta_t)} \quad \because \quad \beta_t \equiv \frac{P_t}{P_{loss}} \\ & = (1 + \beta_{in}^*)Q_L \quad \qquad \qquad \end{split}$$

$$\beta_{in}^* \equiv \frac{P_e}{P_{loss}^*}$$
 (When $P_{in} = 0$)

$$Q_o^* = \frac{Q_o}{(1+\beta_t)} = (1+\beta_{in}^*) \cdot Q_L$$

$$Q_{o} = (1 + \beta_{in}^{*}) \cdot (1 + \beta_{t}) \cdot Q_{L}$$
$$= \left[1 + (1 + \beta_{t}) \cdot \beta_{in}^{*} + \beta_{t}\right] \cdot Q_{L}$$

$$\mathbf{Q}_0 = (1 + \boldsymbol{\beta}_{in} + \boldsymbol{\beta}_t) \cdot \mathbf{Q}_L \longrightarrow \boldsymbol{\beta}_{in} = (1 + \boldsymbol{\beta}_t) \cdot \boldsymbol{\beta}_{in}^*$$

$$Q_{o} \equiv \frac{\omega U}{P_{loss}}, Q_{t} \equiv \frac{\omega U}{P_{t}} = \frac{\omega U / P_{loss}}{P_{t} / P_{loss}} = \beta_{t}^{-1} \cdot Q_{o}$$

$$\omega U = Q_{o} \cdot P_{loss} = Q_{t} \cdot P_{t}$$


$$Qt = Q_{o} \cdot P_{loss} / P_{t}$$

$P_{loss} = P_{in} - P_r - P_t$

Pin, Pr, Pt : Measured values

Stable Status : h=const ← U const
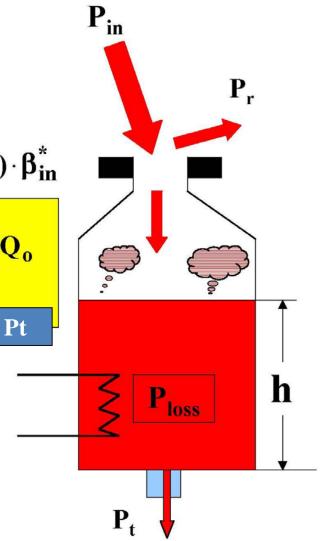
$$\begin{aligned} Q_L &= \omega U / \left(Ploss + Pe + Pt \right) \\ &= Q_0 / \left(1 + \beta in + \beta t \right) \quad when \ Pin = 0 \end{aligned}$$



Calculation of Acceleration Gradient

$$\begin{split} R_{sh} &= \frac{V^2}{P_{loss}} & \because V = E_{acc} \cdot d_{eff} \\ &= (E_{acc} \cdot d_{eff})^2 \text{ / Ploss} \\ &= (E_{acc} \cdot d_{eff})^2 \text{ / Ploss} \\ E_{acc} &= \frac{1}{d_{eff}} \cdot \sqrt{R_{sh} \cdot P_{loss}} = \frac{1}{d_{eff}} \cdot \sqrt{\begin{pmatrix} R_{sh} / Q_O \end{pmatrix} \cdot (Q_O \cdot P_{loss})} \\ &= Z \sqrt{Q_O \cdot P_{loss}} \text{ (One-port)} \\ &= Z \sqrt{Q_t \cdot P_t} \text{ (Two-port)} \\ &= Z \sqrt{Q_t \cdot P_t} \text{ (Two-port)} \\ &\because Q_t &= \frac{\omega U}{P_t} = \frac{Q_o \cdot P_{loss}}{P_t}, \qquad Q_o \cdot P_{loss} = Q_t \cdot P_t \end{split}$$

Set $Qt \gg Q_0$ (Pt \ll Ploss).

Qt is constant during the measurement if using a fixed antenna. Z is independent of surface resistance (material of cavity).

Summary:

Measured parameters:

$$f, \tau_{1/2} \longrightarrow Q_{L} = 2\pi f \tau_{1/2} / ln(2)$$

$$\beta_{in} *= \frac{1 \pm \sqrt{\frac{P_{R}}{P_{IN}}}}{1 \mp \sqrt{\frac{P_{R}}{P_{IN}}}}$$
Stable state (CW)
$$P_{loss} = P_{in} - P_{r} - P_{t}$$

$$\beta_{t} = P_{t} / P_{loss}$$

$$Q_{t} = Q_{O} / \beta_{t}$$

$$\beta_{in} = (1 + \beta_{t}) \beta_{in} *$$


$$Q_{O} = (1 + \beta_{in} + \beta_{t}) Q_{L}$$


$$R_{s} = \frac{\Gamma}{Q_{o}}$$

Eacc =
$$Z \cdot \sqrt{P_t \cdot Q_t}$$
, $Q_0 = Q_t \beta_t$

Control Room of Vertical Test (VT)

Power-meter (Pin, Pr, Pt)

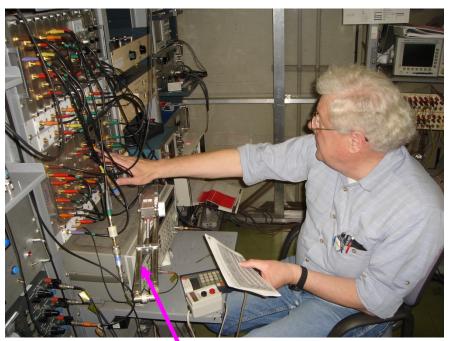

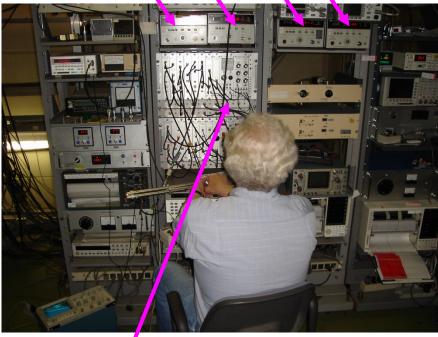


Signal Generator (SG)

Feed-back system (PLL)

Cable Correction

 p_{in} , p_r , p_t : measured in the measurement room

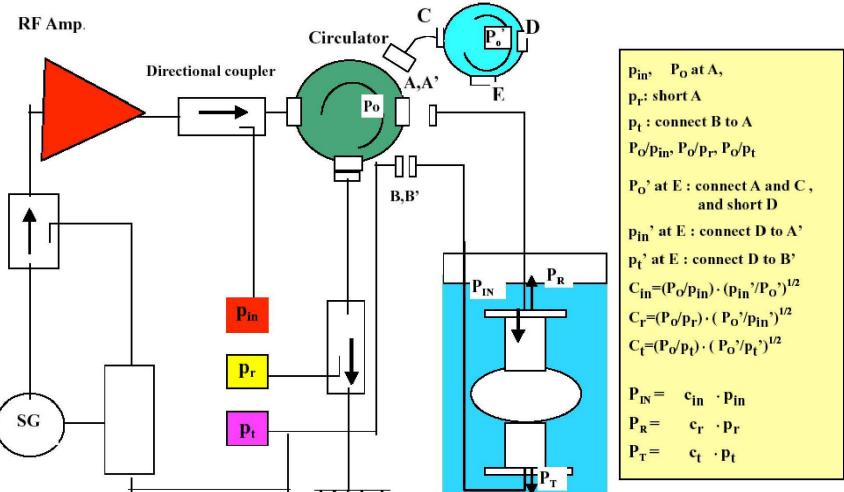 $P_{\text{IN}}, P_{\text{R}}, P_{\text{T}}$: Power at the cavity (cooled), $P_{\text{IN}} = c_{in} \cdot p_{in}$, $P_{\text{R}} = c_{r} \cdot p_{r}$, $P_{\text{T}} = c_{t} \cdot p_{t}$



Feed Back System

